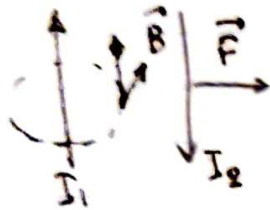


Homework 7


Problem 1

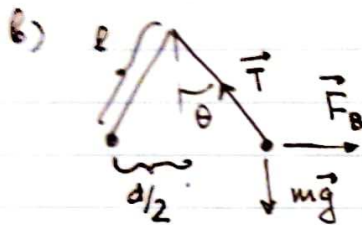a) The magnetic field created by the first current acts on the second (and vice versa). If the two currents are counter-propagating, this force is directed away from the first current.



$$B = \frac{\mu_0 I_1}{2\pi d} \quad F = L I_2 B = \frac{\mu_0 I_1 I_2}{2\pi d} L$$

$$\frac{F}{B/L} = \frac{\mu_0 I^2}{2\pi d} \quad I_1 = I_2$$



Equilibrium: $F_B - T \sin \theta = 0$

$$mg - T \cos \theta = 0$$

$$F_B = mg \tan \theta = \frac{\mu_0 I^2}{2\pi d} L$$

$$\theta = 8^\circ \quad d/2 = l \sin \theta$$


$$d = 2l \sin \theta = 1.67 \text{ cm}$$

$$\frac{m}{L} g \tan \theta = \frac{\mu_0 I^2}{2\pi d}$$

$$I = \sqrt{2\pi d g \tan \theta \cdot \frac{m}{L} \frac{1}{\mu_0}} = 67.8 \text{ A}$$

Written assignment 7 (solutions)

Q2.

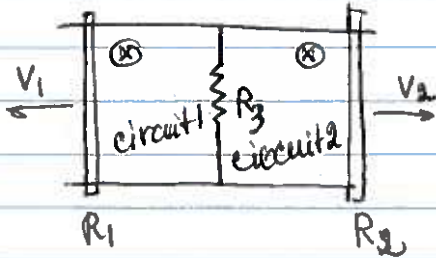

Circuit 1

$$\Delta\Phi_1 = B \cdot d \cdot v_1 \Delta t$$


$$\mathcal{E}_1 = \left| - \frac{\Delta\Phi_1}{\Delta t} \right| = B d v_1$$

Circuit 2

$$\Delta\Phi_2 = B d v_2 \Delta t$$

$$\mathcal{E}_2 = \left| - \frac{\Delta\Phi_2}{\Delta t} \right| = B d v_2$$

Equivalent circuit

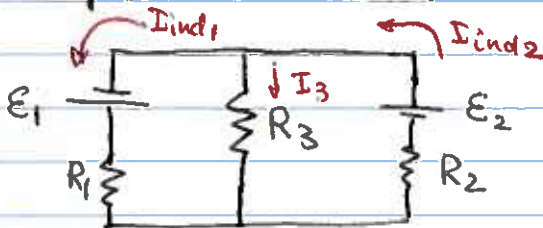

Kirchhoff's rules

$$\begin{cases} I_2 = I_1 + I_3 & (1) \\ \mathcal{E}_2 - I_3 R_3 - I_2 R_2 = 0 & (2) \\ \mathcal{E}_1 - R_1 I_1 + I_3 R_3 = 0 & (3) \end{cases}$$

$$I_1 = \frac{\mathcal{E}_1}{R_1} + I_3 \frac{R_3}{R_1} \quad \text{from (3)}$$


$$I_2 = \frac{\mathcal{E}_2}{R_2} - I_3 \frac{R_3}{R_1} \quad \text{from (2)}$$

$\mathcal{E}_{1,2}$ direction \rightarrow from Lenz rule
to reduce the flux

$$\text{from (1)} \quad \frac{\mathcal{E}_2}{R_2} - I_3 \frac{R_3}{R_2} = \frac{\mathcal{E}_1}{R_1} + I_3 \frac{R_3}{R_1} + I_3$$

$$\frac{\mathcal{E}_2}{R_2} - \frac{\mathcal{E}_1}{R_1} = I_3 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right)$$
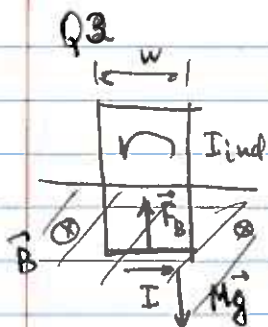
$$I_3 = \frac{\mathcal{E}_2/R_2 - \mathcal{E}_1/R_1}{1 + \frac{R_3}{R_1} + \frac{R_3}{R_2}} = B \cdot d \frac{v_2/R_2 - v_1/R_1}{1 + R_3/R_1 + R_3/R_2}$$




$$\frac{d\Phi_B}{dt} = Bw \cdot v = |\mathcal{E}_{\text{ind}}|$$

$$I_{\text{ind}} = \frac{\mathcal{E}_{\text{ind}}}{R} = \frac{Bwv}{R}$$

$$F_B = w \cdot B I_{\text{ind}} = \frac{B^2 w^2 v}{R}$$

In the beginning v is small, so the loop accelerates down $F_B - Mg = ma$ $a < 0$ (down)
 However, as v increases, F_B approaches Mg , and the velocity increase becomes smaller
 For the terminal velocity
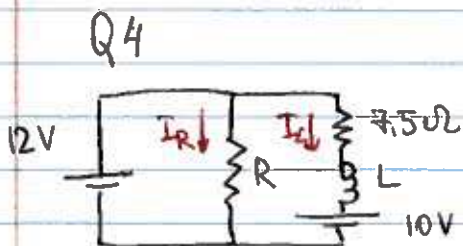
$$Mg = F_B = \frac{B^2 w^2 v_t}{R} \Rightarrow v_t = \frac{MgR}{B^2 w^2}$$




Before disconnect

$$I_R = 12V/R$$

$$12V = I_L \cdot 7.5\Omega + 10V$$

$$I_L = \frac{2V}{7.5\Omega}$$

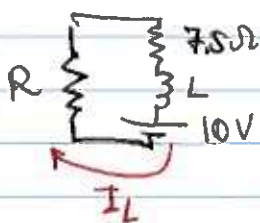Once the 12V battery is disconnected, the inductance will prevent I_L to change instantaneously.




So at the first moment the current through the resistor R is also I_L , and the voltage drop is

$$V_R = I_L \cdot R \Rightarrow R = \frac{V_R}{I_L} = \frac{80V}{\frac{2V}{7.5\Omega}}$$

$$R_{\text{max}} = 300\Omega$$

Q5

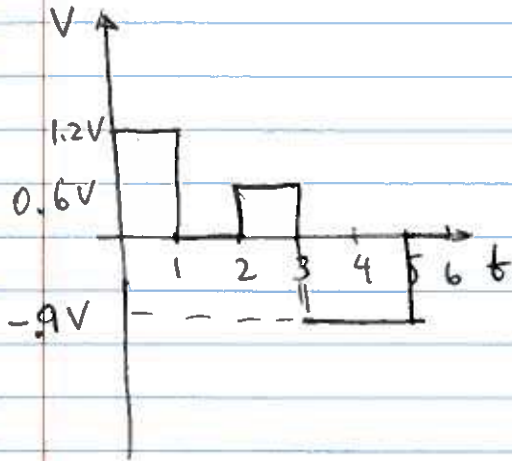

$$0-1s \quad \frac{dI}{dt} = -6A/s \quad V = -L \frac{dI}{dt} = 1.2V$$

$$1-2s \quad \frac{dI}{dt} = 0 \quad V = 0$$

$$2-3s \quad \frac{dI}{dt} = -3A/s \quad V = 0.6V$$

$$3-5s \quad \frac{dI}{dt} = 4.5A/s \quad V = -0.9V$$

$$5-6s \quad \frac{dI}{dt} = 0 \quad V = 0$$