

Electric circuits with batteries and resistors

Series connection




$$I_1 = I_2 = I \text{ same current}$$

$$V_1 = IR_1 \quad V_2 = IR_2$$

$$V_{\text{tot}} = V_1 + V_2$$

Paralled connection

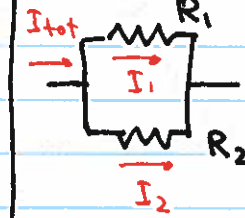

$$V_1 = I_1 R_1$$

$$V_2 = I_2 R_2$$

$$V_1 = V_2$$

$$I_1 + I_2 = I_{\text{total}}$$


Connection to the battery



$$I_0 = \frac{E}{R}$$

$$P_0 = I \cdot V = \frac{E^2}{R}$$

Series connection

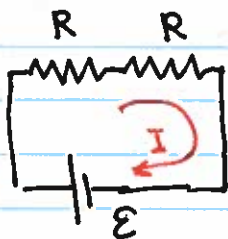

$$I_s = \frac{E}{2R} \quad (\text{lower than for one resistor})$$

Power dissipated on a single bulb

$$P = I^2 \cdot R = \frac{E^2}{4R^2} \cdot R = \frac{E^2}{4R}$$

Four time dimmer than a single bulb

Parallel connection



Current through each resistor

$$I_p = \frac{E}{R} \quad \text{same as for a single resistor}$$

Power dissipated on a single resistor


$$P = I_p^2 \cdot R = \frac{E^2}{R} \quad \text{same}$$

Total current



drawn from the battery

$$I = 2I_p = \frac{2E}{R}$$

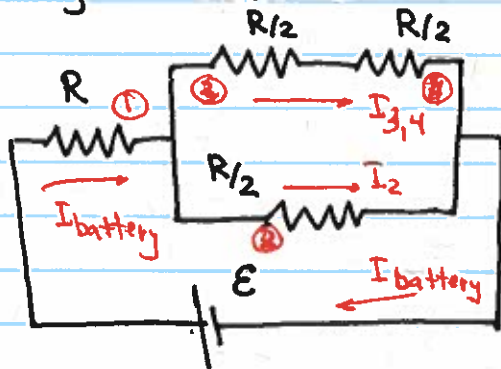Circuits with one battery and many resistors



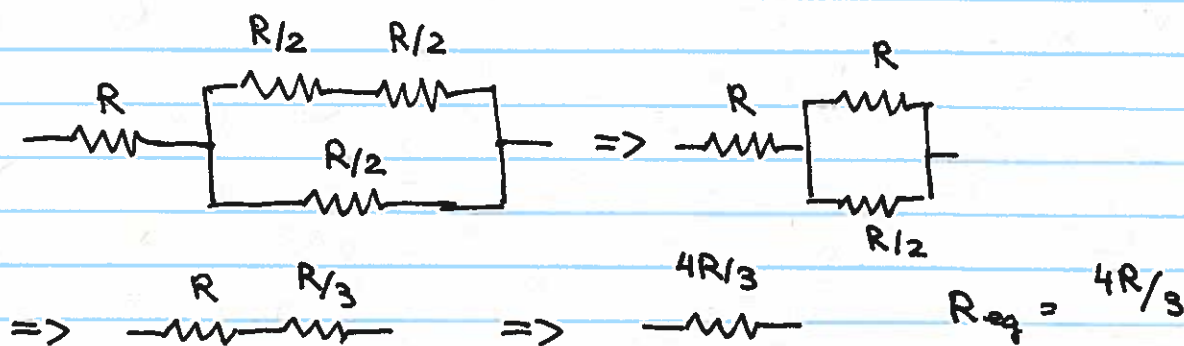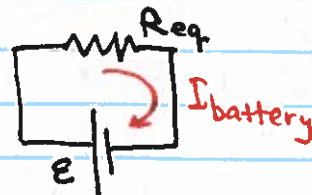1. Let's find I_{battery} by calculating the equivalent resistance




$$I_{\text{battery}} = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{3\mathcal{E}}{4R}$$


What is the current and the voltage drop on each of the resistors?

Resistor	Current	Voltage
1	$I_1 = I_{\text{battery}}$	$V_1 = R \cdot I_{\text{battery}} = \frac{3\mathcal{E}}{4}$
2	$I_2 = \frac{V_2}{R/2} = \frac{\mathcal{E}}{2R}$	$V_2 = \mathcal{E} - \frac{3\mathcal{E}}{4} = \frac{\mathcal{E}}{4}$
3,4	$I_{3,4} = I_{\text{battery}} - I_2 = \frac{\mathcal{E}}{4R}$	$V_3 = V_4 = I_{3,4} \cdot \frac{R}{2} = \frac{\mathcal{E}}{8}$

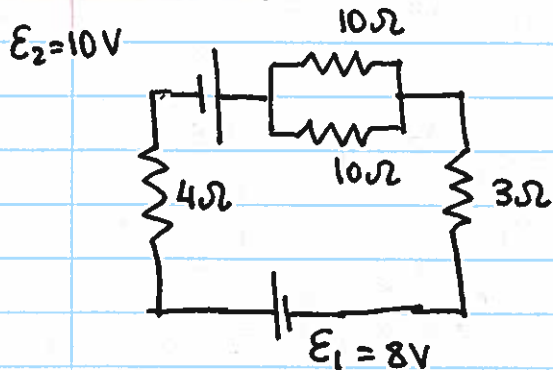More complex circuits with multiple batteries



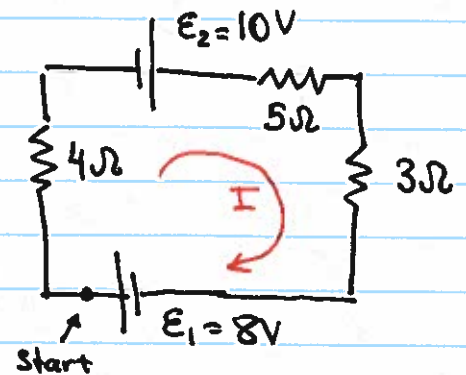can be equivalent to a single loop \Rightarrow




In a single loop total voltage drop must be zero

$$-4\Omega \cdot I + 10V - 5\Omega \cdot I - 3\Omega I + 8V = 0$$

$$18V = 12\Omega \cdot I \quad I = 3/2 A$$

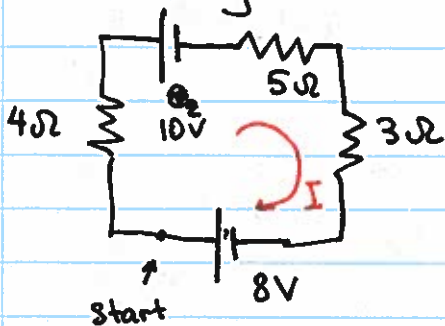What if I accidentally connect the second battery backwards?



$$-4\Omega \cdot I - 10V - 5\Omega \cdot I - 3\Omega \cdot I + 8V = 0$$

$$-2V = 12\Omega \cdot I$$

$$I = -\frac{1}{6} A$$

Minus sign means we guessed the wrong direction for the current