
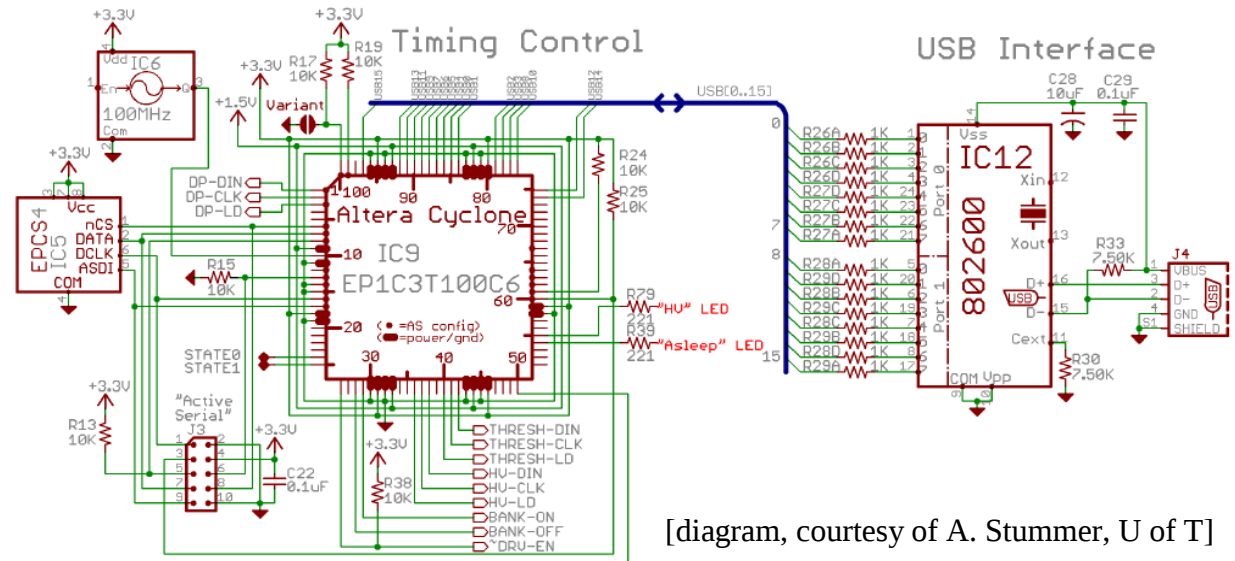


Physics 351: Electronics II

Introduction to Digital Circuits

Prerequisites: PHYS 252.

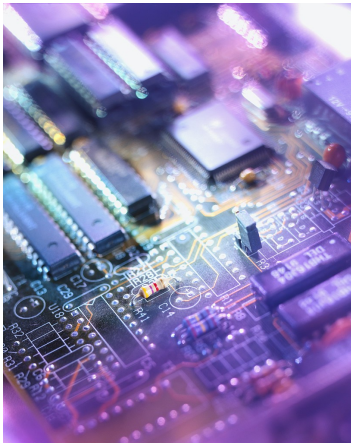Introduction to digital electronics: Theory, design, and application of digital circuits ... or how to understand and make circuits like these:



Small print: If you don't have any experience with analog electronics you should talk to me after class.

Instructors

A. Dayle Hancock

Office: Small 239, telephone: 221-3503

e-mail: adhancock@wm.edu

web: <http://physics.wm.edu/~hancock/351>

Office hours Monday 1-2pm, Wednesday 1-2pm

Charlie Fancher

Office: Small 320B

e-mail: ctfancher@email.wm.edu

Course Objectives

Primary: Design and test both basic and advanced digital circuits for *digital logic*, *signal acquisition*, and *digital signal processing*.

Secondary: Learn experimental research skills.



Covered topics:

- Binary numbers, logic gates, and Karnaugh maps.
- Memory, flip-flops, and clocked latches.
- Clocks, timing, and one-shots.
- Counters, registers, and state machines.
- Analog-to-Digital Converters (ADC) and Digital-to-Analog Converters (DAC).
- Optical and magnetic isolation.
- **Field Programmable Gate Arrays (FPGA).**
- Verilog language FPGA programming.
- **Digital Signal Processing (DSP).**
- Microprocessors.

FPGAs for Physicists

Field Programmable Gate Array (FPGA) chips for physicists

- Contain 2,000-100,000 logic gates + memory.
- Reprogrammable via a computer (Quartus II v7-9).
- Stand alone circuitry (with flash memory).
- Parallel processing.
- ***Useful for complex circuits and Digital Signal Processing (DSP).***



Note: Quartus II is available on lab computers

DSP design project (I)

A central component of the course is an FPGA-based digital signal processing (DSP) project. The general guidelines for the projects are:

- Teams of 2-3 students (depends on lab section distribution).
- Each team has a budget of \$150 USD.
- All teams have the same project.
- This section of the course is a design and construction competition.

The purpose of the one month team project is to help you develop practical circuit design skills, as well as the following more general research skills:

- Complex device design.
- Project budgeting.
- Formal project proposal writing.
- Finding, selecting, and purchasing device components.
- Device construction.
- Troubleshooting and debugging.
- Oral and web presentations of the device.

DSP design project

The design project:

- Digital **DSP VOICE RECORDER** with playback
 - 1 analog input (i.e. microphone).
 - 1 analog output (i.e. speaker).
 - FPGA core.
 - Comments: more memory handling, more involved analog.



DSP design project (III)

- Easier project than last year, with more project time scheduled.
- The project will be based on an FPGA.
- The specific project requirements will be announced next week.
- The project is the most important part of the course.
- It will be graded according to the following weights:

Formal project proposal	10%
Device construction	15%
Device performance	15%
Web presentation of device	5%
<u>Project lab book</u>	<u>5%</u>
Total	50%

Evaluation

Notebooks:	40%
Participation:	10%
<u>DSP project:</u>	<u>50%</u>
Total =	100%

Note: There is no final exam for the course

Due Dates

➤ **Lab books**

In addition to lab notes, the lab books should include all design exercises.

Lab books are due by 5pm on Fridays after lab & will be returned by the next lab period:

Introduction to Digital Logic

Digital Variables

A digital circuit has only 2 possible values HIGH (H or 1) and LOW (L or 0)

→ Does not need to be precision designed.

→ Not very sensitive to electronic noise.

Here are a few voltage-logic conventions:

Convention	Supply	LOW	HIGH	Speed
TTL	+ 5 V	< 0.7 V	> 2.0 V	~5 nS
LVTTL	+ 3.3 V	< 0.7 V	> 2.0 V	~5 nS
CMOS	+ 3-15 V	< 20% Supply	> 80% Supply	~10 nS
GaAs	undefined	undefined	undefined	~100 pS

Digital vs. Analog

Digital

- Easy to design (linear logic flow).
 - No feedback !
- Insensitive to electronic noise.
- Easy to design and make very complex circuits.
- Insensitive to specific components.
- Reliable isolation circuitry.
- Tends to consume a lot of power.
- Slower than analog equivalent.
- Very bad if a single bit is corrupted (std. error rate 1 part per 10^{10}).
 - Error correction is important.

Analog

- Harder to design and read a circuit, especially with feedback.
- Noise is critical.
- Complex circuits are hard to design.
- Sensitive to specific components and quality of assembly.
- Isolation circuitry reduces accuracy.
- Can be low power.
- Very fast.
- Some circuits must be analog.

Transistor-Transistor-Logic (TTL)

In this course, we will use almost exclusively the TTL family of logic chips.

Characteristics:

- Very reliable.
- Widely available.
- Silicon-based with bipolar transistors.
- Supply: + 5 V, High > 2 V, Low < 0.7 V
- 1 output can drive 10 inputs (fanout = 10).
- Never leave an input (or output) floating: it will tend to wander between H and L.


CAUTION: If any of your voltages are close to the range 0.7 – 2.0 V, then you should check your circuit and the components.

Boolean Operators

Identity

1 input \rightarrow 1 output

0 input \rightarrow 0 output

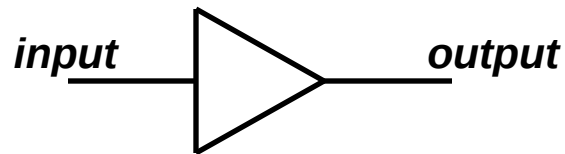


(also called a buffer)

Inverter

1 input \rightarrow 0 output

0 input \rightarrow 1 output

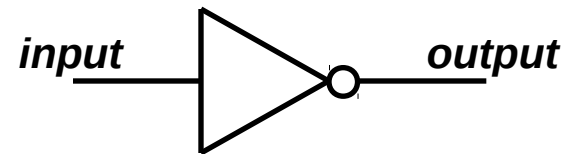


Note: Boolean (adj.) refers to something that is 2-valued (named after G. Boole, 1815-1864).

2-input operators

AND

→ Outputs H only if both inputs are H.

→ Written as a product:
 $Y=AB$

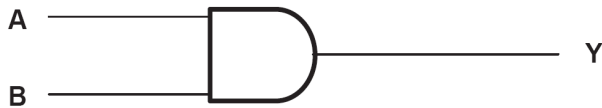

INPUTS		OUTPUT
A	B	$AB = Y$
L	L	L
L	H	L
H	L	L
H	H	H

OR

→ Outputs H only if either input is H.

→ Written as a sum:
 $Y=A+B$



INPUTS		OUTPUT
A	B	$A+B = Y$
L	L	L
L	H	H
H	L	H
H	H	H

More operators

NAND



INPUTS		OUTPUT
A	B	$\overline{AB} = Y$
L	L	H
L	H	H
H	L	H
H	H	L

NOR




INPUTS		OUTPUT
A	B	$\overline{A+B} = Y$
L	L	H
X	H	L
H	X	L

X = don't care (H or L)

A little bit of analog

Analog realization of a NOR gate

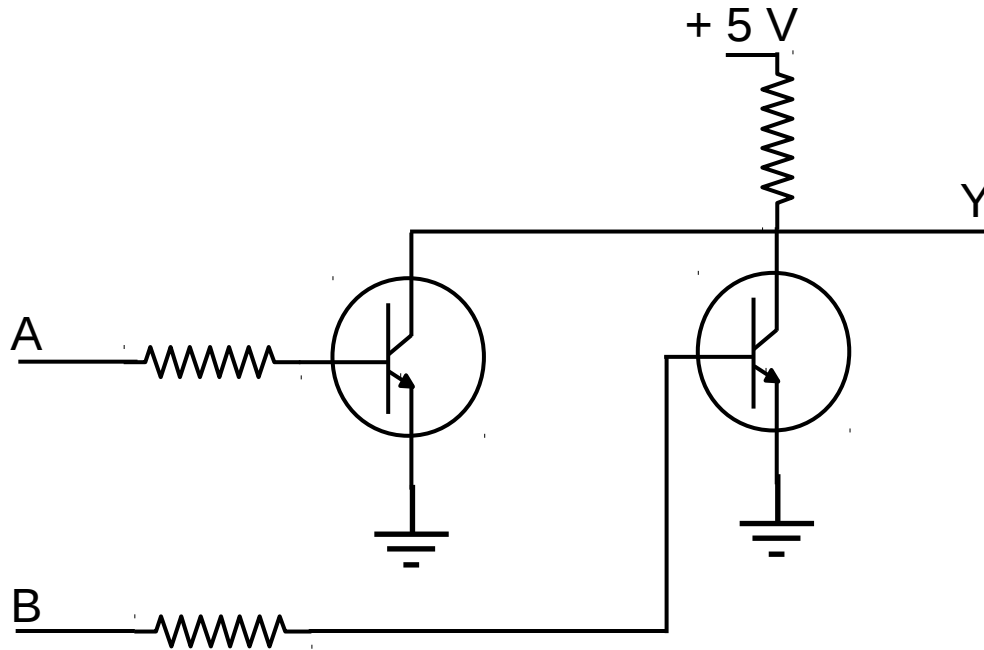

INPUTS		OUTPUT
A	B	$\overline{A+B} = Y$
L	L	H
X	H	L
H	X	L

Boolean logic identities

Associative

$$ABC = (AB)C = A(BC)$$

$$A+B+C = (A+B)+C = A+(B+C)$$

Commutative

$$AB = BA$$

$$A+B = B+A$$

Others

$$AA = A$$

$$A1 = A$$

$$A0 = 0$$

$$A+A = A$$

$$A+1 = 1$$

$$A+0 = A$$

$$A + AB = A$$

$$A+BC = (A+B)(A+C)$$

$$A + \bar{A} = 1$$

$$A \bar{A} = 0$$

$$A + \bar{A} B = A+B$$

DeMorgan's Theorem

$$\overline{A+B} = \bar{A} \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

Exclusive OR


XOR

- Outputs H if either input is H, but not both.
- Written as a plus sign with a circle around it: $Y=A\oplus B$

INPUTS		OUTPUT
A	B	$A\oplus B = Y$
L	L	L
L	H	H
H	L	H
H	H	L



XOR realization

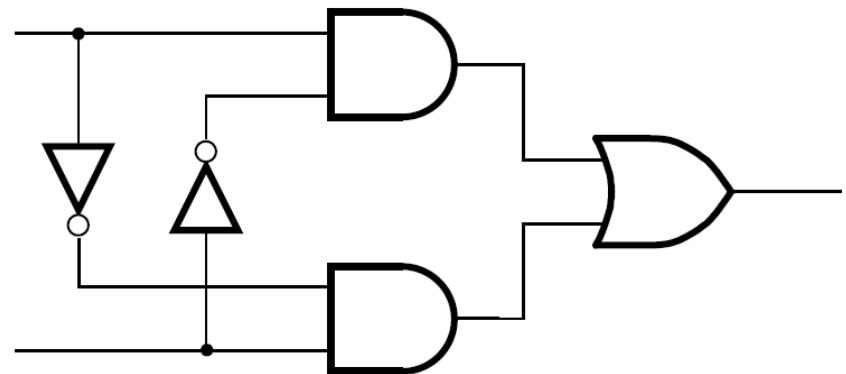

[diagram courtesy of Altera Inc.]

The NAND and NOR gates

DeMorgan's theorem corollary:

Any logic gate or operation can be constructed exclusively of NAND gates (or NOR gates).

Note: a NAND gate with the inputs tied together is a NOT gate.

Hardware



Name	Expression	Inputs	Part #
AND	AB	2 (also 3&4)	74xx08
NAND	\overline{AB}	2 (also 3&4)	74xx00
OR	$A+B$	2 (also 3&4)	74xx32
NOR	$\overline{A+B}$	2 (also 3&4)	74xx02
Invert	\overline{A}	1	74xx04
Buffer	A	1	74xx365
XOR	$A\oplus B$	2 (also 3&4)	74xx86 / 386
XNOR	$\overline{A\oplus B}$	2 (also 3&4)	74xx266

Note: We will use mostly Low Speed TTL (xx = LS).

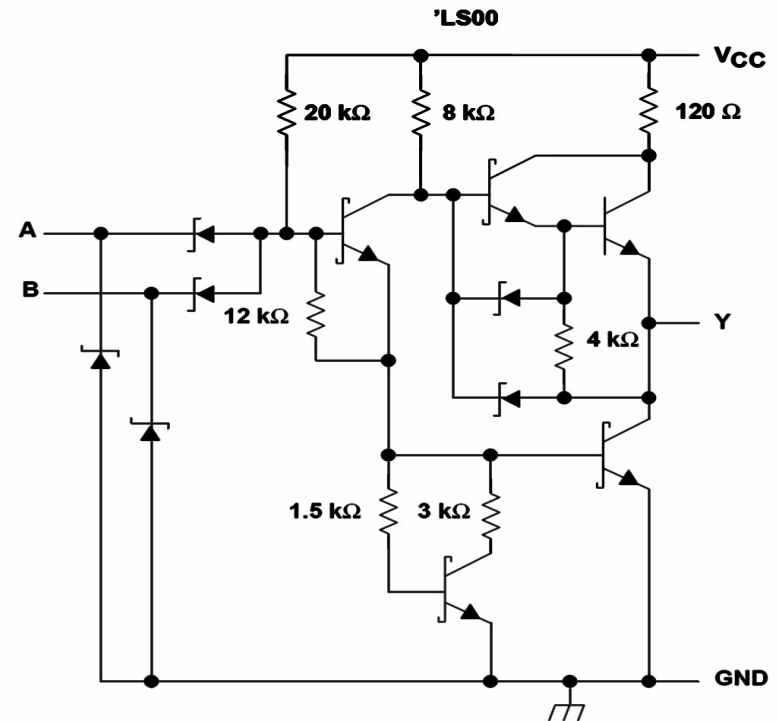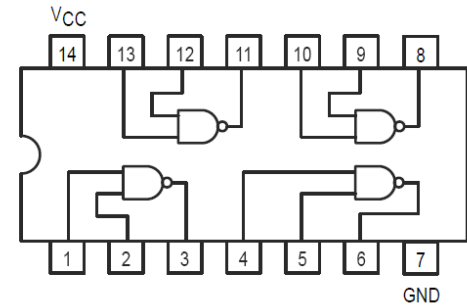Example: 74LS00

Quad NAND gate chip

- 4 gates per chip.
- Requires + 5 V of power at Vcc.
- Requires a ground connection at GND.
- Never float an input (i.e. it will wander between 0 and 1).
- Each gate consists of about 20 components.



Karnaugh Maps (I)

Logic table \rightarrow Karnaugh Map \rightarrow digital logic circuit

- Up to 4 inputs, 1 output.
- Always gives a solution, though not the most efficient one.

Example:

- 3 person vote.
- 2-person majority produces H output.

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Karnaugh Maps (II)

- Arrange inputs on either one of the two table axes.
 - Up to 2 inputs per axis.
 - Order of inputs is important: only one input change per row or column.
- (note: column order is circular.)

	A	L	L	H	H
	B	L	H	H	L
C					
L		L	L	H	L
H		L	H	H	H

Karnaugh Maps (II)

- Arrange inputs on either one of the two table axes.
- Up to 2 inputs per axis.
- Order of inputs is important: only one input change per row or column.
- Group together the adjacent “ones”: these correspond to AND gates.
- Alternatively, group adjacent “zeros”: these correspond to OR gates.
- Write down the corresponding AND gates: AB, BC, AC

	A	LL	L	H	H
	B		H	H	L
C					
L		L	L	H	L
H		L	H	H	H
			BC	AB	AC

Solution: $AB + BC + AC$

Karnaugh Maps (III)

		A	0	0	1	1
		B	0	1	1	0
C	D					
	0	0	1	1	0	1
0	1	0	1	0	0	
1	1	0	1	1	0	
1	0	1	1	1	0	

Karnaugh Maps (III)

		A	0	0	1	1
		B	0	1	1	0
C	D					
	0	0	1	1	0	1
0	1	0	1	0	0	
1	1	0	1	1	0	
1	0	1	1	1	0	

Karnaugh Maps (III)

		A			
		0	0	1	1
C \ D		B			
		0	1	1	0
0	0	1	1	0	1
0	1	0	1	0	0
1	1	0	1	1	0
1	0	1	1	1	0

AD (circled in green)
AB (circled in red)
BC (circled in blue)
BCD (circled in orange)

Solution: $\bar{A}B + BC + \bar{A}\bar{D} + \bar{B}\bar{C}\bar{D}$

Binary Numbers

Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

Base 2 (i.e. binary numbers)

$$\begin{aligned} 10011101 &= 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2 \\ &= 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10} \end{aligned}$$

Binary Numbers

Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

Base 2 (i.e. binary numbers)

$$10011101 = 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2$$

$$\text{1-bit} = 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10}$$

8-bits = 1 byte

Binary Numbers

Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

Base 2 (i.e. binary numbers)

$$10011101 = 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2$$

$$\text{1-bit} = 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10}$$

8-bits = 1 byte

Base 16 (i.e. Hexadecimal numbers)

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

Decimal → Binary

- To convert from decimal to binary
 - Divides by 2 repeatedly & write the remainders
- To convert 13_{10} to binary
 - $13/2 = 6$ remainder 1
 - $6/2 = 3$ remainder 0
 - $3/2 = 1$ remainder 1
 - $1/2 = 0$ remainder 1
- The digits come out in **right to left** order
 - $13_{10} = 1101_2$

Binary Addition

➤ Examples

$$0101_2 + 0010_2 = 0111_2$$

$$0101_2 + 0001_2 = 0110_2$$

$$0111_2 + 0001_2 = 1000_2$$

➤ Differences between decimal & binary addition...

- In binary we carry half the time, on average.
- There are only a limited number of possible operands & resultants (1s or 0s).
- Makes digital implementation fairly simple.