

# Flip-Flops

## Outline:

### 2. *Timing noise*

- Signal races, glitches
- FPGA example (“assign” → bad)

- *Synchronous circuits and memory*

- Logic gate example

### 4. *Flip-Flop memory*

- RS-latch example

- *D and JK flip-flops*

- Flip-flops in FPGAs

- *Synchronous circuit design with FPGAs*

- FPGA example (“always” → good).
- Parallel circuit design with FPGAs.

# Timing noise

## Amplitude Noise

A digital circuit is very immune to amplitude noise, since it can only have two values (Low or High, True or False, 0 or 1). Digital electronics circuits typically have error rates smaller than 1 part in  $10^9$  (no error correction).

## Timing Noise



Just like an analog circuit, a digital circuit can experience timing noise. Fortunately, good clocks are cheap and easily available, and a good design will eliminate the effects of timing noise.

Timing issues/errors can easily produce amplitude noise (bit errors).

# Signal Race

The timing delays produced by wires and logic gates can produce unwanted (illogical) outputs.



Example: 3-input NAND gate

  

# Signal Race

The timing delays produced by wires and logic gates can produce unwanted (illogical) outputs.



Example: 3-input NAND gate

  


# Signal Race

The timing delays produced by wires and logic gates can produce unwanted (illogical) outputs.

Example: 3-input NAND gate

  


# Signal Race with Glitch

 

[diagram courtesy of Altera Inc.]


XOR

A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

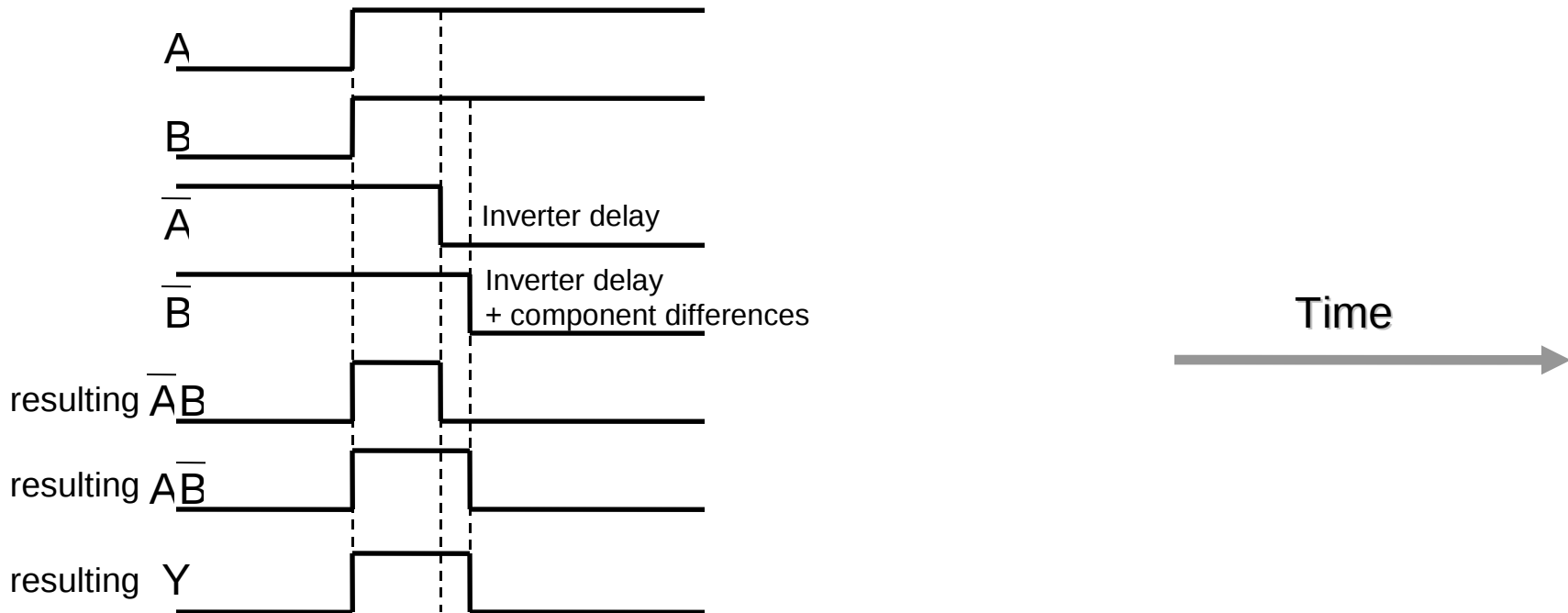

[Figure adapted from *Principles of Electronics: Analog & Digital* by L. R. Fortney]


# Signal Race with Glitch

 

[diagram courtesy of Altera Inc.]

XOR

A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

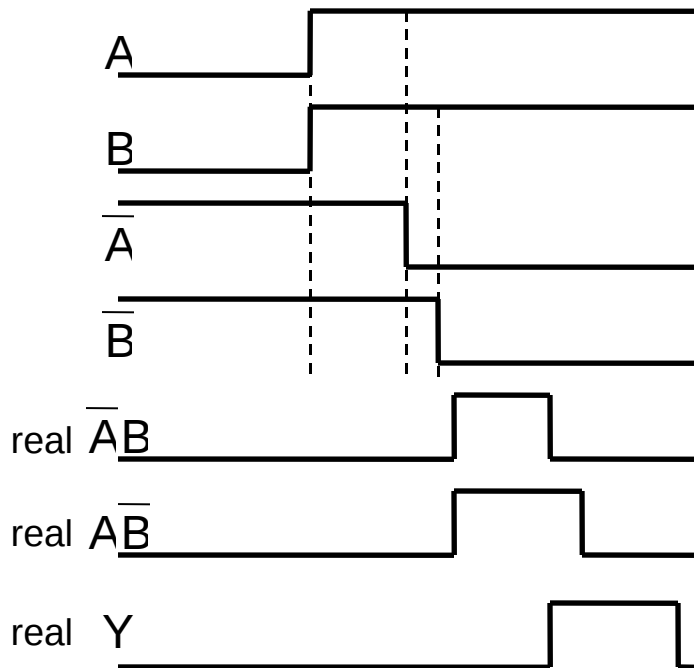


Time →

[Figure adapted from *Principles of Electronics: Analog & Digital* by L. R. Fortney]
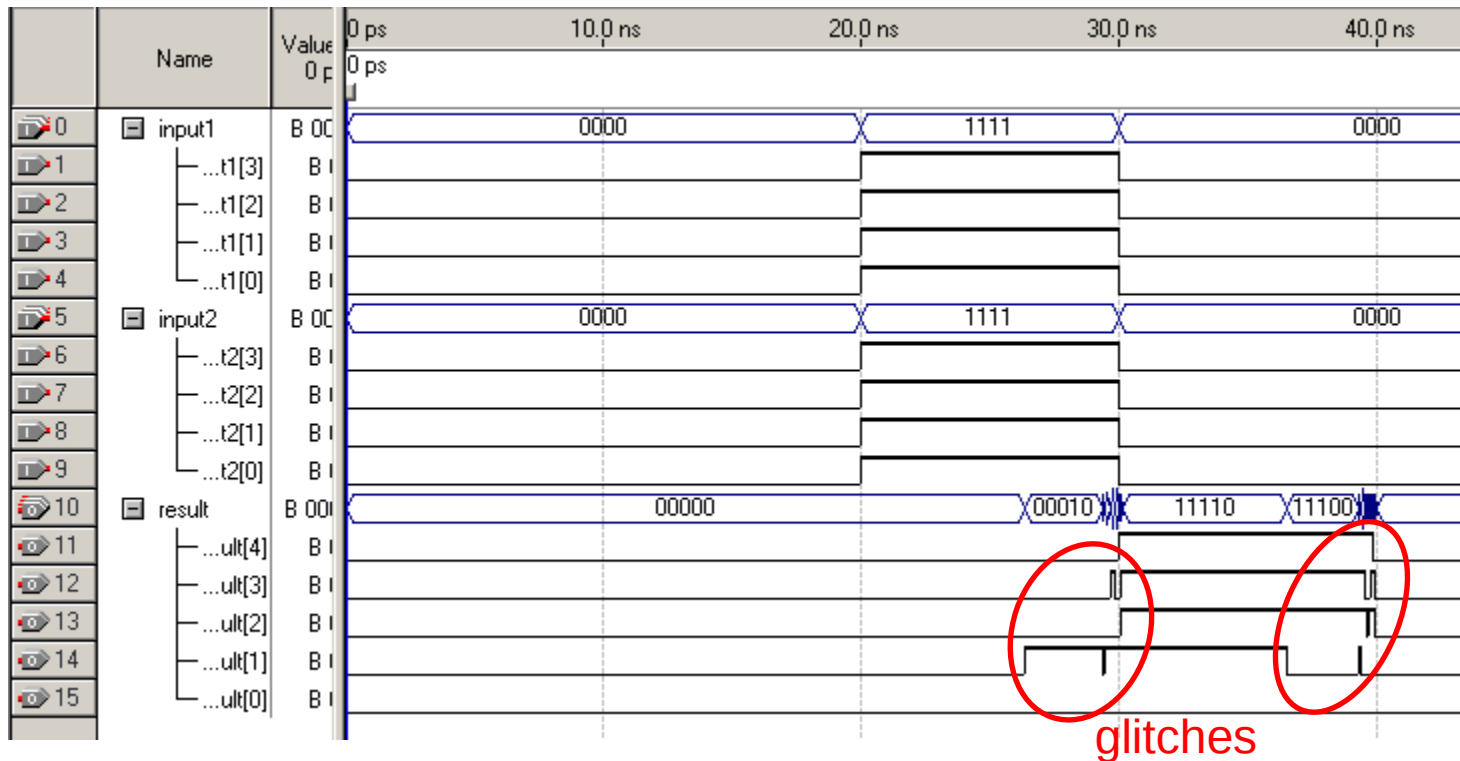
# Glitches with FPGAs

Quartus II will simulate glitches

```
1 module adder_assign(input1, input2, result);  
2     input [3:0] input1;  
3     input [3:0] input2;  
4     output [4:0] result;  
5  
6     assign result = input1 + input2;  
7  
8 endmodule  
9
```





# Asynchronous Design

**Asynchronous design** requires very careful attention to signal delays to avoid producing glitches and other spurious signals.


**Glitches** will produce false data and can produce very wrong results

e.g. a glitch on the most-significant-bit will produce a factor of 2 error.

Asynchronous design can produce very fast digital circuits, but is generally avoided due to more difficult design.
 
# Synchronous Design

The use of **memory** and a **clock** can eliminate signal races and glitches.




## Basic flip-flop operation

The flip-flop will record and output the value at the input if the **clock** is HIGH. If the **clock** goes LOW, then the flip-flop does not change its value or output.



- Glitches are eliminated if
1. The clock HIGH and LOW times are longer than any gate delays.
  2. The inputs are synchronized to the clock.

# Synchronous Timing

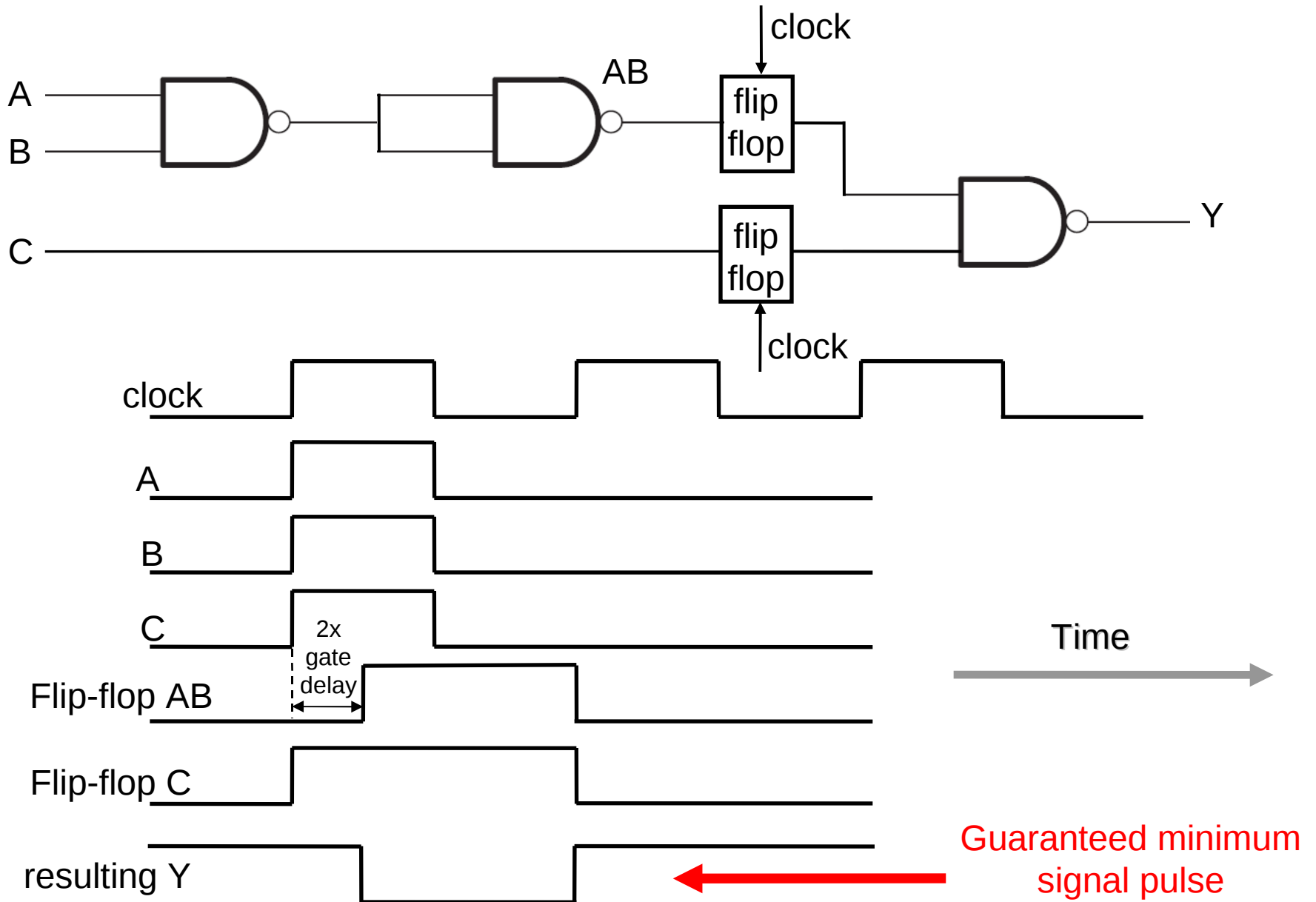
 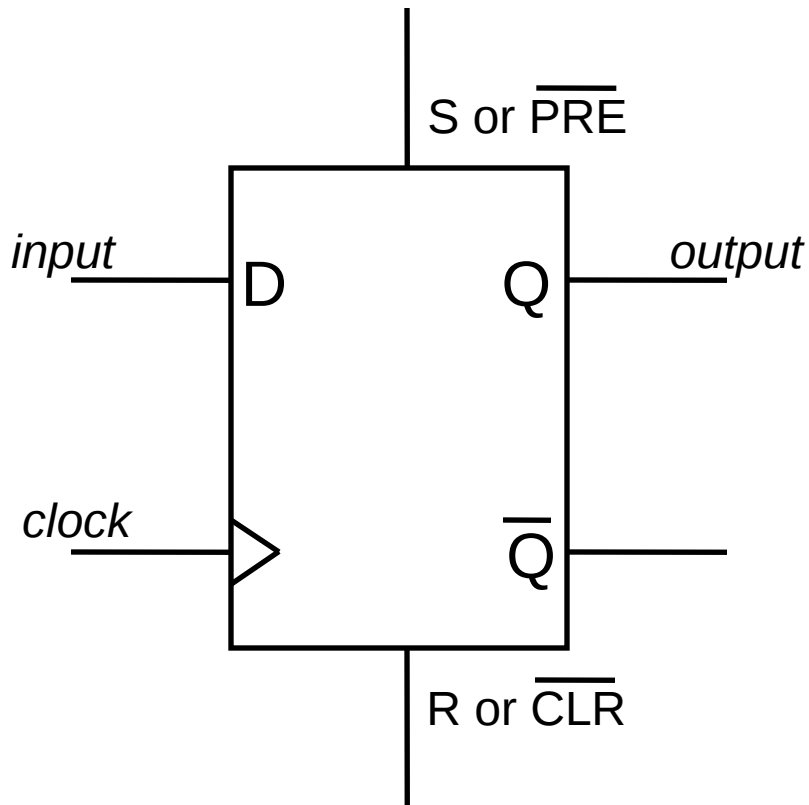
# D-type Edge-Triggered Flip-Flop

Generally, the flip-flop changes state on a clock signal “edge”, not the level. The flip-flop takes the value *just before* the clock “edge”.



For 74LS74: minimum  $t_s = 20\text{ ns}$   
 minimum  $t_h = 5\text{ ns}$

FUNCTION TABLE



INPUTS				OUTPUTS	
$\overline{PRE}$	$\overline{CLR}$	CLK	D	Q	$\overline{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H <sup>†</sup>	H <sup>†</sup>
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q <sub>0</sub>	$\overline{Q_0}$

[Texas Instruments 74LS74 flip-flop datasheet]

Note: A flip-flop saves information (i.e. 1 bit); it does not modify it.
  
# D-type Edge-Triggered Flip-Flop

Generally, the flip-flop changes state on a clock signal “edge”, not the level. The flip-flop takes the value *just before* the clock “edge”.



For 74LS74: minimum  $t_s = 20\text{ ns}$   
 minimum  $t_h = 5\text{ ns}$


FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{PRE}$	$\overline{CLR}$	CLK	D	Q	$\overline{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H <sup>†</sup>	H <sup>†</sup>
H	H	↑	H	H	L
H	H	↓	L	L	H
H	H	L	X	Q <sub>0</sub>	$\overline{Q_0}$

[Texas Instruments 74LS74 flip-flop datasheet]


Note: A flip-flop saves information (i.e. 1 bit); it does not modify it.

# Synchronous Timing (revisited)

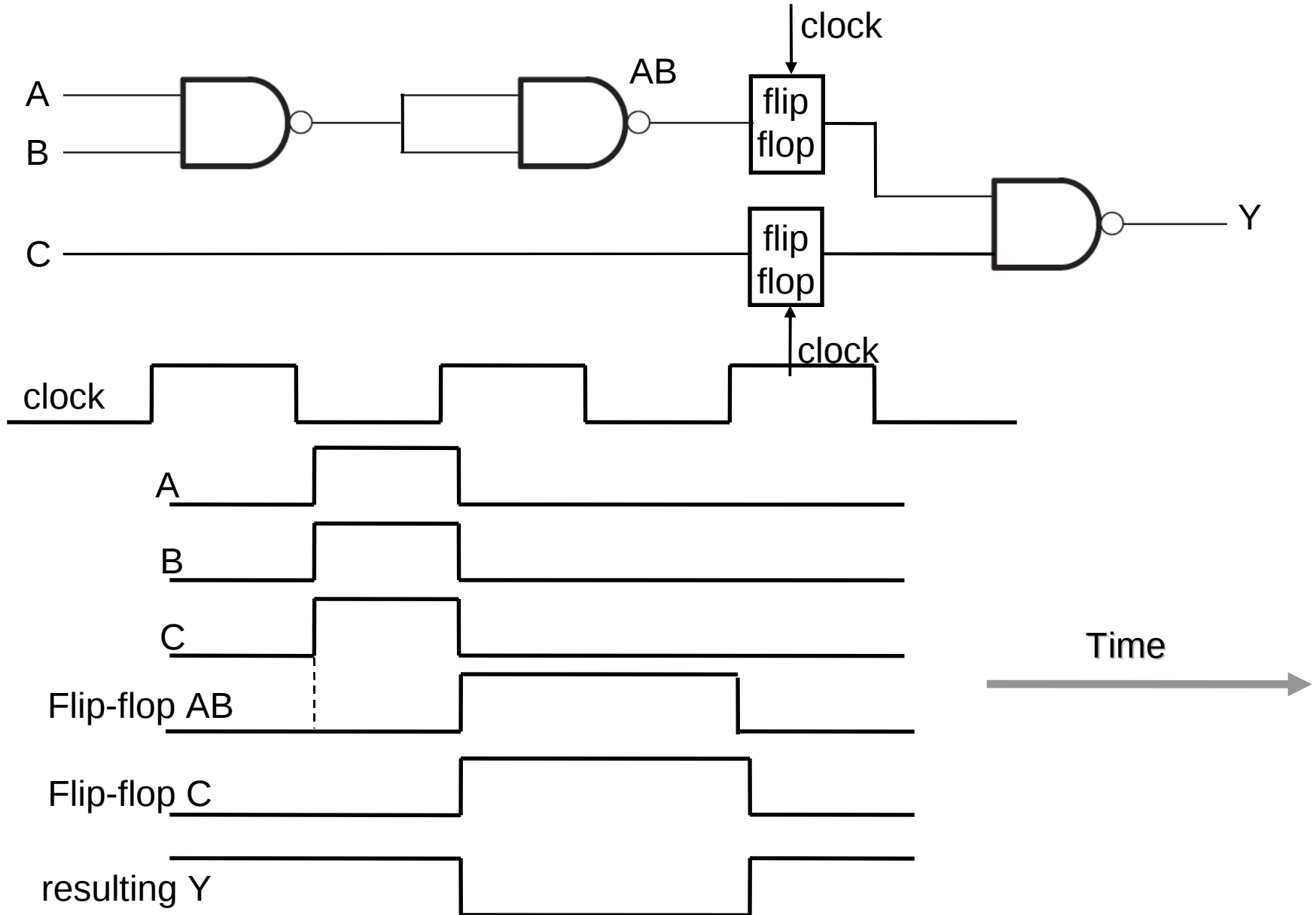

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

*Logic table*

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1


$Q_0$  = value before  
S&R changes

$\bar{R} = 0$  &  $\bar{S} = 0$ :

- $\bar{S} = 0$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .
- $\bar{S} = 0$  & assume  $\bar{Q} = 1 \rightarrow Q = 1$ .
- $\bar{R} = 0$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .
- $\bar{R} = 0$  & assume  $Q = 1 \rightarrow \bar{Q} = 1$ .

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

*Logic table*

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1

$Q_0$  = value before  
S&R changes

$\bar{R} = 0$  &  $\bar{S} = 0$ :

➤  $\bar{S} = 0$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .

$\bar{S} = 0$  & assume  $\bar{Q} = 1 \rightarrow Q = 1$ .

➤  $\bar{R} = 0$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .

$\bar{R} = 0$  & assume  $Q = 1 \rightarrow \bar{Q} = 1$ .


consistent

$\bar{R}=0$  &  $\bar{S}=0 \rightarrow Q=1$  &  $\bar{Q}=1$



# How does a flip-flop work?

Basic flip-flop: the SR latch

 

*Logic table*

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1

$Q_0$  = value before  
S&R changes

**$\bar{R} = 0$  &  $\bar{S} = 1$ :**

➤  $\bar{S} = 1$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .


$\bar{S} = 1$  & assume  $\bar{Q} = 1 \rightarrow Q = 0$ .

➤  $\bar{R} = 0$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .

$\bar{R} = 0$  & assume  $Q = 1 \rightarrow \bar{Q} = 1$ .

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1

$Q_0$  = value before  
S&R changes

$\bar{R} = 0$  &  $\bar{S} = 1$ :

➤  $\bar{S} = 1$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .

$\bar{S} = 1$  & assume  $\bar{Q} = 1 \rightarrow Q = 0$ .

➤  $\bar{R} = 0$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .

$\bar{R} = 0$  & assume  $Q = 1 \rightarrow \bar{Q} = 1$ .


consistent



$\bar{R}=0$  &  $\bar{S}=1 \rightarrow Q=0$  &  $\bar{Q}=1$

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

*Logic table*

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1


$Q_0$  = value before  
S&R changes

$\bar{R} = 1$  &  $\bar{S} = 0$ :

→ The opposite of  $\bar{R} = 0$  &  $\bar{S} = 1$  by symmetry.

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1

$Q_0$  = value before  
S&R changes

$\bar{R} = 1$  &  $\bar{S} = 1$ :

➤  $\bar{S} = 1$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .


$\bar{S} = 1$  & assume  $\bar{Q} = 1 \rightarrow Q = 0$ .

➤  $\bar{R} = 1$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .

$\bar{R} = 1$  & assume  $Q = 1 \rightarrow \bar{Q} = 0$ .

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1

$Q_0$  = value before  
S&R changes

$\bar{R} = 1$  &  $\bar{S} = 1$ :

➤  $\bar{S} = 1$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .

consistent

$\bar{R}=1$  &  $\bar{S}=1 \rightarrow Q=1$  &  $\bar{Q}=0$

$\bar{S} = 1$  & assume  $\bar{Q} = 1 \rightarrow Q = 0$ .

➤  $\bar{R} = 1$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .


consistent

$\bar{R}=1$  &  $\bar{S}=1 \rightarrow Q=0$  &  $\bar{Q}=1$

$\bar{R} = 1$  & assume  $Q = 1 \rightarrow \bar{Q} = 0$ .

# How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
1	1	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
0	0	1	1

$Q_0$  = value before  
S&R changes

$\bar{R} = 1$  &  $\bar{S} = 1$ :

➤  $\bar{S} = 1$  & assume  $\bar{Q} = 0 \rightarrow Q = 1$ .

consistent →

$\bar{R}=1$  &  $\bar{S}=1 \rightarrow Q=1$  &  $\bar{Q}=0$

$\bar{S} = 1$  & assume  $\bar{Q} = 1 \rightarrow Q = 0$ .

consistent →

$\bar{R}=1$  &  $\bar{S}=1 \rightarrow Q=0$  &  $\bar{Q}=1$

➤  $\bar{R} = 1$  & assume  $Q = 0 \rightarrow \bar{Q} = 1$ .

$\bar{R} = 1$  & assume  $Q = 1 \rightarrow \bar{Q} = 0$ .

**Two settings are possible**




**→ i.e. flip-flop keeps its state.**

# SR Latch Switch Debouncer


SR latch flip-flops are not used much for memory, but they are used for debouncing switches.
   
## Switch Bounce:

When a switch is toggled it will not go smoothly from HIGH to LOW, or vice versa.



# Clocked D-type Latch

 

*Logic table*


$D$	$C$	$Q$	$\bar{Q}$
$X$	0	$Q_0$	$\bar{Q}_0$
1	1	1	0
0	1	0	1

## Clock Circuit Analysis:

- $C = 1 \ \& \ D = 1 \rightarrow \bar{S} = 0 \ \& \ \bar{R} = 1.$   
 $C = 1 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 0.$
- $C = 0 \ \& \ D = 1 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$   
 $C = 0 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$



# Clocked D-type Latch

 

*Logic table*

$D$	$C$	$Q$	$\bar{Q}$
$X$	$0$	$Q_0$	$\bar{Q}_0$
$1$	$1$	$1$	$0$
$0$	$1$	$0$	$1$

## Clock Circuit Analysis:

- $C = 1 \ \& \ D = 1 \rightarrow \bar{S} = 0 \ \& \ \bar{R} = 1.$
- $C = 1 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 0.$




**Clock HIGH: D sets the flip-flop state**

- $C = 0 \ \& \ D = 1 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$
- $C = 0 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$



**Clock LOW: flip-flop state is locked**

# Clocked D-type Latch

 

Logic table

$D$	$C$	$Q$	$\bar{Q}$
$X$	0	$Q_0$	$\bar{Q}_0$
1	1	1	0
0	1	0	1

## Clock Circuit Analysis:

➤  $C = 1 \ \& \ D = 1 \ \rightarrow \ \bar{S} = 0 \ \& \ \bar{R} = 1.$   
 $C = 1 \ \& \ D = 0 \ \rightarrow \ S = 1 \ \& \ \bar{R} = 0.$




**Clock HIGH: D sets the flip-flop state**

➤  $C = 0 \ \& \ D = 1 \ \rightarrow \ \bar{S} = 1 \ \& \ \bar{R} = 1.$   
 $C = 0 \ \& \ D = 0 \ \rightarrow \ S = 1 \ \& \ \bar{R} = 1.$




**Clock LOW: flip-flop state is locked**

# Master-Slave D-type Flip-Flop

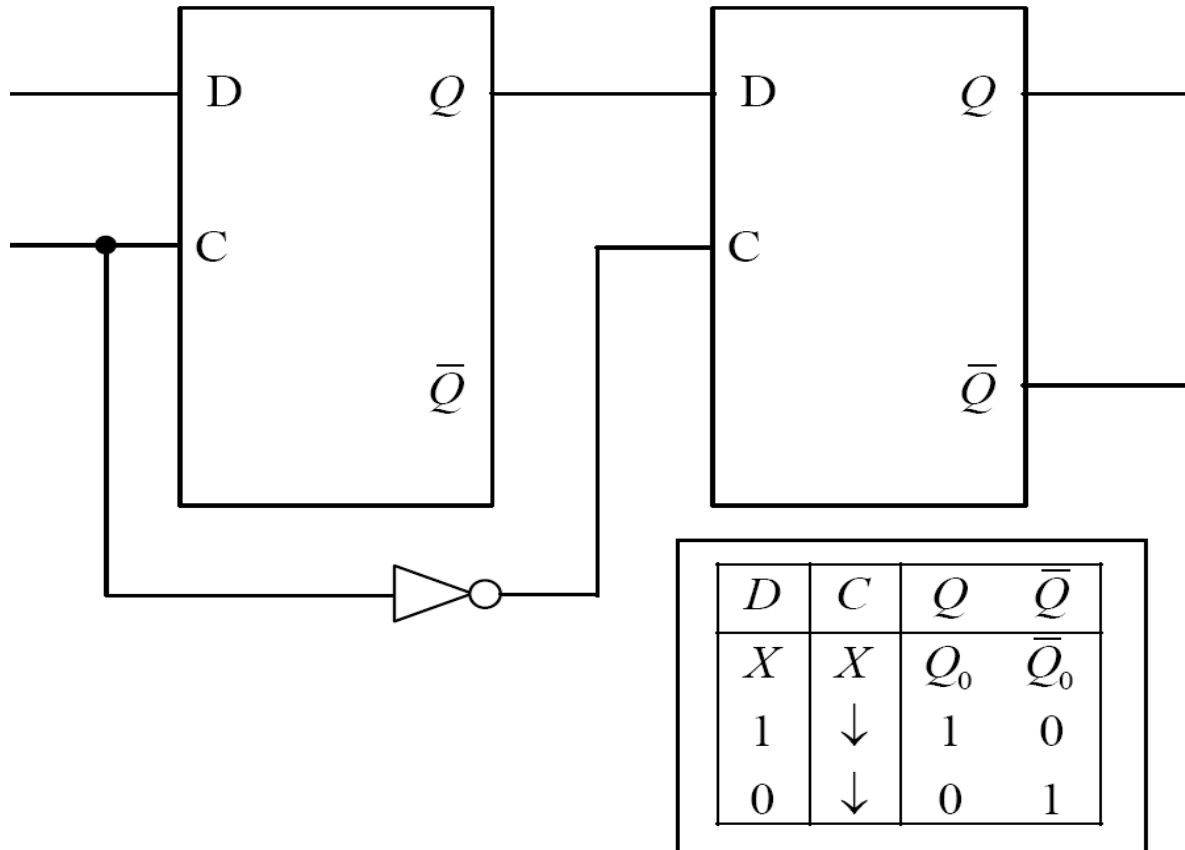

Note: The flip-flop triggers on a the falling edge of the clock.

# 74LS74 D-type edge-triggered flip-flop

 

FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{PRE}$	$\overline{CLR}$	CLK	D	Q	$\overline{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	$H^\dagger$	$H^\dagger$
H	H	$\uparrow$	H	H	L
H	H	$\uparrow$	L	L	H
H	H	L	X	$Q_0$	$\overline{Q}_0$


[Texas Instruments 74LS74 flip-flop datasheet]

Both  $\overline{PRE}$  and  $\overline{CLR}$  behave like  $\overline{S}$  and  $\overline{R}$  inputs, respectively, on the SR latch.

**IMPORTANT:** Both  $\overline{PRE}$  and  $\overline{CLR}$  must be high for normal D-type operation.

**Note:** The flip-flop triggers on the rising edge of the clock.

# 74LS74 D-type edge-triggered flip-flop

 

FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{PRE}$	$\overline{CLR}$	CLK	D	Q	$\overline{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H <sup>†</sup>	H <sup>†</sup>
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q <sub>0</sub>	$\overline{Q_0}$


[Texas Instruments 74LS74 flip-flop datasheet]

Both  $\overline{PRE}$  and  $\overline{CLR}$  behave like  $\overline{S}$  and  $\overline{R}$  inputs, respectively, on the SR latch.

**IMPORTANT:** Both  $\overline{PRE}$  and  $\overline{CLR}$  must be high for normal D-type operation.

**Note:** The flip-flop triggers on the rising edge of the clock.

# JK-type flip-flop

 


Logic table  
for clock falling edge

J	K	$Q_{n+1}$
0	0	$Q_n$
1	0	0
0	1	1
1	1	$\overline{Q_n}$

JK-type flip-flops are used in counters.

# Flip-flops in FPGAs

Architecture of a single Logic Element

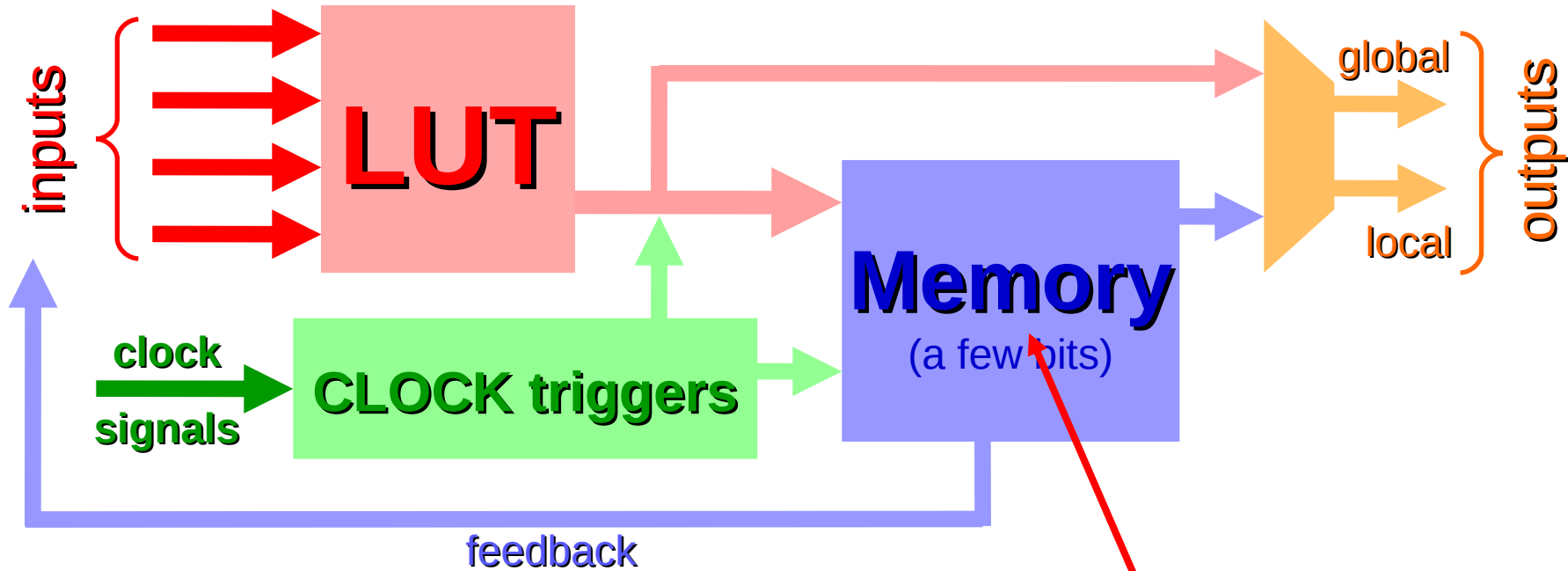


Frequently a D-type Flip-Flop



FPGAs are already set-up for synchronous circuit designs

# Flip-flops in FPGAs

Architecture of a single Logic Element

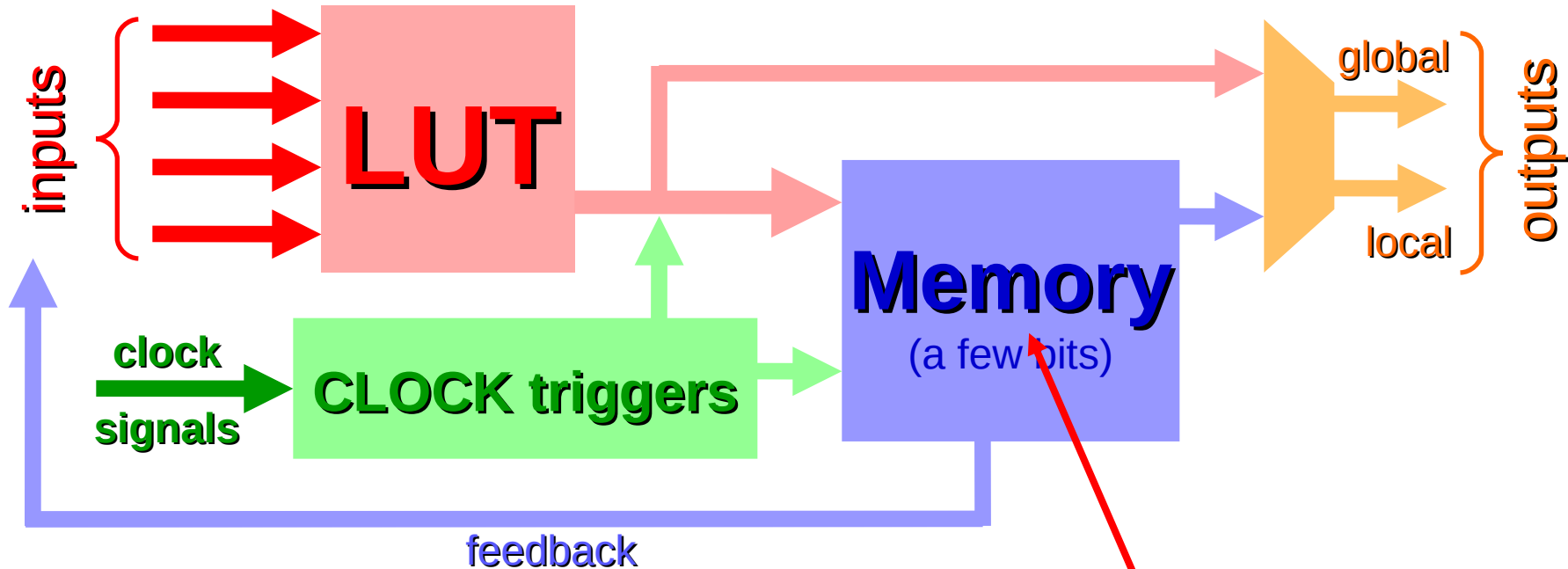

Frequently a D-type Flip-Flop



FPGAs are already set-up for synchronous circuit designs



# Synchronous programming in Verilog (I)

```
1  module adder_always(clock, input1, input2, result);
2      input [3:0] input1;           // 4-bit input, first number
3      input [3:0] input2;           // 4-bit input, second number
4
5      input clock;                  // 1-bit clock input
6
7      output reg [4:0] result;      // 5-bit output register
8
9      always@(posedge clock)        // performs this section on the positive clock edge
10     begin
11         result = input1 + input2;  // Standard 4-bit addition
12     end
13
14 endmodule
15
```

# Synchronous programming in Verilog (I)

```
1 module adder_always(clock, input1, input2, result);
2     input [3:0] input1;           // 4-bit input, first number
3     input [3:0] input2;           // 4-bit input, second number
4
5     input clock;                  // 1-bit clock input
6
7     output reg [4:0] result;      // 5-bit output register
8
9     always@(posedge clock)        // performs this section on the positive clock edge
10    begin
11        result = input1 + input2; // Standard 4-bit addition
12    end
13
14 endmodule
15
```

Clock  
variable

output register  
(i.e. flip-flop memory)

# Synchronous programming in Verilog (I)

```
1  module adder_always(clock, input1, input2, result);
2      input [3:0] input1;           // 4-bit input, first number
3      input [3:0] input2;           // 4-bit input, second number
4
5      input clock;                  // 1-bit clock input
6
7      output reg [4:0] result;      // 5-bit output register
8
9      always@(posedge clock)        // performs this section on the positive clock edge
10     begin
11         result = input1 + input2; // Standard 4-bit addition
12     end
13
14 endmodule
15
```

Clock variable

output register (i.e. flip-flop memory)


**Read as “always at the positive clock edge do the following ...”**

“always” is the core command for synchronous programming, it should be used as frequently as possible.

“assign” should be used as little as possible. It is only useful for DC-type signals (signals that don’t change).

# Synchronous programming in Verilog (II)

*Quartus II circuit simulation*

 

# Synchronous programming in Verilog (II)

*Quartus II circuit simulation*


Clock  
Line



No more glitches


# How did the FPGA implement the circuit?

Tools > Netlists > Technology Map Viewer

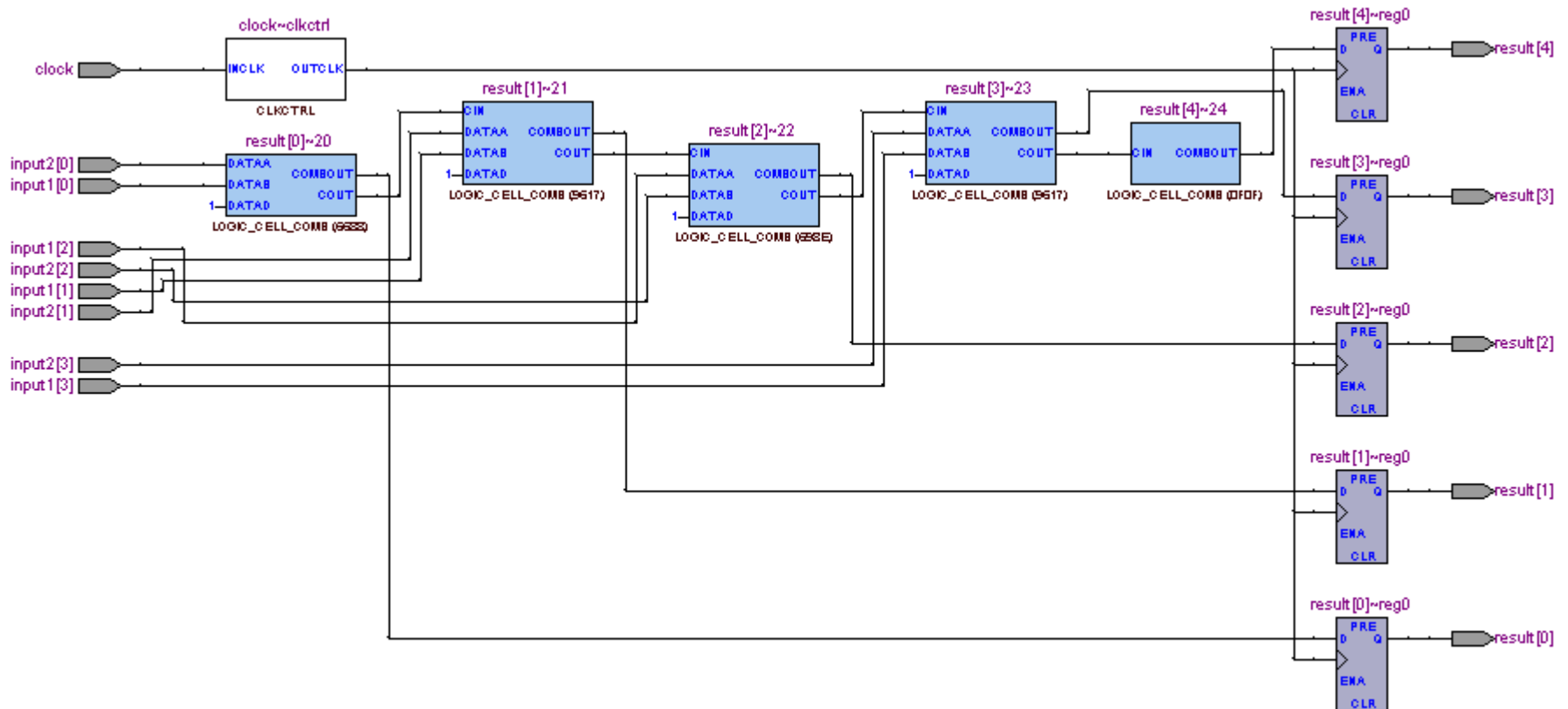

# How did the FPGA implement the circuit?

Tools > Netlists > Technology Map Viewer

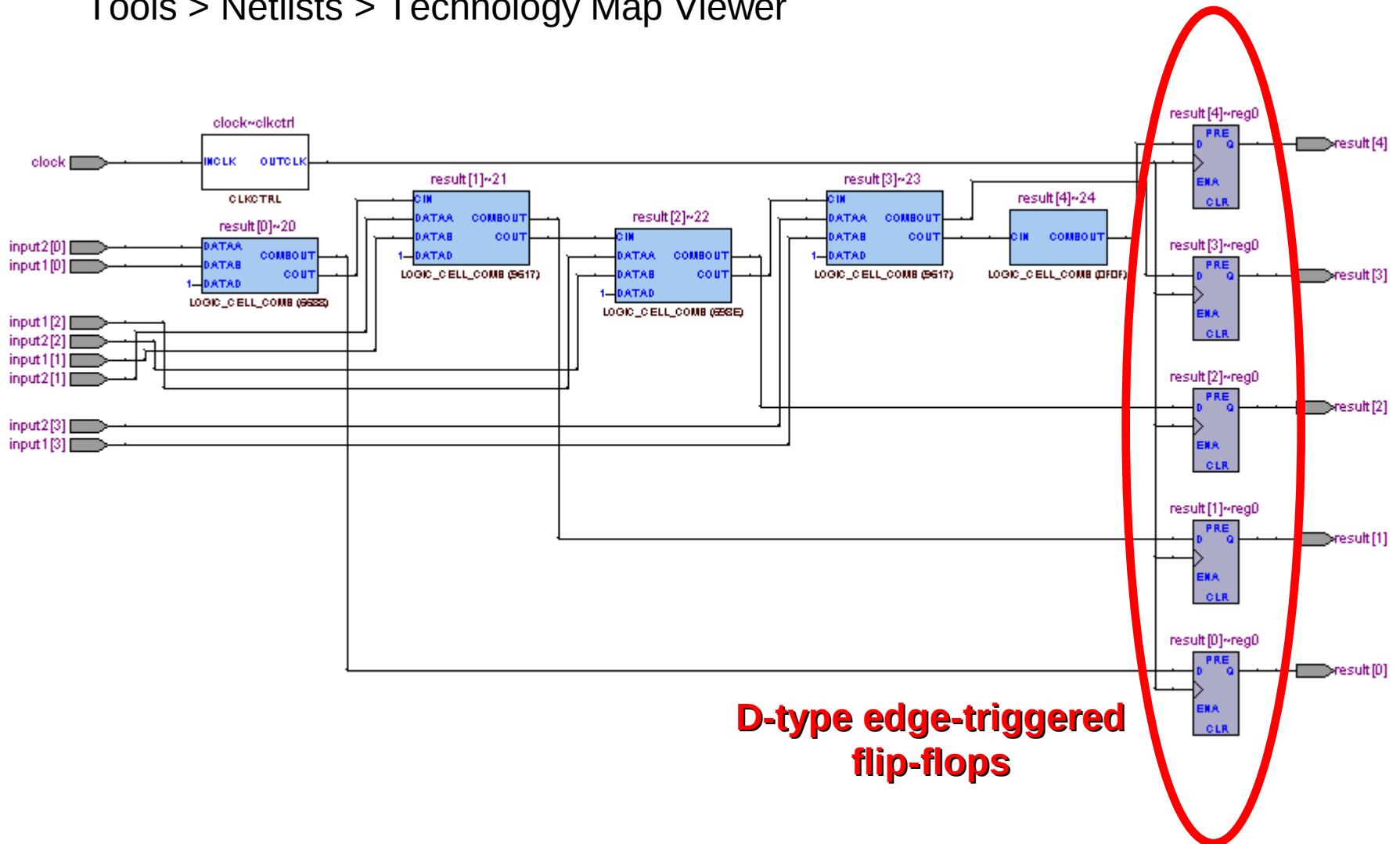

**Always use  
“always”**

– A. Stummer, U. of Toronto.



# Parallel programming in Verilog

- The “always” structure is used for exploiting the parallel processing features of the FPGA.
- Parallel processing must almost always be synchronous if several processes exchange data.

*Parallel and Sequential processing examples:*

## Sequential

```
always@ (negedge clock)  
begin  
a = b;  
c = a;  
end
```

## Parallel

```
always@ (negedge clock)  
begin  
a <= b;  
c <= a;  
end
```

# Parallel programming in Verilog

- The “always” structure is used for exploiting the parallel processing features of the FPGA.
- Parallel processing must almost always be synchronous if several processes exchange data.

*Parallel and Sequential processing examples:*

```
Sequential  
always@ (negedge clock)  
begin  
a = b;  
c = a;  
end
```



```
Parallel  
always@ (negedge clock)  
begin  
a <= b;  
c <= a;  
end
```

*executed simultaneously*

