

DSP Project

Reminder:

Project proposals are due on Friday, October 19th by 5pm.


Budget: \$150/team.

Registers

Registers are a general type of memory

A Parallel In Parallel Out (PIPO) is very fast since each bit is stored or retrieved independently..

 PIPO registers require a large number of input/output lines for storing large binary numbers.




Registers

Shift Registers store serial information using a clock signal

Single bits of data (0 or 1) are presented on the input with each clock cycle. The data can then be 'clocked out' one bit at a time (as shown below) or in parallel.

 Shift registers require only a few input/output lines.




74LS164

- The 74LS164 is a 8 bit parallel out Serial shift Register
- The parallel output bits are labeled Q_{a-h}
- Clocking of data occurs on the low to high level transition
- A and B are serial inputs. A&B high sets data on clock \uparrow
- Clear is asynchronous.


FUNCTION TABLE

| INPUTS | | | | OUTPUTS | | | |
|---------------------------|------------|---|---|----------|-----------|----------|--|
| $\overline{\text{CLEAR}}$ | CLOCK | A | B | Q_A | Q_B ... | Q_H | |
| L | X | X | X | L | L | L | |
| H | L | X | X | Q_{A0} | Q_{B0} | Q_{H0} | |
| H | \uparrow | H | H | H | Q_{An} | Q_{Gn} | |
| H | \uparrow | L | X | L | Q_{An} | Q_{Gn} | |
| H | \uparrow | X | L | L | Q_{An} | Q_{Gn} | |

 

74LS164 Timing

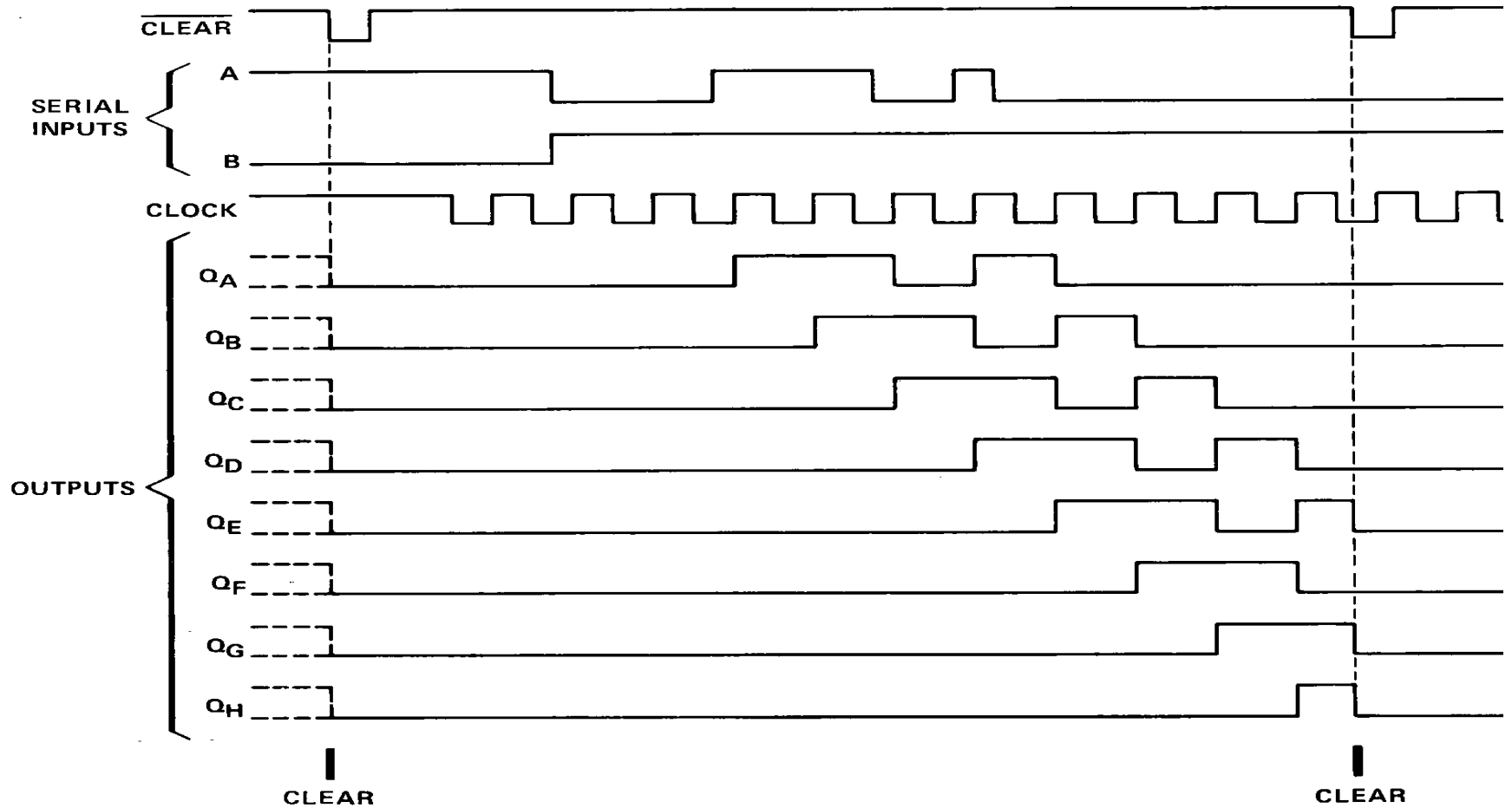typical clear, shift, and clear sequences



Multiplexers

What's a multiplexer ?

A multiplexer is a generalized multi-input and multi-output gate. It will produce a specific multiple line output for each specific multiple line input.

Example: 3-line input and 4-line output (i.e. 3-to-4 multiplexer).

| A | B | C | 1 | 2 | 3 | 4 |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

N.B. Multiplexers can be very useful for converting a binary number to a HEX display code.

Multiplexers with FPGAs (Table)

You could build a multiplexer out of logic gates ... or you could let the Verilog compiler figure it out.

N-to-1 multiplexer:

`mux_primitive.v`

```
1  primitive mux_primitive(out1,A,B,C);    // 3-to-1 multiplexer
2      input  A, B, C;                    // 3 input wires
3      output out1;                       // 1 output wire
4
5  table                                  // table defines the output based on the 3 inputs
6      // A B C out1
7      0 0 0 : 0 ;
8      0 0 1 : 0 ;
9      0 1 0 : 0 ;
10     1 0 0 : 1 ;
11     1 1 0 : 1 ;
12     0 1 1 : 0 ;
13     1 0 1 : 1 ;
14     1 1 1 : 0 ;
15     endtable
16
17 endprimitive
18
```

Multiplexers with FPGAs (if)

An always block with “if” statements can be used for an N-to-M multiplexer:

mux_always_if.v

```
1 module mux_always_if(input_3bit, output_4bit); // 3-to-4 multiplexer
2     input [2:0] input_3bit; // 3 input lines (bits)
3     output reg [3:0] output_4bit; // 4-bit output register
4
5     // always block with "if" statement for each input case
6     always
7     begin
8         if(input_3bit == 3'b000) output_4bit <= 4'b0001;
9         if(input_3bit == 3'b001) output_4bit <= 4'b0010;
10        if(input_3bit == 3'b010) output_4bit <= 4'b0100;
11        if(input_3bit == 3'b100) output_4bit <= 4'b1000;
12        if(input_3bit == 3'b110) output_4bit <= 4'b1100;
13        if(input_3bit == 3'b011) output_4bit <= 4'b0110;
14        if(input_3bit == 3'b101) output_4bit <= 4'b1010;
15        if(input_3bit == 3'b111) output_4bit <= 4'b0001;
16    end
17 endmodule
18
```

An always block guarantees that you won't have any signal races or glitches.

Multiplexers with FPGAs (case)

An always block with “case” constructs can be used for an N-to-M multiplexer:

```
1  module mux_always_case(input_3bit,output_4bit);    // 3-to-4 multiplexer
2      input  [2:0] input_3bit;                       // 3-bit input
3      output reg [3:0] output_4bit;                 // 4-bit output
4
5      always    // always block with "case" construct
6      begin
7          case(input_3bit)
8              3'b000: output_4bit <= 4'b0001;
9              3'b001: output_4bit <= 4'b0010;
10             3'b010: output_4bit <= 4'b0100;
11             3'b100: output_4bit <= 4'b1000;
12             3'b110: output_4bit <= 4'b1100;
13             3'b011: output_4bit <= 4'b0110;
14             3'b101: output_4bit <= 4'b1010;
15             3'b111: output_4bit <= 4'b0001;
16         endcase
17     end
18
19 endmodule
```

Multiple Modules

multiple_modules.v

```
1 module multiple_modules(input_clock, output_FourBits); // top-level module
2     input input_clock; // input wire
3     output [3:0] output_FourBits; // output wires
4
5     wire [2:0] counter_output; // output wires of counter
6     wire [2:0] mux_input; // input wires of multiplexer
7
8     assign mux_input = counter_output; // connect the counter output and multiplexer input wires
9
10    counter counter_result(input_clock, counter_output); // call the "counter" module
11 // with instance "counter_result"
12
13    mux_always_case mux_output(mux_input, output_FourBits); // call the "mux_always_case" module
14 // with instance " mux_output"
15
16 endmodule
17
```

counter.v

```
1 module counter(input_clk, output_3bit);
2     input input_clk;
3     output reg [2:0] output_3bit;
4
5     always@(posedge input_clk)
6     begin
7         output_3bit <= output_3bit + 3'b001;
8     end
9
10 endmodule
11
```

mux_always_case.v*

```
1 module mux_always_case(input_3bit,output_4bit); // 3-
2     input [2:0] input_3bit; // 3-bit input
3     output reg [3:0] output_4bit; // 4-bit output
4
5     always // always block with "case" construct
6     begin
7         case(input_3bit)
8             3'b000: output_4bit <= 4'b0001;
9             3'b001: output_4bit <= 4'b0010;
10            3'b010: output_4bit <= 4'b0100;
11            3'b100: output_4bit <= 4'b1000;
12            3'b110: output_4bit <= 4'b1100;
13            3'b011: output_4bit <= 4'b0110;
14            3'b101: output_4bit <= 4'b1010;
15            3'b111: output_4bit <= 4'b0001;
16        endcase
17    end
18
19 endmodule
20
```

Multiple Modules

multiple_modules.v

```
1 module multiple_modules(input_clock, output_FourBits); // top-level module
2     input input_clock; // input wire
3     output [3:0] output_FourBits; // output wires
4
5     wire [2:0] counter_output; // output wires of counter
6     wire [2:0] mux_input; // input wires of multiplexer
7
8     assign mux_input = counter_output; // connect the counter output and multiplexer input wires
9
10    counter counter_result(input_clock, counter_output); // call the "counter" module
11                                     // with instance "counter_result"
12
13    mux_always_case mux_output(mux_input, output_FourBits); // call the "mux_always_case" module
14                                                         // with instance " mux_output"
15
16 endmodule
17
```

Wires for connecting the 2 lower level modules

module name instance name

counter.v

```
1 module counter(input_clk, output_3bit);
2     input input_clk;
3     output reg [2:0] output_3bit;
4
5     always@(posedge input_clk)
6     begin
7         output_3bit <= output_3bit + 3'b001;
8     end
9
10 endmodule
11
```

mux_always_case.v*

```
1 module mux_always_case(input_3bit,output_4bit); // 3-
2     input [2:0] input_3bit; // 3-bit input
3     output reg [3:0] output_4bit; // 4-bit output
4
5     always // always block with "case" construct
6     begin
7         case(input_3bit)
8             3'b000: output_4bit <= 4'b0001;
9             3'b001: output_4bit <= 4'b0010;
10            3'b010: output_4bit <= 4'b0100;
11            3'b100: output_4bit <= 4'b1000;
12            3'b110: output_4bit <= 4'b1100;
13            3'b011: output_4bit <= 4'b0110;
14            3'b101: output_4bit <= 4'b1010;
15            3'b111: output_4bit <= 4'b0001;
16        endcase
17    end
18
19 endmodule
20
```

Multiple Modules

multiple_modules.v

```
1 module multiple_modules(input_clock, output_FourBits); // top-level module
2     input input_clock; // input wire
3     output [3:0] output_FourBits; // output wires
4
5     wire [2:0] counter_output; // output wires of counter
6     wire [2:0] mux_input; // input wires of multiplexer
7
8     assign mux_input = counter_output; // connect the counter output and multiplexer input wires
9
10    counter counter_result(input_clock, counter_output); // call the "counter" module
11    // with instance "counter_result"
12    module name instance name
13    mux_always_case mux_output(mux_input, output_FourBits); // call the "mux_always_case" module
14    // with instance " mux_output"
15
16 endmodule
17
```

Warning: DO NOT make these registers !!!

mux_always_case.v*

```
1 module mux_always_case(input_3bit,output_4bit); // 3-
2     input [2:0] input_3bit; // 3-bit input
3     output reg [3:0] output_4bit; // 4-bit output
4
5     always // always block with "case" construct
6     begin
7         case(input_3bit)
8             3'b000: output_4bit <= 4'b0001;
9             3'b001: output_4bit <= 4'b0010;
10            3'b010: output_4bit <= 4'b0100;
11            3'b100: output_4bit <= 4'b1000;
12            3'b110: output_4bit <= 4'b1100;
13            3'b011: output_4bit <= 4'b0110;
14            3'b101: output_4bit <= 4'b1010;
15            3'b111: output_4bit <= 4'b0001;
16        endcase
17    end
18
19 endmodule
20
```

counter.v

```
1 module counter(input_clk, output_3bit);
2     input input_clk;
3     output reg [2:0] output_3bit;
4
5     always@(posedge input_clk)
6     begin
7         output_3bit <= output_3bit + 3'b001;
8     end
9
10 endmodule
11
```