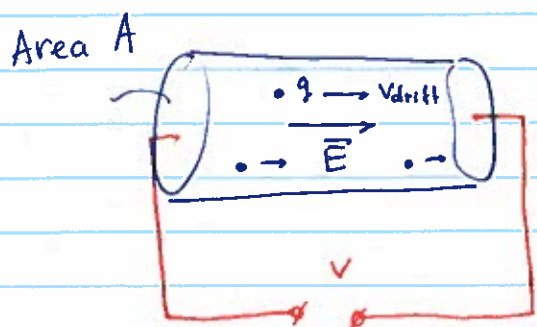


## Electric current $I$ (measured in Ampere)

Electric current is the amount of positive charge passing through a wire in a given time

(yes, the current flows officially in the opposite direction of moving electrons)



$$V = E \cdot l$$

$$I = \frac{dQ}{dt} = q \cdot A \cdot n_q \cdot \langle v_q \rangle$$

$q$  - unit charge "positive electron"

$n_q$  - density of free carriers

$\langle v_q \rangle = v_{\text{drift}}$  - common velocity of charges in electric field

$$\langle v_q \rangle \propto E$$

$$I = A \cdot \sigma \cdot E$$

$\sigma$  - conductivity, depends on the material

$$\rho = \frac{1}{\sigma} \text{ resistivity}$$

$$V = \frac{I}{A \cdot \sigma} \cdot l = \frac{l}{\sigma \cdot A} \cdot I = \boxed{\frac{l \rho}{A}} \cdot I$$

$R$  - resistance

$$V = R \cdot I \quad - \text{Ohm's law} \quad R = \frac{V}{I} \quad [R] = \frac{\text{Ohm}}{\Omega}$$

For a uniform wire / piece of conductor

$$R = \rho \frac{l}{A}$$

$R \uparrow$  if area is smaller

$R \uparrow$  if the ~~met~~ wire is longer

Power dissipated at a resistor

$$P = \frac{dU}{dt} = \frac{V dQ}{dt} = V \cdot I = \frac{V^2}{R} = I^2 R$$

Thick wires are better to use for high current, since they loose less energy (and are less likely to melt)

# Electric circuits

DC (direct current)  
constant current

AC (alternating current)  
[we'll get ~~to~~ to them soon]

## Common elements

— wires —  $\frac{1}{2}$  when assumed ideal (default), connect points of equal potential  $\Delta V_{\text{wire}} = 0$

$R$  resistors  $V_A - V_B = \Delta V_R = I \cdot R$




- Batteries: sources of constant potential difference

Ideal battery is a source of electromotive force (emf):  $\mathcal{E}$  - max voltage a battery can produce.

Real batteries have some internal resistance, so their actual output voltage can be less than their emf - we'll discuss it later.

Notation:


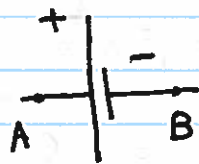


$$V_A - V_B = \mathcal{E}$$

My favorite mnemonics


| → break in half | → + combine

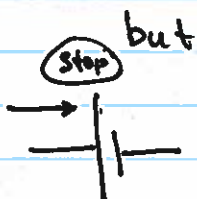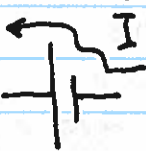In what direction battery would push the current?  
easy to get over, taking the steps



hard to get through, with high fence

Simplest circuit

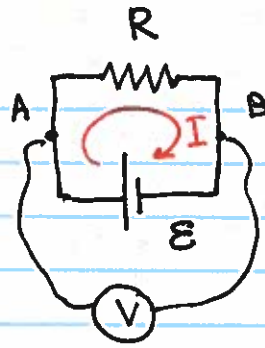

$$V_A - V_B = \epsilon$$


$$V_A - IR = V_B$$

$$V_A - V_B = IR$$

$$\epsilon = IR$$

$$I = \epsilon/R$$

Series connection

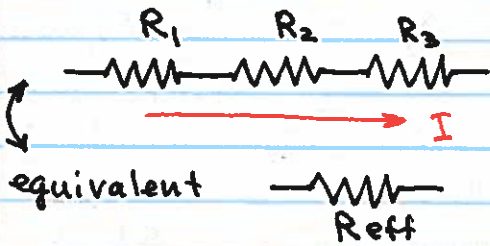

equivalent

Total voltage drop  
Effective resistance


Same current flows through each resistor for connection in series

(since all the charges must get from one end to another)

$$IR_1 + IR_2 + IR_3 = V_{tot}$$

$$R_{eff} = \frac{V_{tot}}{I} = R_1 + R_2 + R_3$$


Parallel connection

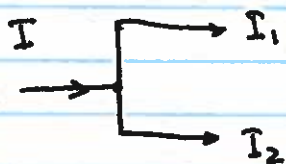

$$I = I_1 + I_2$$

original flow of charges splits in two (or more) streams, but their total current stays the same

Parallel resistor connection

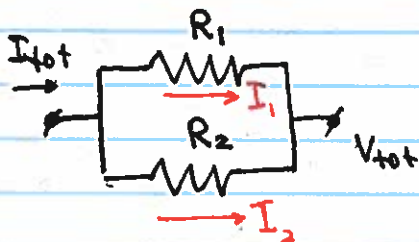

$$I_{tot} = I_1 + I_2$$


$$V_1 = V_2 = V_{tot}$$

$$V_1 = I_1 R_1 \quad V_2 = I_2 R_2$$

↓

$$I_1 = \frac{V_1}{R_1} = \frac{V_{tot}}{R_1} \quad I_2 = \frac{V_2}{R_2} = \frac{V_{tot}}{R_2}$$

equivalent

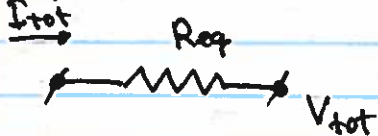

$$I_{tot} = \frac{V_{tot}}{R_{eq}} = \frac{V_{tot}}{R_1} + \frac{V_{tot}}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$