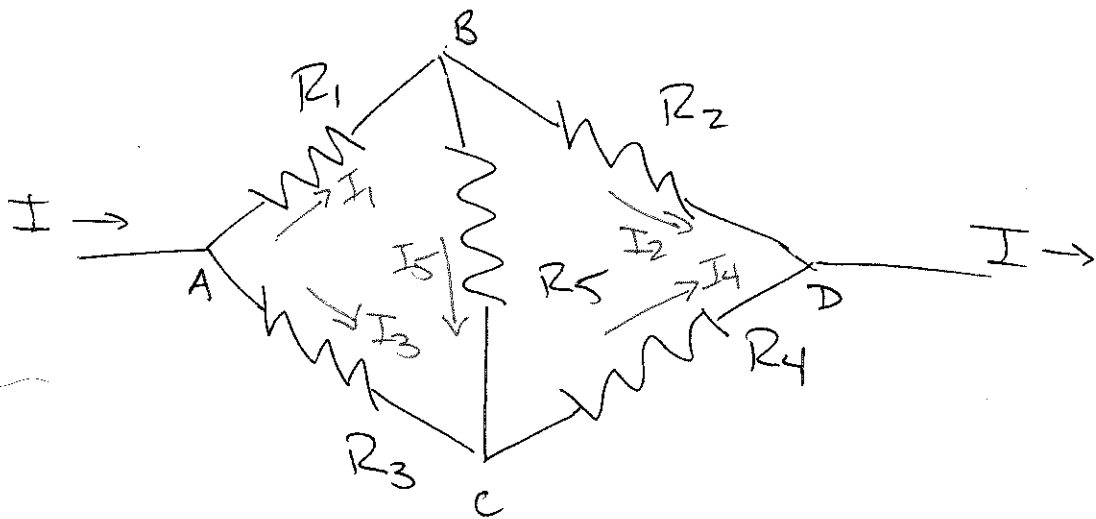


2-1



Junctions

$$A: \quad I = I_1 + I_3$$

$$B: \quad I_1 = I_2 + I_5$$

$$C: \quad I_4 = I_3 + I_5$$

$$D: \quad I = I_2 + I_4$$

Not independent.

only need,

$$I_1 = I_2 + I_5$$

$$I_4 = I_3 + I_5$$

Loops

$$ABCA: \quad -I_1 R_1 - I_5 R_3 + I_3 R_3 = 0$$

$$BDDB: \quad -I_2 R_2 + I_4 R_4 + I_5 R_5 = 0$$

$$\text{want } R_{eq} = \frac{\Delta V}{I} = \frac{\Delta V_{AB} + \Delta V_{BD}}{I}$$

$$= \frac{I_1 R_1 + I_2 R_2}{I_1 + I_3}$$

(from junction A)

5 unknown currents, 4 Equations. 1 is arbitrary
Solve by hand or via Matrix. (under constrained problem)

Equations:

$$\textcircled{1} \quad I_1 + I_2 + I_5 = 0$$

$$\textcircled{2} \quad I_3 - I_4 + I_5 = 0$$

$$\textcircled{3} \quad I_1 R_1 - I_3 R_3 + I_5 R_3 = 0$$

$$\textcircled{4} \quad -I_2 R_2 + I_4 R_4 + I_5 R_5 = 0$$

forms Matrix,

$$\begin{pmatrix} 1 & -1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & -1 \\ R_1 & 0 & -R_3 & 0 & R_3 \\ 0 & -R_2 & 0 & R_4 & R_5 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

2-1

restart,

with(LinearAlgebra) :

$m := \text{Matrix}([[1, -1, 0, 0, -1], [0, 0, -1, 1, -1], [R_1, 0, -R_3, 0, R_5], [0, -R_2, 0, R_4, R_5]])$;

$b := \text{Matrix}([[0], [0], [0], [0]])$:

$$\begin{bmatrix} 1 & -1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & -1 \\ R_1 & 0 & -R_3 & 0 & R_5 \\ 0 & -R_2 & 0 & R_4 & R_5 \end{bmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad (1)$$

LinearSolve(m, b, free = k)

$$\begin{aligned} I_1 &= \frac{k_{1,1} (R_3 R_5 + R_3 R_4 + R_5 R_4 + R_2 R_3)}{R_4 R_1 - R_2 R_3} \\ I_2 &= \frac{k_{1,1} (R_3 R_5 + R_3 R_4 + R_5 R_4 + R_4 R_1)}{R_4 R_1 - R_2 R_3} \\ I_3 &= \frac{k_{1,1} (R_5 R_1 + R_2 R_5 + R_2 R_1 + R_4 R_1)}{R_4 R_1 - R_2 R_3} \\ I_4 &= \frac{(R_5 R_1 + R_2 R_5 + R_2 R_1 + R_2 R_3) k_{1,1}}{R_4 R_1 - R_2 R_3} \\ I_5 &= k_{1,1} \text{ (arbitrary)} \end{aligned} \quad (2)$$

$$R_{eq} := \text{simplify} \left(\frac{\left(-\frac{k_{1,1} (R_3 R_5 + R_3 R_4 + R_5 R_4 + R_2 R_3)}{R_4 R_1 - R_2 R_3} \cdot R_1 + -\frac{k_{1,1} (R_3 R_5 + R_3 R_4 + R_5 R_4 + R_4 R_1)}{R_4 R_1 - R_2 R_3} \cdot R_2 \right)}{-\frac{k_{1,1} (R_3 R_5 + R_3 R_4 + R_5 R_4 + R_2 R_3)}{R_4 R_1 - R_2 R_3} + -\frac{k_{1,1} (R_5 R_1 + R_2 R_5 + R_2 R_1 + R_4 R_1)}{R_4 R_1 - R_2 R_3}} \right);$$

$$\frac{R_3 R_5 R_1 + R_3 R_4 R_1 + R_5 R_4 R_1 + R_3 R_2 R_1 + R_3 R_2 R_5 + R_2 R_3 R_4 + R_2 R_5 R_4 + R_2 R_4 R_1}{R_3 R_5 + R_3 R_4 + R_5 R_4 + R_2 R_3 + R_5 R_1 + R_2 R_5 + R_2 R_1 + R_4 R_1} = R_{eq} \quad (3)$$

factor(eval(R_{eq}, R₅=0));

Balanced Bridge check

$$\frac{R_3 R_4 R_1 + R_3 R_2 R_1 + R_2 R_3 R_4 + R_2 R_4 R_1}{(R_2 + R_4) (R_3 + R_1)} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4} \quad (4)$$

$$R_{eq} = \frac{I_1 R_1 + I_2 R_2}{I_1 + I_3}$$