

Full network analysis.

Eugeniy E. Mikhailov

The College of William & Mary



Lecture 02

Notes

Kirchhoff's Current Law

Kirchhoff's Current Law

The algebraic sum of currents entering and exiting a node equals zero

Convention (quite arbitrary): currents going into the nodes are positive, the ones which go out of the node are negative.

Kirchhoff's Voltage Law


The algebraic sum of all voltage changes (aka voltage drops) in a loop equals zero

Notes:

- choose a direction along which you travel a network. If you go over a resistor and current runs the same way then voltage change is negative, otherwise its positive.
- If you go over a voltage source from negative terminal to positive the voltage change is positive, otherwise negative.

Notes

Example

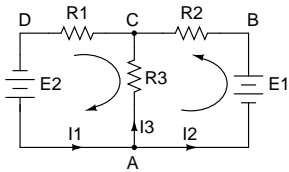

our goal is to find I_1 , I_2 , and I_3

We chose $V_A = 0$

For node A:

$$I_1 - I_2 - I_3 = 0 \quad (1)$$

We need 2 more **independent** equations.

For this we will go over 2 small loops as indicated by arrows.

$$V_{DC} + V_{CA} + V_{AD} = 0 \quad (2)$$

$$V_{AB} + V_{BC} + V_{CA} = 0 \quad (3)$$


Notice:

$$V_{AB} = +E_1, V_{BC} = -R_2 \times I_2, V_{CA} = +R_3 \times I_3,$$

$$V_{DC} = +R_1 \times I_1, V_{AD} = -E_2.$$

Notes

Example (continued)

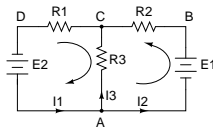

$$I_1 - I_2 - I_3 = 0$$

$$V_{DC} + V_{CA} + V_{AD} = 0$$

$$V_{AB} + V_{BC} + V_{CA} = 0$$

→

$$I_1 - I_2 - I_3 = 0$$

$$R_1 \times I_1 + R_3 \times I_3 - E_2 = 0$$

$$E_1 - R_2 \times I_2 + R_3 \times I_3 = 0$$

Notes

Maple as the math aid

$$\text{solve}((I1 - I2 - I3 = 0, E1 - R2 \cdot I2 + R3 \cdot I3 = 0, R1 \cdot I1 + R3 \cdot I3 - E2 = 0), [I1, I2, I3])$$

$$\left[\left[I1 = \frac{R3 E1 + R3 E2 + R2 E2}{R3 R1 + R1 R2 + R3 R2}, I2 = \frac{R3 E1 + R3 E2 + R1 E1}{R3 R1 + R1 R2 + R3 R2}, I3 = \frac{R1 E1 - R2 E2}{R3 R1 + R1 R2 + R3 R2} \right] \right]$$

(1)

Notes

Maple as the math aid (continued)

$$V_{out} := \frac{V_{in} R_2}{(R1 + R2)} \frac{R_L}{R_L + \frac{R1 R_2}{R1 + R2}}$$


$$\frac{V_{in} R_2 R_L}{(R1 + R2) \left(R_L + \frac{R1 R_2}{R1 + R2} \right)}$$

(1)

$$V_{in} := 10; R1 := 10; R2 := 1;$$

$$\frac{10}{10}$$

(2)

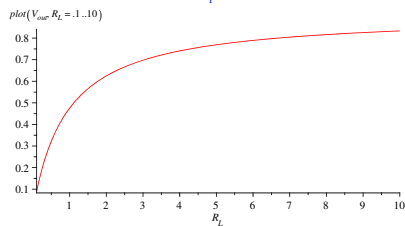


Notes

Thévenin's and Norton's equivalent circuit theorems

Any combination of voltage sources, current sources and resistors with two terminals is electrically equivalent


Thévenin's theorem

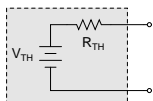to a single voltage source V_{TH} and a single series resistor R_{TH} connected in series.



Norton's theorem

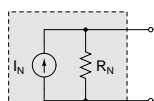to a single current source I_N and a single series resistor R_N connected in parallel.



Note above circuits are equivalent to each other when

$$R_{TH} = R_N \text{ and } I_N = V_{TH} / R_{TH}$$

Notes

Notes
