

# Filters.

Eugeniy E. Mikhailov

The College of William & Mary



Lecture 04

Notes

---

---

---

---

---

---

---

---

## Power dissipation

Recall that power dissipated by element is

$$P = VI$$

where  $V$  and  $I$  are real.

Since we use a substitute

$V \cos(\omega t) \rightarrow V e^{j\omega t}$  and  $I \cos(\omega t) \rightarrow I e^{j\omega t}$ ,

we need to write

$$P = \text{Re}(V)\text{Re}(I)$$

Recall the Ohm's law

$$V = ZI$$

Notes

---

---

---

---

---

---

---

---

## Power dissipation by a reactive element

### Theorem

**Average power dissipated by a reactive element (C or L) is 0**

Lets use as example an inductor.

$$Z_L = i\omega L = e^{i\frac{\pi}{2}}\omega L, I_L = I_p e^{j\omega t}$$

$$V_L = Z_L I_L = e^{i\frac{\pi}{2}}\omega L I_L = \omega L I_p e^{i(\omega t + \frac{\pi}{2})}$$

$$\text{Re}(I_L) = I_p \cos(\omega t), \text{Re}(V_L) = -\omega L I_p \sin(\omega t)$$

Thus average power dissipated by the inductor

$$P = \int_0^T \text{Re}(I_L)\text{Re}(V_L)dt = -\int_0^T I_p \cos(\omega t)\omega L I_p \sin(\omega t)dt$$

$$P = -\omega I_p^2 L \int_0^T \cos(\omega t)\sin(\omega t)dt = \omega I_p^2 L \int_0^T \frac{1}{2} \sin(2\omega t)dt = 0$$

Notes

---

---

---

---

---

---

---

---

## Fourier transform

If function  $f(t)$  goes to zero at  $\pm\infty$  then  $\hat{f}(w)$  exists such as

$$f(t) = \int_{-\infty}^{\infty} \hat{f}(w)e^{j\omega t}d\omega$$

Notes

---

---

---

---

---

---

---

---


# Transfer function

Time domain



$$V_{out}(t) = \int_{-\infty}^t H(t - \tau) V_{in}(\tau) d\tau$$

Frequency domain

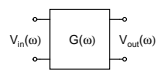

$$V_{out}(\omega) = G(\omega) V_{in}(\omega)$$

Where  $G$  is complex transfer function or gain.


## Definition

$$G(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)} = |G(\omega)| e^{j\phi(\omega)}$$

Often used values of  $G$  in dB

$$dB = 20 \log_{10}(|G(\omega)|)$$

## Simple example: RC low-pass filter

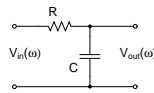

$$G(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)} = \frac{1}{R + \frac{1}{i\omega C}} = \frac{1}{i\omega RC} \frac{1}{1 + \frac{1}{i\omega RC}} = \frac{1}{1 + i\omega RC}$$

defining  $\omega_{3dB} = \frac{1}{RC}$


$$G(\omega) = \frac{1}{1 + i\frac{\omega}{\omega_{3dB}}} = \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_{3dB}^2}}} e^{j\phi}, \phi = \text{atan}\left(-\frac{\omega}{\omega_{3dB}}\right)$$

Note


$$|G(\omega = \omega_{3dB})| = 20 \log_{10}\left(\frac{1}{\sqrt{1+1}}\right) = 20 \log_{10}\left(\frac{1}{\sqrt{2}}\right) = -3dB$$

## RC low-pass filter at $\omega = .1/RC$

Signal vs time

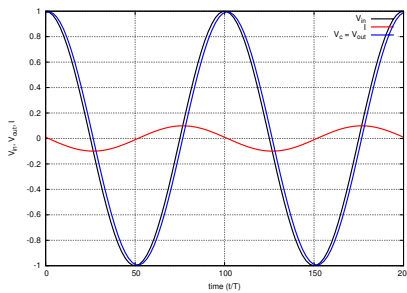


Lissajous plot

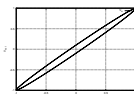

## RC low-pass filter at $\omega = 1/RC$

Signal vs time

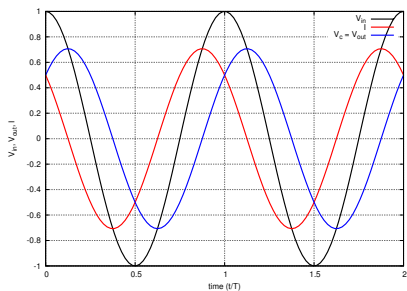

Lissajous plot



Notes

---

---

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---


---

---


---

# RC low-pass filter at $\omega = 10/RC$

Signal vs time

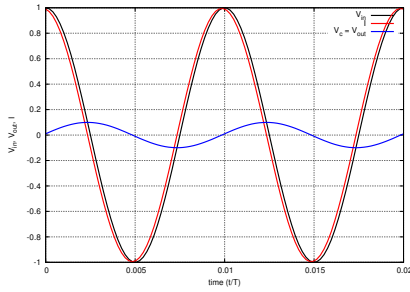

Lissajous plot

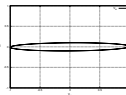

Notes

---

---

---

---

---

---


---

---


## Bode plots

Definition

Bode plot: plots of magnitude and phase of the transfer function, where  $|G|$  is often plotted in dB

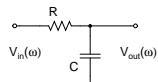
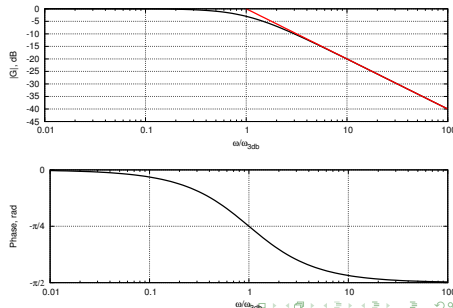
$$G(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{3dB}}}$$



Notes

---

---

---

---



---

---

---

---

## RC high-pass filter

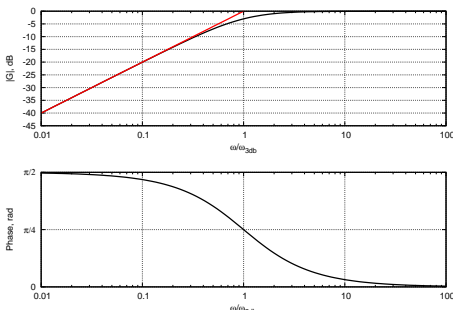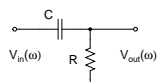

$$G(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\frac{\omega}{\omega_{3dB}}}{1 + j\frac{\omega}{\omega_{3dB}}}$$

with  $\omega_{3dB} = \frac{1}{RC}$

Notes

---

---

---

---

---


---

---


---

## RL filters


RL low-pass filter

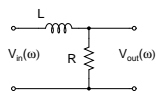

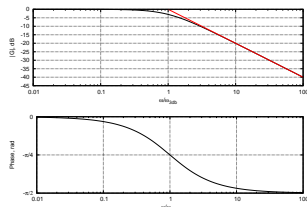
$$G(\omega) = \frac{R}{R + j\omega L}, \omega_{3dB} = \frac{R}{L}$$



RL high-pass filter

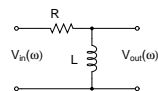
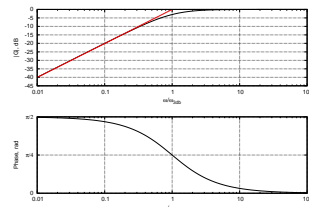
$$G(\omega) = \frac{j\omega L}{R + j\omega L}$$



Notes

---

---

---

---


---

---

---

---

## Filters chain

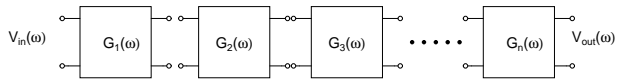

Technically next stage loads the previous and it is quite hard to calculate total transfer function.  
However if we use rule of 10 to avoid overloading the previous filter.  
Every next stage resistor  $R_{i+1} > 10R_i$  we can approximate

$$G_T(\omega) \approx G_1(\omega)G_2(\omega)G_3(\omega) \cdot \dots \cdot G_n(\omega)$$

Notes

---

---

---

---


---

---

---

---


## Example band pass filter

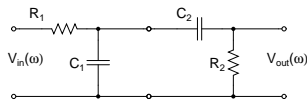

$$G_T(\omega) \approx G_1(\omega)G_2(\omega)$$

$$G_T(\omega) \approx \frac{1}{1 + j\frac{\omega}{\omega_{1,3dB}}} \cdot \frac{j\frac{\omega}{\omega_{2,3dB}}}{1 + j\frac{\omega}{\omega_{2,3dB}}}$$

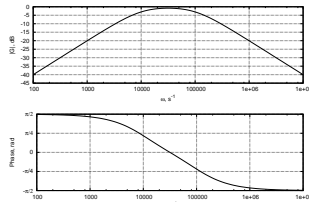For  $R_1 = 1k\Omega$ ,  $R_2 = 100k\Omega$ ,  
 $C_1 = C_2 = .01\mu F$



Notes

---

---

---

---


---

---


---

---

## Notch filter - Band stop filter

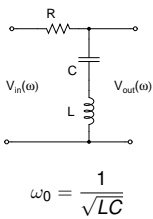

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

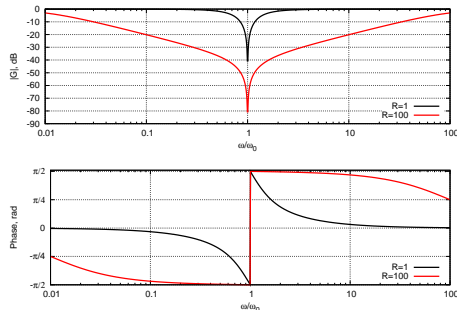

It is impossible to make band stop filter with  $G \approx 1$  with only R,C or R,L elements. R, L, and C combo is required.

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---