

# Diodes.

Eugeniy E. Mikhailov

The College of William & Mary



Lecture 05

Notes

---

---

---

---

---

---

---

---

## Midterm exam

Where: In the lab

When: During the first hour of the lab

Material:

- everything from first 4 weeks of class
- Resistors, capacitors, inductors, and transformers.
- Kirchhoff's laws
- Complex impedances.
- Thévenin's theorem
  - Source impedance and voltage
- Voltage divider in various forms
- Filters

Lab will follow the midterm.

You can skip design exercise preparation prior to the lab. However, at the time of log book submission it must be fully done. Treat it as a home work.

Notes

---

---

---

---


---

---

---

---

## Ideal diode

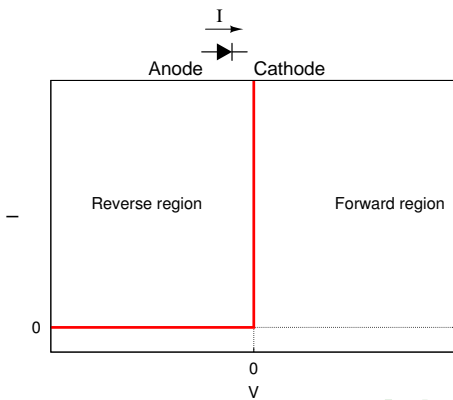

Notes

---

---

---

---

---


---

---

---

## Semiconductors and doping

Pure semiconductor

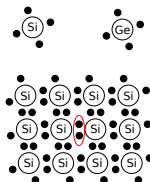

Notes

---

---

---

---


---

---


---

---

# Semiconductors and doping

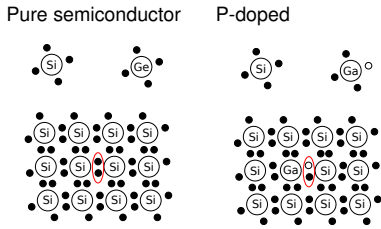


# Semiconductors and doping

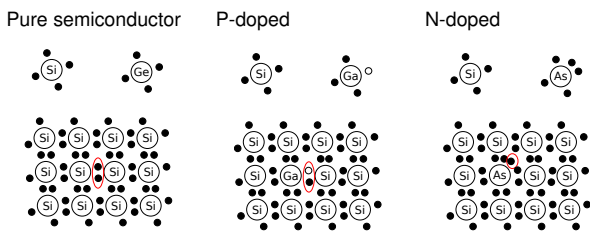


# PN-junction

No bias

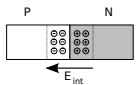


# PN-junction

No bias

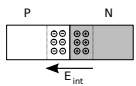

Reverse bias

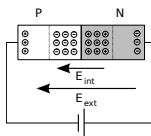

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---


---

---


---

# PN-junction


No bias

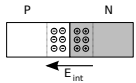

Reverse bias

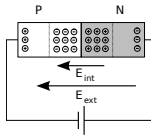

Forward bias

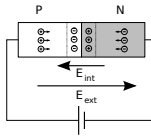

Notes

---

---

---

---


---

---

---

---


# Real diode

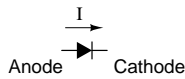

$$I(V) = I_0 \left( e^{V/(nV_T)} - 1 \right)$$

Typical parameters

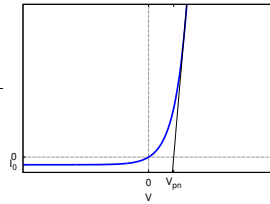- saturation current  $I_0 = 1 \text{ nA}$
- thermal voltage  $V_T = \frac{kT}{q} = 25.85 \text{ mV}$  at 300 K
- emission coefficient  $n = 1..2$



Notes

---

---

---

---


---

---

---

---


# Real diode

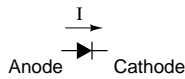

$$I(V) = I_0 \left( e^{V/(nV_T)} - 1 \right)$$

Typical parameters

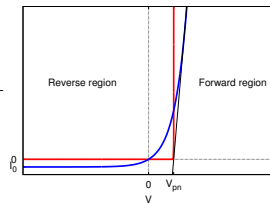- saturation current  $I_0 = 1 \text{ nA}$
- thermal voltage  $V_T = \frac{kT}{q} = 25.85 \text{ mV}$  at 300 K
- emission coefficient  $n = 1..2$



Notes

---

---

---

---


---

---

---


---

# Simplified diode

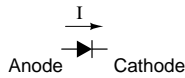


$V_{pn}$  diode P-N junction opening voltage

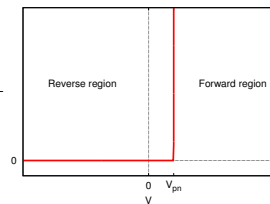- $V_{pn} = 0.6 \text{ V}$  for Si
- $V_{pn} = 0.3 \text{ V}$  for Ge



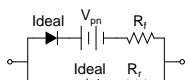A bit more realistic diode ( $R_r \gg R_f$ )



Notes

---

---

---

---

---

---

---

---

# Diodes applications

- Circuit Protection
- Rectification
  - current gate
  - half wave rectifier
  - full wave rectifier
  - Power Supplies
- Frequency manipulation
  - Frequency multiplier
  - Mixers
- and more ...
  - Voltage clamps
  - light emitting diodes (LED)
  - photo-diode

Notes

---

---

---

---

---


---

---

---

Eugeniy Mikhailov (W&M) Electronics 1 Lecture 05 8 / 13

## Half-wave rectifier, current gate

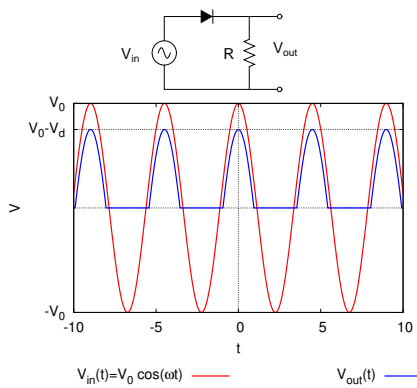

Notes

---

---

---

---

---


---

---

---

Eugeniy Mikhailov (W&M) Electronics 1 Lecture 05 9 / 13

## Full-wave rectifier: $V_{in} \gg V_d \rightarrow V_{out} \approx |V_{in}|$

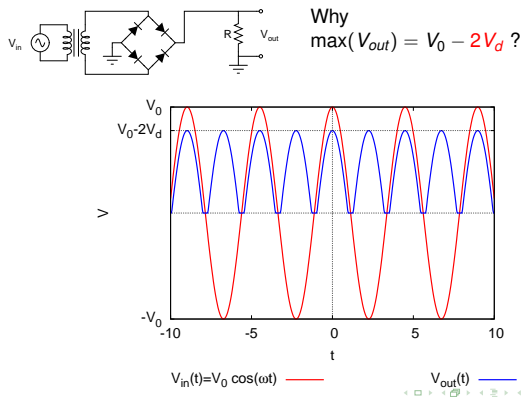

Notes

---

---

---

---

---


---

---

---

Eugeniy Mikhailov (W&M) Electronics 1 Lecture 05 10 / 13
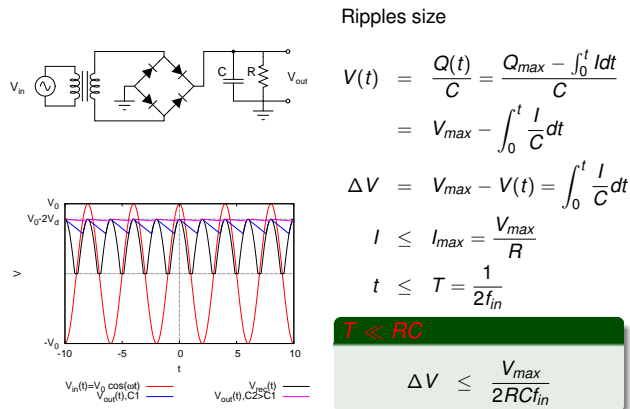
## Full-wave rectifier filtered - power supply



Notes

---

---

---

---



---

---

---



---
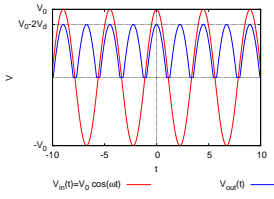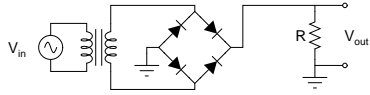
# Full-wave rectifier as Frequency doubler





Navigation icons: back, forward, search, etc.
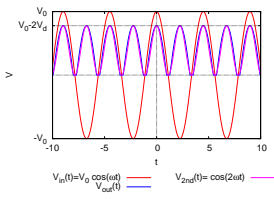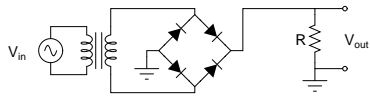
# Full-wave rectifier as Frequency doubler





Navigation icons: back, forward, search, etc.
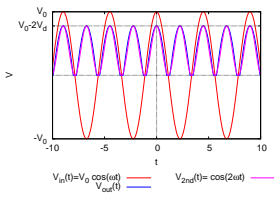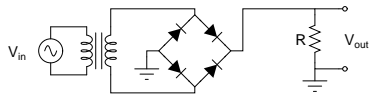
# Full-wave rectifier as Frequency doubler



Navigation icons: back, forward, search, etc.
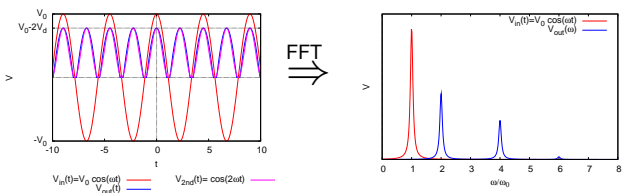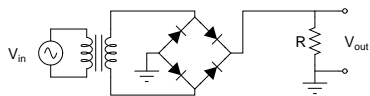
# Full-wave rectifier as Frequency doubler



Navigation icons: back, forward, search, etc.

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---


---

---

---

---
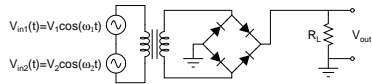
## Full-wave rectifier as Frequency adder



$$V_{out}(t) = |V_{in}(t)| = \sqrt{V_{in}^2(t)} = \sqrt{(V_1 \cos(\omega_1 t) + V_2 \cos(\omega_2 t))^2}$$

$$= \sqrt{V_1^2 \cos^2(\omega_1 t) + 2 V_1 V_2 \cos(\omega_1 t) \cos(\omega_2 t) + V_2^2 \cos^2(\omega_2 t)}$$

Assuming  $V_1 \gg V_2$

$$V_{out}(t) \approx \sqrt{V_1^2 \cos^2(\omega_1 t) + 2 V_1 V_2 \cos(\omega_1 t) \cos(\omega_2 t) + V_2^2 \cos^2(\omega_2 t)}$$

$$\approx V_1 \left( \cos(\omega_1 t) + \frac{V_2}{V_1} \cos(\omega_1 t) \cos(\omega_2 t) \right)$$

$$\approx V_1 \left( \cos(\omega_1 t) + \frac{V_2 \cos((\omega_1 + \omega_2)t) + \cos((\omega_1 - \omega_2)t)}{2} \right)$$

Navigation icons: back, forward, search, etc.

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---

Notes

---

---

---

---

---

---

---

---