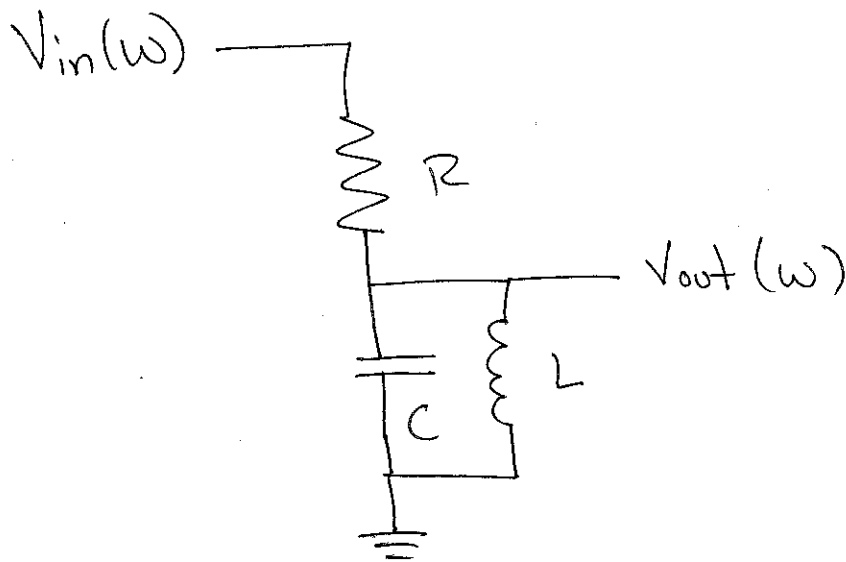


3-4



$$V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$$

$$Z_1 = R$$

$$Z_2 = Z_C \parallel Z_L$$

$$= \frac{Z_C Z_L}{Z_C + Z_L}$$

$$\text{where } Z_C = \frac{1}{i\omega C}$$

$$Z_L = i\omega L$$

$$Z_2 = \frac{\left(\frac{i\omega L}{i\omega C}\right)}{i \cdot \frac{1}{i\omega C} + i\omega L} = \frac{(L/C)}{i(\omega L - 1/\omega C)}$$

$$V_{out} = V_{in} \left(\frac{\frac{L/C}{i(\omega L - 1/\omega C)}}{R + \frac{L/C}{i(\omega L - 1/\omega C)}} \right) \cdot \frac{i(\omega L - 1/\omega C)}{i(\omega L - 1/\omega C)}$$

$$= \frac{LC^{-1}}{LC^{-1} + i(\omega L - 1/\omega C)R}$$

$$\frac{LC^{-1} - i(\omega L - 1/\omega C)R}{LC^{-1} - i(\omega L - 1/\omega C)R}$$

$$V_{out} = V_{in} \frac{(LC^{-1})^2 - i(\omega L - 1/\omega C)LC^{-1}R}{(LC^{-1})^2 + (\omega L - 1/\omega C)^2 R^2}$$

$$= a + ib$$

$$|V_{out}| = \sqrt{a^2 + b^2} = \frac{[(LC^{-1})^4 + (\omega L - 1/\omega C)^2 (LC^{-1}R)^2]^{1/2}}{(LC^{-1})^2 + (\omega L - 1/\omega C)^2 R^2}$$

$$\tan \phi = b/a$$

$$\phi = \tan^{-1} \left(\frac{-(\omega L - 1/\omega C)LC^{-1}R}{(LC^{-1})^2} \right)$$

$$= \tan^{-1} \left(\frac{-(\omega L - 1/\omega C)R}{LC^{-1}} \right)$$

$$\phi = \tan^{-1} \left(\frac{RC(1/\omega C - \omega L)}{L} \right)$$

$$L = 10 \mu H$$

$$C = 1 \mu F$$

$$R = 1 k \Omega$$

```

R := 1000 :
C := 10-6 :
L := 10 · 10-6 :
evalf(ω0 = (L · C)-1/2);

```

$$\omega_0 = 3.162277660 \cdot 10^5$$


(1)

$$V_{out} := \frac{\left(\left(\frac{L}{C} \right)^4 + \left(\omega \cdot L - \frac{1}{\omega \cdot C} \right)^2 \left(\frac{L \cdot R}{C} \right)^2 \right)^{\frac{1}{2}}}{\left(\frac{L}{C} \right)^2 + \left(\omega \cdot L - \frac{1}{\omega \cdot C} \right)^2 R^2} :$$

$$phase := \arctan \left(\frac{R \cdot C \cdot \left(\frac{1}{\omega \cdot C} - \omega \cdot L \right)}{L} \right) :$$

```
with(plots) :
```
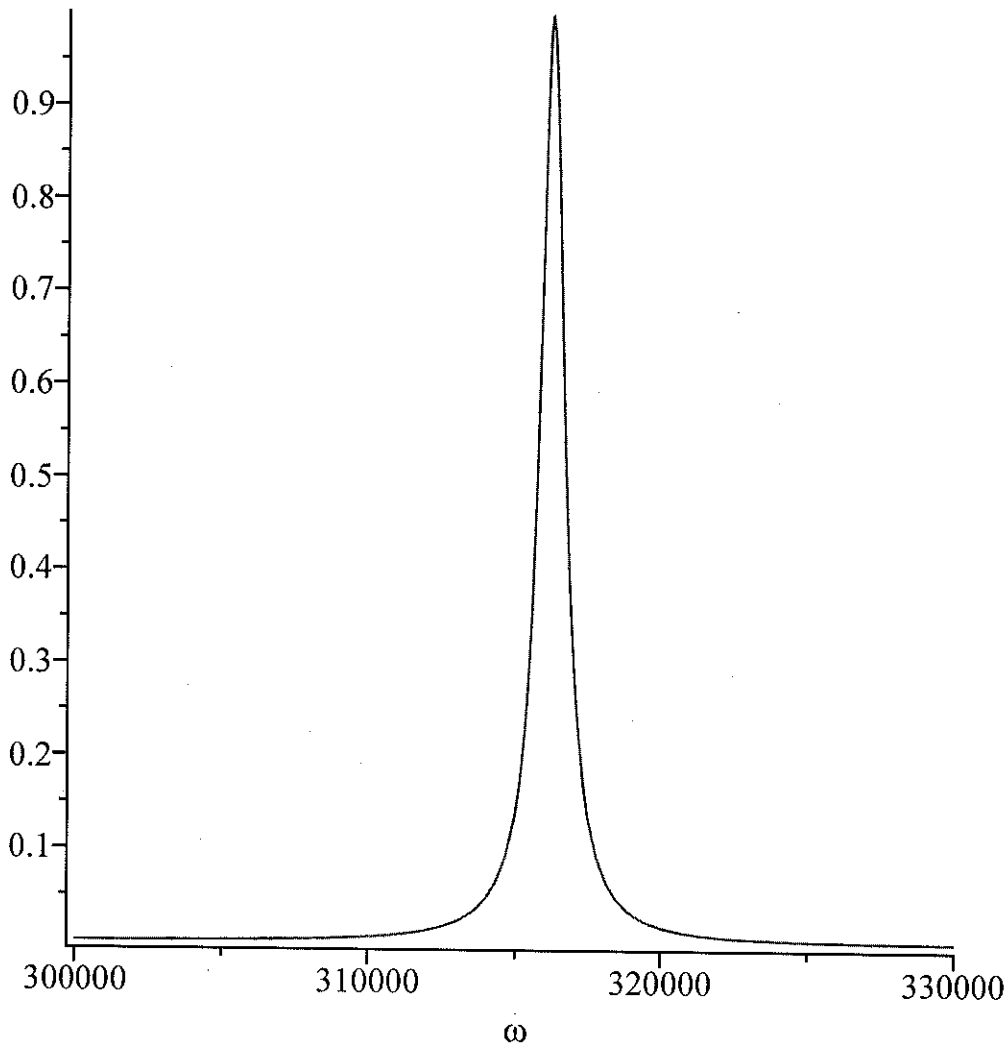
```
plot([Vout], ω = 300000 .. 330000);
```



```
plot(phase, ω = 300000 .. 330000);
```

