

# Transistors: Field-effect transistors

Eugeniy E. Mikhailov

The College of William & Mary



Lecture 08

Notes

---

---

---

---

---

---


---

---

## Field-effect transistor (FET)

### Junction-FET

NJFET

 

PJFET



### Metal-Oxide-Semiconductor FET (MOSFET)

- gate is truly isolated
- there is a fourth terminal usually connected to source

NMOSFET



PMOSFET



Notes

---

---

---

---

---

---

---

---

## FET vs BJT

### FET pros

- very high input impedance
  - JFET - impedance  $10^{12} \Omega$
  - MOSFET - impedance  $10^{14} \Omega$
- thus very small current into the base (pA range)
- as result very little power consumption for the biasing network
- can operate bidirectionally

### FET cons

- have large parameter spread

Notes

---

---

---

---

---

---

---

---

## Let's focus on NJFET



### General notes

- N-channel usually faster due to higher mobility of electrons vs holes
- current goes from drain to source (thus the names)
- drain and source are nearly identical
  - thus sometimes gate is centered on some diagrams
- can be used backwards with almost the same performance
- arrow indicates direction of the PN junction
- thus normal operation (low current into the gate) when  $V_G < V_S$

Notes

---

---

---

---

---

---


---

---
 
## NJFET gate voltage rules

$V_p$ : pinch-off voltage (intrinsic parameter),  $V_p < 0$  for NJFETs  
it is called  $V_{th}$ :threshold voltage for MOSFETs

- $V_{GS} < V_p$ 
  - $I_D = 0$
- $V_{GS} > 0.6\text{ V}$ 
  - device fails, remember about gate diode



- $V_p < V_{GS} < 0.6\text{ V}$ 
  - normal operation
  - $I_d(V_{GS}, V_{DS})$

## $I_d$ vs $V_{DS}$


Linear region

- $V_{DS} < V_{GS} - V_p$ 
  - $I_d(V_{DS}, V_{GS}) = k(2(V_{GS} - V_p)V_{DS} - V_{DS}^2)$


Saturation region

- $V_{DS} > V_{GS} - V_p$ 
  - $I_d(V_{DS}, V_{GS}) = k(V_{GS} - V_p)^2$


$k$  is a constant

 

## Real $I_d$ vs $V_{DS}$ linear region

 

## Real $I_d$ vs $V_{DS}$ linear region

 

- $V_{DS} < V_{GS} - V_p$ 
  - $I_d(V_{DS}) = k(2(V_{GS} - V_p)V_{DS} - V_{DS}^2) \approx 2k(V_{GS} - V_p)V_{DS}$


Notes

Notes

Notes

Notes
 
## Real $I_d$ vs $V_{DS}$ saturation region



Notes

---

---

---

---

---

---

---


---

---

---

$I_{DSS}$  saturation drain current, depends on  $V_{GS}$  and  $V_p$
 
## Real $I_d$ vs $V_{DS}$ saturation region



- $V_{DS} > V_{GS} - V_p$
- $I_d(V_{DS}) = k(V_{GS} - V_p)^2$

$I_{DSS}$  saturation drain current, depends on  $V_{GS}$  and  $V_p$

Notes

---

---

---

---

---

---

---

---

---

---

## Reading the specifications

2N3958

Vishay Siliconix



SPECIFICATIONS ( $T_A = 25^\circ\text{C}$ UNLESS OTHERWISE NOTED)						
Parameter	Symbol	Test Conditions	Limits			Unit
			Min	Typ <sup>2</sup>	Max	
<b>Static</b>						
Gate-Source Breakdown Voltage	$V_{BSS}$	$I_S = -1\ \mu\text{A}, V_{GS} = 0\ \text{V}$	-50	-57		V
Gate-Source Forward Current	$I_{GS}$	$V_{GS} = 20\ \text{V}, V_{DS} = 0\ \text{V}$		10	20	mA
Saturation Drain Current	$I_{SDS}$	$V_{GS} = -30\ \text{V}, V_{DS} = 0\ \text{V}$		10	150	mA
Gate Reverse Current	$I_{RSS}$	$V_{GS} = -30\ \text{V}, V_{DS} = 0\ \text{V}$ $T_A = 150^\circ\text{C}$	-10		-100	mA
Gate Operating Current	$I_G$	$V_{GS} = 20\ \text{V}, I_D = 200\ \text{mA}$ $T_A = 150^\circ\text{C}$	-5		-50	mA
Gate-Source Voltage	$V_{GS}$	$V_{DS} = 20\ \text{V}, I_D = 200\ \text{mA}$ $I_G = 50\ \mu\text{A}$	-0.5	-1.5	-4	V
Gate-Source Forward Voltage	$V_{GS(F)}$	$I_G = 1\ \text{mA}, V_{GS} = 0\ \text{V}$			2	V
<b>Dynamic</b>						
Common-Source Forward Transconductance	$g_m$	$V_{GS} = 20\ \text{V}, V_{DS} = 0\ \text{V}$ $I_D = 1\ \text{mA}$		2	35	mS
Common-Source Output Conductance	$g_{os}$					μS

Notes

---

---

---

---

---

---

---


---

---

---

$V_{GS(on)}$  is the same as  $V_p$

## NJFET voltage controlled divider

 

Transistor in the linear region

$$I_d(V_{DS}, V_{GS}) = k(2(V_{GS} - V_p)V_{DS} - V_{DS}^2)$$

Notes

---

---

---

---

---

---


---

---

---

---
 
## NJFET compensated voltage controlled divider



Transistor in the linear region

$$I_d(V_{DS}, V_{GS}) = k (2(V_{GS} - V_p)V_{DS} - V_{DS}^2)$$

$$V_g = (V_{ds} + V_{ctrl})/2$$

$$R \gg R_d$$

Notes

---

---

---

---

---



---

---

---

## NJFET constant current source

Transistor in the saturation region

  

Notes

---

---

---

---

---


---

---

---

## FET source follower


Transistor in saturation region

 

$$V_{out} = \frac{R_s}{R_s + 1/g_m} V_{in}$$

$$r_{th} > 1/g_m$$

$$V_{out} > V_{in}$$

 

Notes

---

---

---

---

---


---

---

---

## FET source follower improved

Transistor in saturation region

 

Requires **matched** pair of transistors

$$V_{out} = V_{in}$$

$$V_{out} = V_{in}$$

$$R_{th} = R_s$$

Notes

---

---

---

---

---

---

---

---