

# Week 11 lab - Real OpAmps

## Task 1

Build a **simple** inverting amplifier with a gain of 10. Use an LM741 and an input resistor  $R_1$  around (10 — 15) k $\Omega$ . Connect the input to the reference. Measure the output voltage.

Try at least 5 different LM741, and keep track which OpAmp generates which output.

## Task 2

Repeat the previous assignment with all resistors increased by a factor of 10. Find the worst OpAmp and put it aside.

Assuming that there is no input offset current, deduce the input offset voltage ( $V_{OS}$ ) and input bias current ( $I_B$ ) for each of the OpAmp. How does it compare with the specification sheet?

## Task 3

Replace the LM741 with OP27 and measure output voltage again. What can you say about the LM741 OpAmp and the OP27 OpAmp? Which one is better and why?

## Task 4

Use the worst OpAmp selected in task 2. Build the bias compensation circuit and measure the deviation of the output from 0 V.

## Task 5 - bonus 2 point

You will get the bonus if you are able to "fully" compensate your amplifier, i.e. the output voltage deviates from 0 V to less than 2 mV.