

Diodes.

Eugeniy E. Mikhailov

The College of William & Mary



Lecture 05

Notes

Midterm exam

Where: In the lab

When: During the first hour of the lab

Material:



- everything from first 4 weeks of class
- Resistors, capacitors, inductors, and transformers.
- Kirchhoff's laws
- Complex impedances.
- Thévenin's theorem
 - Source impedance and voltage
- Voltage divider in various forms
- Filters

Lab will follow the midterm.

You can skip design exercise preparation prior to the lab. However, at the time of log book submission it must be fully done. Treat it as a home work.

Notes


Ideal diode

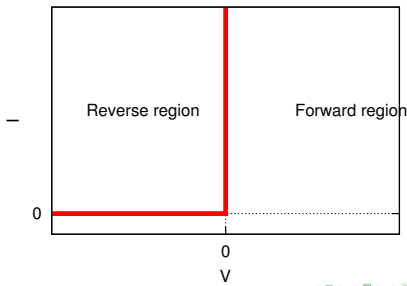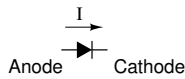

Notes


Semiconductors and doping

Pure semiconductor

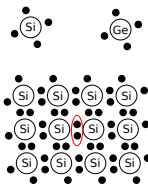


Notes


Semiconductors and doping

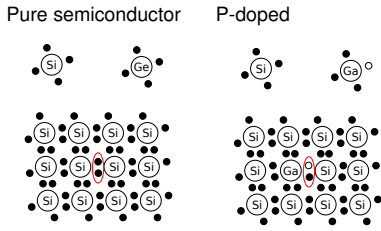


Semiconductors and doping

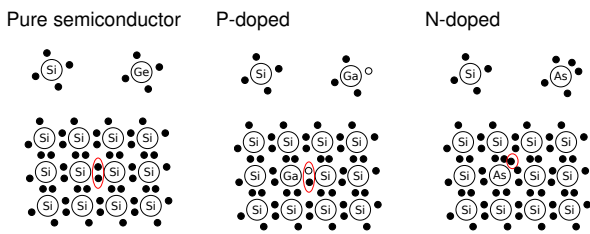

PN-junction

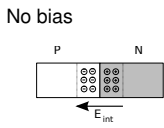

PN-junction

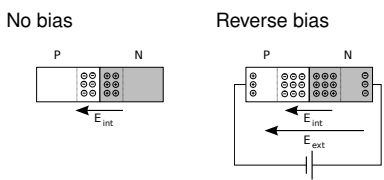

Notes


Notes

Notes


Notes

PN-junction


No bias

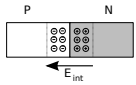

Reverse bias

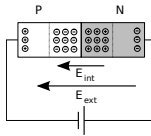


Forward bias

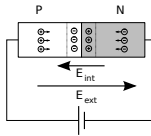

Notes


Real diode

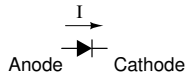

$$I(V) = I_0 \left(e^{V/(nV_T)} - 1 \right)$$


Typical parameters

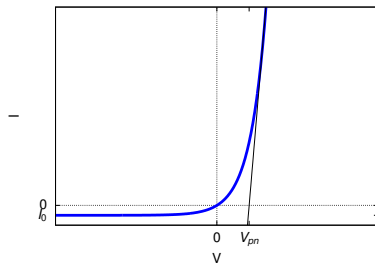- saturation current $I_0 = 1 \text{ nA}$
- thermal voltage $V_T = \frac{kT}{q} = 25.85 \text{ mV at } 300 \text{ K}$
- emission coefficient $n = 1..2$



Notes


Real diode

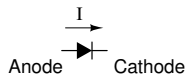

$$I(V) = I_0 \left(e^{V/(nV_T)} - 1 \right)$$


Typical parameters

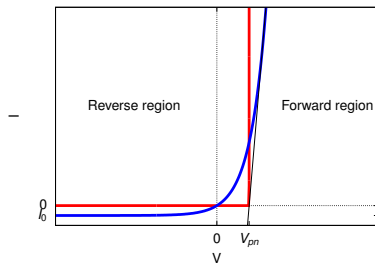- saturation current $I_0 = 1 \text{ nA}$
- thermal voltage $V_T = \frac{kT}{q} = 25.85 \text{ mV at } 300 \text{ K}$
- emission coefficient $n = 1..2$




Notes

Simplified diode

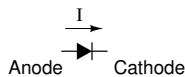


V_{pn} diode P-N junction opening voltage

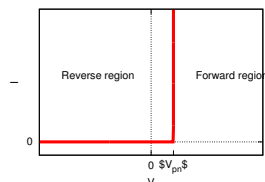- $V_{pn} = 0.6 \text{ V for Si}$
- $V_{pn} = 0.3 \text{ V for Ge}$



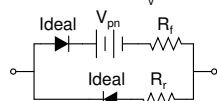A bit more realistic diode ($R_r \gg R_f$)





Notes

Diodes applications

- Circuit Protection
- Rectification
 - current gate
 - half wave rectifier
 - full wave rectifier
 - Power Supplies
- Frequency manipulation
 - Frequency multiplier
 - Mixers
- and more ...
 - Voltage clamps
 - light emitting diodes (LED)
 - photo-diode


Notes

Half-wave rectifier, current gate

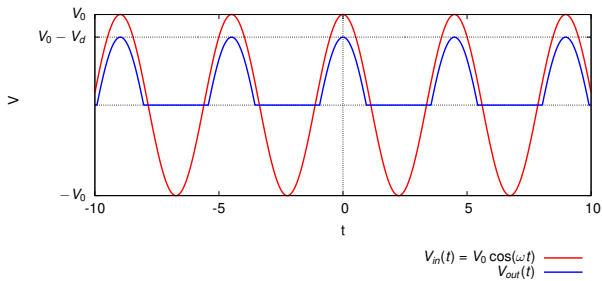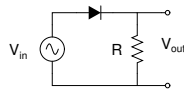


Notes

Full-wave rectifier: $V_{in} \gg V_d \rightarrow V_{out} \approx |V_{in}|$

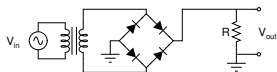


Why $\max(V_{out}) = V_0 - 2V_d$?

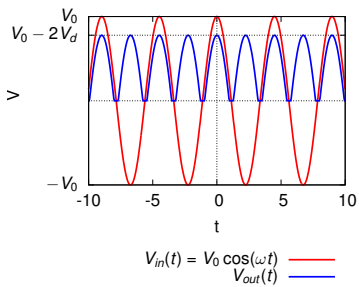


Notes

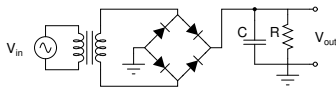Full-wave rectifier filtered - power supply



Ripples size
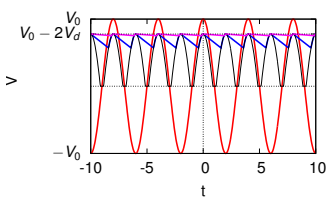
$$\begin{aligned}
 V(t) &= \frac{Q(t)}{C} = \frac{Q_{max} - \int_0^t I dt}{C} \\
 &= V_{max} - \int_0^t \frac{I}{C} dt \\
 \Delta V &= V_{max} - V(t) = \int_0^t \frac{I}{C} dt \\
 I &\leq I_{max} = \frac{V_{max}}{R} \\
 t &\leq T = \frac{1}{2f_{in}}
 \end{aligned}$$




$T \ll RC$

$$\Delta V \leq \frac{V_{max}}{2RCf_{in}}$$


Notes

Full-wave rectifier as Frequency doubler

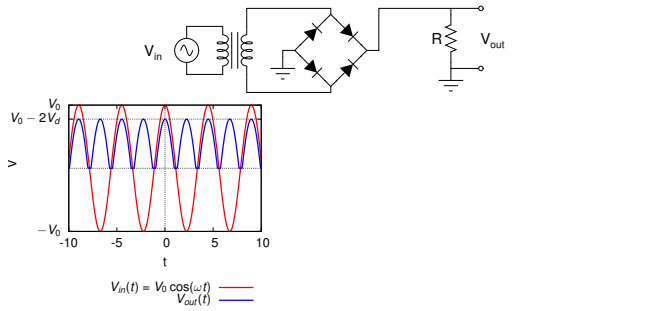


Navigation icons: back, forward, search, etc.

Full-wave rectifier as Frequency doubler

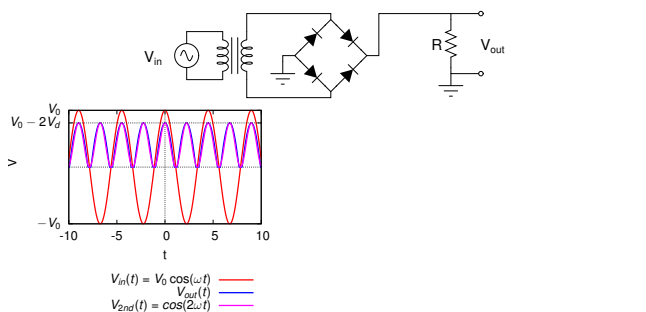


Navigation icons: back, forward, search, etc.

Full-wave rectifier as Frequency doubler

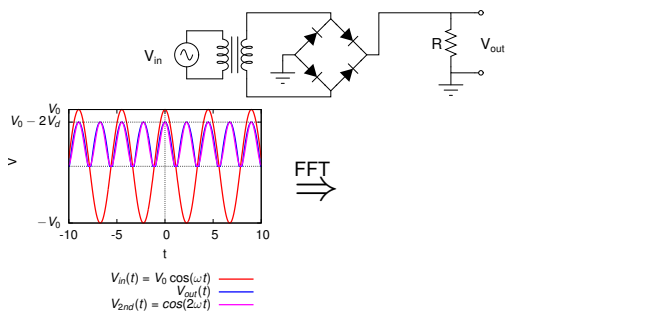

Navigation icons: back, forward, search, etc.

Full-wave rectifier as Frequency doubler

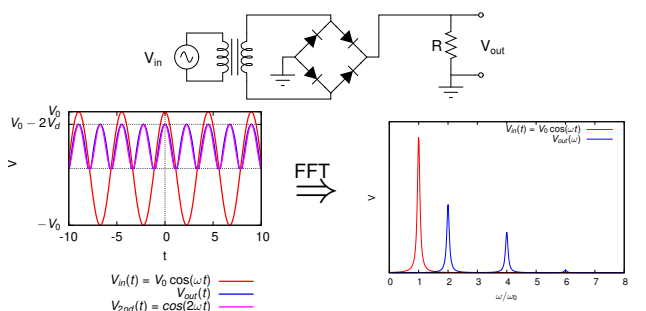

Navigation icons: back, forward, search, etc.


Notes

Notes

Notes

Notes

Full-wave rectifier as Frequency adder

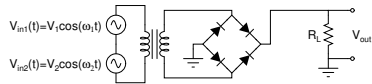

$$V_{out}(t) = |V_{in}(t)| = \sqrt{V_{in}^2(t)} = \sqrt{(V_1 \cos(\omega_1 t) + V_2 \cos(\omega_2 t))^2}$$

$$= \sqrt{V_1^2 \cos^2(\omega_1 t) + 2 V_1 V_2 \cos(\omega_1 t) \cos(\omega_2 t) + V_2^2 \cos^2(\omega_2 t)}$$

Assuming $V_1 \gg V_2$

$$V_{out}(t) \approx \sqrt{V_1^2 \cos^2(\omega_1 t) + 2 V_1 V_2 \cos(\omega_1 t) \cos(\omega_2 t) + V_2^2 \cos^2(\omega_2 t)}$$

$$\approx V_1 \left(\cos(\omega_1 t) + \frac{V_2}{V_1} \cos(\omega_1 t) \cos(\omega_2 t) \right)$$

$$\approx V_1 \left(\cos(\omega_1 t) + \frac{V_2 \cos((\omega_1 + \omega_2)t) + \cos((\omega_1 - \omega_2)t)}{2} \right)$$

Navigation icons: back, forward, search, etc.

Notes

Notes

Notes

Notes
