
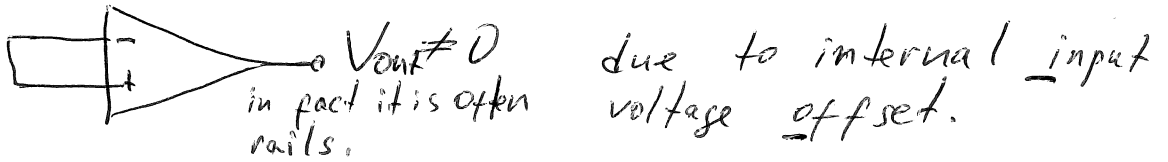


Non-ideality of OpAmps

Input voltage offset

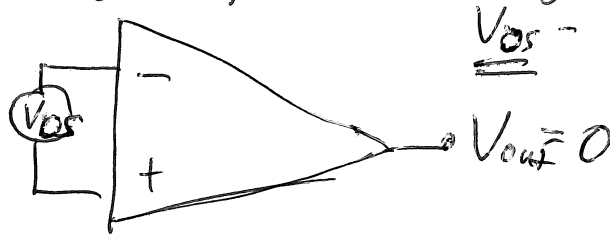


Voltage required to get $V_o = 0$ is called




Impact of V_{io}

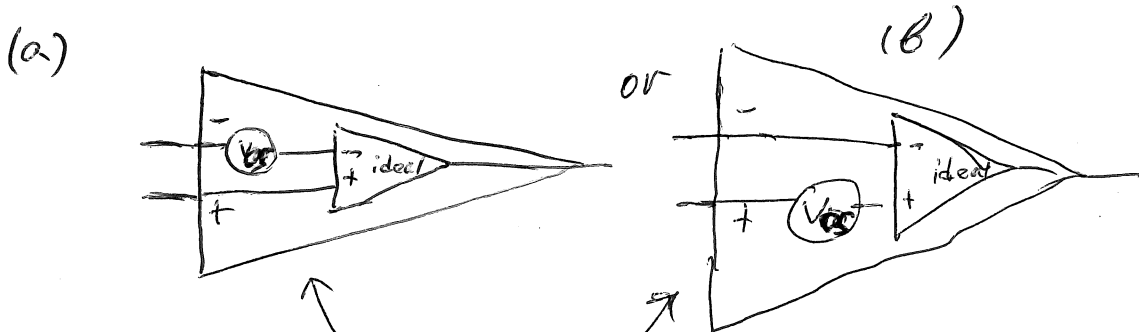It is convenient to treat non-ideal OpAmp as ideal + some disturbance.




they are equivalent except the V_{os} sign flip

Non-inverting Op-Amp

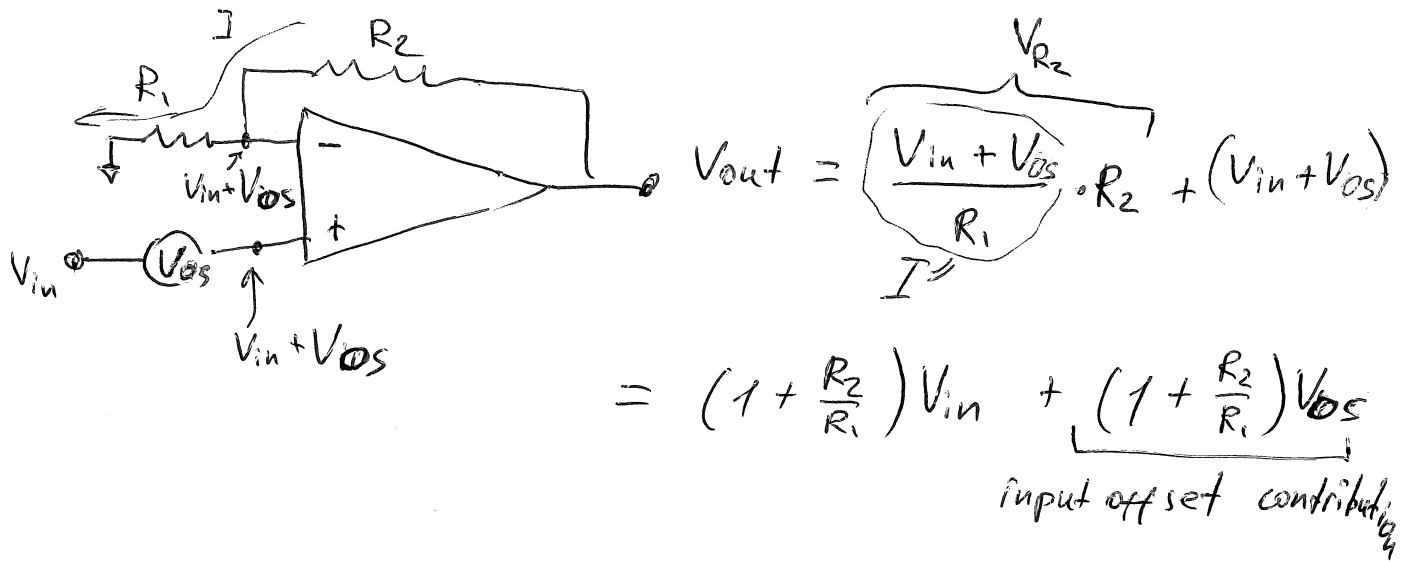

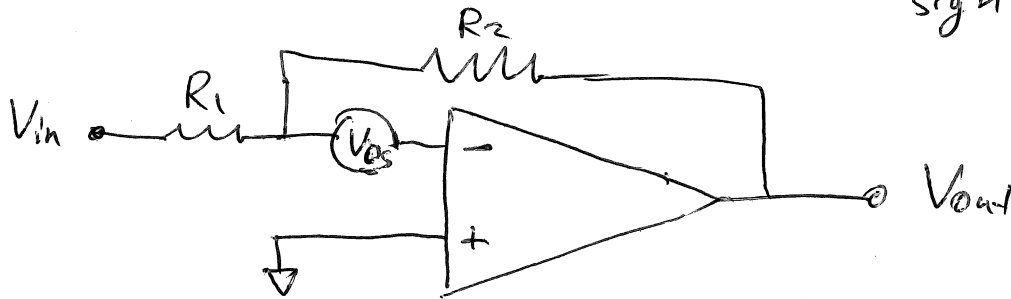HW 1 Show that model (a) is equivalent to (b), i.e. prove that V_{io} contribution to the output is the same as above in the following model. Mind the (-) sign.




Some spec. sheet values

LM741	$V_{os} = 2 \div 6 \text{ mV}$
OP27	$V_{os} = 30 \div 100 \mu\text{V}$


Moreover V_{os} has temperature dependence and drifts with time.

How to compensate input offset voltage?

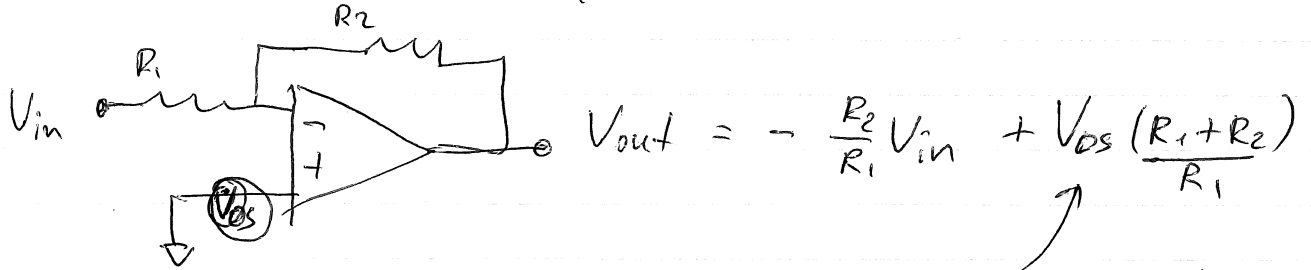by adding compensating voltage via adder circuit for example



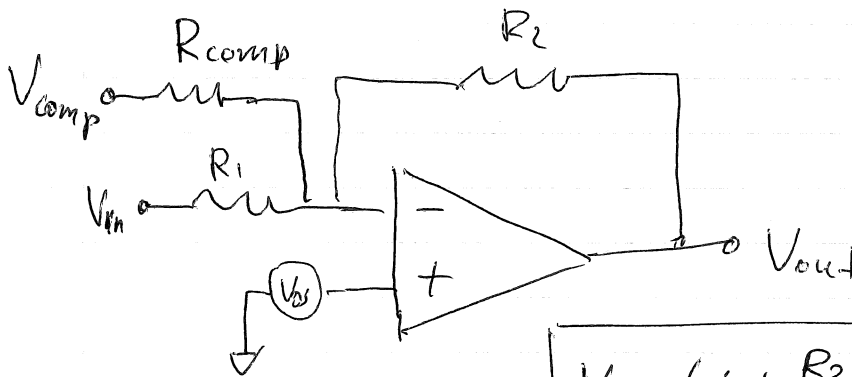
So we need to provide compensating voltage



$$V_{0s} \left(1 + \frac{R_2}{R_1}\right) = \frac{R_2}{R_{comp}} V_{comp}$$

Input Bias current

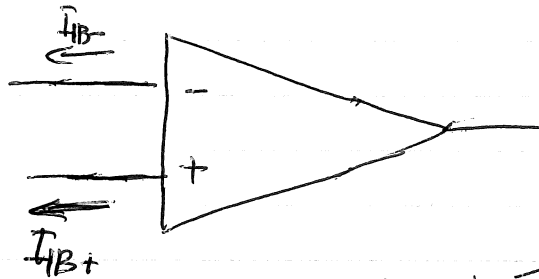Unlike an ideal opAmp story, the inputs of this op-amp might feed or source current



I_B is defined as

$$I_{IB} = \frac{I_{IB-} + I_{IB+}}{2}$$


input bias current.

For simplicity it is often assumed or modeled that

$$I_{IB+} = I_{IB-} = I_{IB}$$

By the way direction of I_{IB} could be any : in or out

Inverting of Amp and I_{IB}

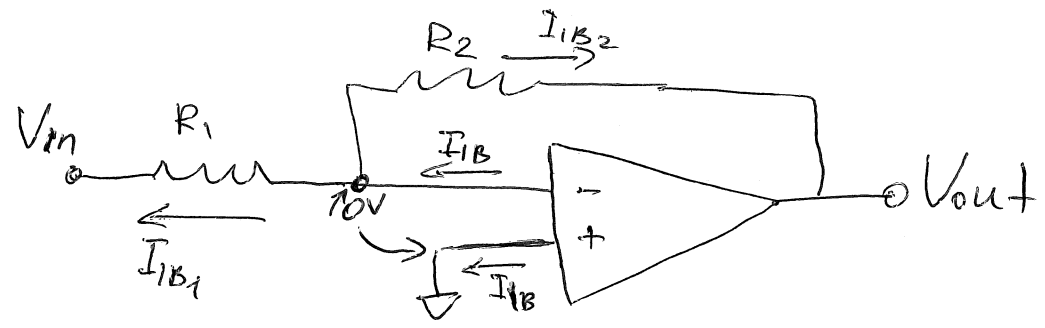


We will use principle of superposition

$$V_{out} = \text{Sum of } V_{in \text{ contrib}} = -\frac{R_2}{R_1} V_{in}$$

and I_{IB} contribution.

First notice $V_+ = 0$ there is no voltage drop on hook up wire. ~~also~~


Bias current contribution

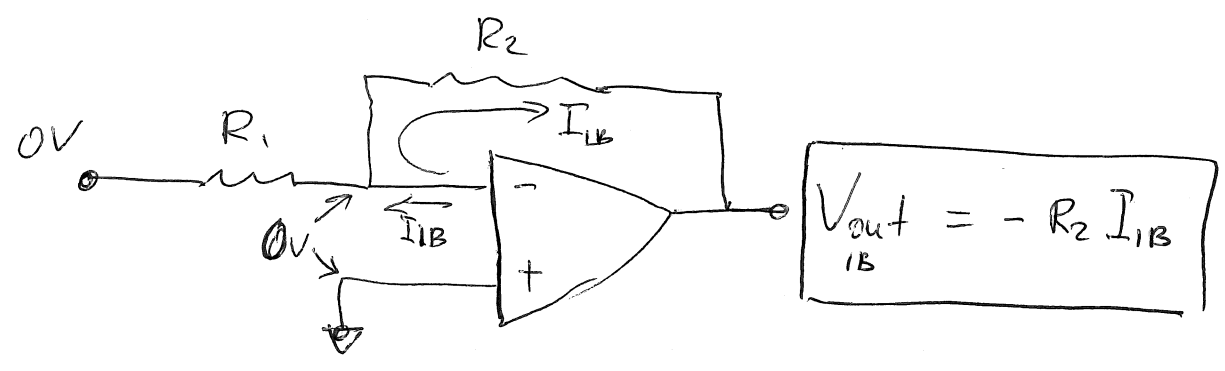

Is it a big deal?

Op Amp	I_{IB}	$V_{out_{IB}}$ for $1k\Omega R_2$	$V_{out_{IB}}$ for $R_2 = 1M\Omega$
LM741	$80 \div 500 \text{ nA}$	$80 - 500 \mu\text{V}$	$80 - 500 \text{ mV} \leftarrow \text{wow!}$
OP27	$15 \div 80 \text{ nA}$	$15 \div 80 \mu\text{V}$	$15 \div 80 \text{ mV}$

How to cure non zero I_{IB} problem?

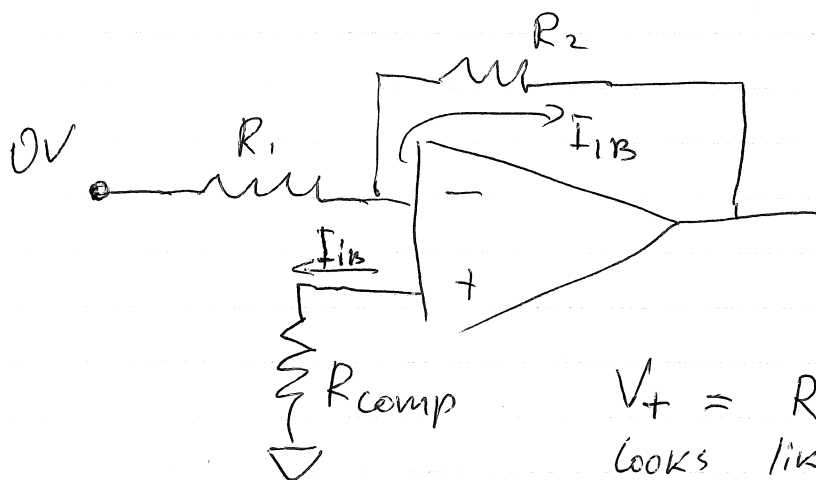

$V_+ = R_{comp} I_{IB}$
looks like offset voltage problem


$$\Rightarrow V_{comp} = (R_{comp} \cdot I_{IB}) \left(1 + \frac{R_2}{R_1} \right)$$

We want $V_{comp} + V_{out} = 0$

$$R_{comp} \left(\frac{R_1 + R_2}{R_1} \right) - R_2 = 0$$

$$\Rightarrow R_{comp} = \frac{R_2 R_1}{R_1 + R_2} = R_{2||1}$$

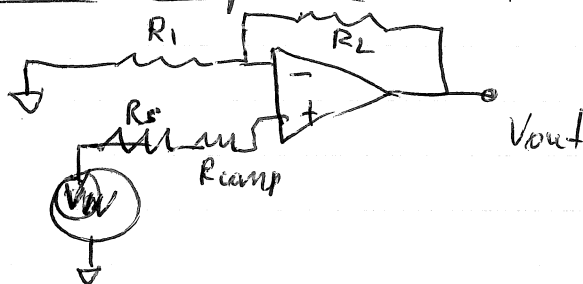Notice that similar case can be shown for Non-Inverting op Amp but one should remember about source impedance of input voltage



Input offset current

Usually $I_{IB-} \neq I_{IB+}$
 $\rightarrow I_{IO} = I_{IB-} - I_{IB+}$

Op Amp	I_{IO}
LM441	20 ÷ 200 nA
OP27	12 ÷ 75 nA

HW2

Show the contribution of I_{IO} to the non compensated for I_{IB} inverting opAmp output voltage.

HW3

Do the same but for I_{IB} compensated inverting opAmp.

Hint: Use superposition principle