

# Lecture 13

(P1)

## Digital electronics

We are concerned with signals only in two states: yes/no, on/off, high/low, 0/1.

When we are working with a real circuit it is convenient to talk about voltage states. Then we would say: high/low

On paper we would represent it as 1 or 0

Truth tables spell out output state(s) for all possible combinations of input(s)

Some common elements of digital electronics, also known as gates

Symbol



in	out
1	1
0	0


Expression

$$\text{Out} = A$$



in	out
1	0
0	1


$$\text{Out} = \bar{A}$$

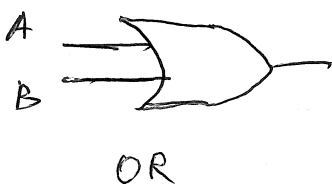

in		out
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

$$\text{Out} = A + B$$

(P2)

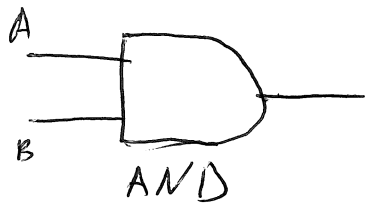

in		out
A	B	
0	0	0
0	1	0
1	0	0
1	1	1

$$\text{out} = AB$$



in		out
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

$$\text{out} = A \oplus B$$

Switch on a buzzer when a car engine is working and a driver is present but no earlier than timer  $t_1$  is triggered, switch the buzzer off after time  $t_2$  but do not do it if special switch overrides  $t_2$  timer.

$$e \cdot d \cdot t_1 \cdot (\overline{t_2} + s)$$

e	d	t <sub>1</sub>	t <sub>2</sub>	s	b
0	x	x	x	x	0
x	0	x	x	x	0
x	x	0	x	x	0
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	0
1	1	1	1	1	1

note x stands for do not care

# Adding two numbers (actually bits)

We would like to do arithmetic sum

A + B in decimal world it is easy

Both A and B can be 0 or 1

$$A + B = \left\{ \begin{matrix} 0 \\ 1 \\ 2 \end{matrix} \text{ in decimal} \right\} = \left\{ \begin{matrix} 00 \\ 01 \\ 10 \end{matrix} \text{ in binary} \right\}$$

↑  
arithmetic

## Truth table


A	B	out <sub>2</sub>	out <sub>1</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

↑  
carry on bit

$$\text{out}_2 = A \cdot B$$


$$\text{out}_1 = A \oplus B$$

↑  
logical

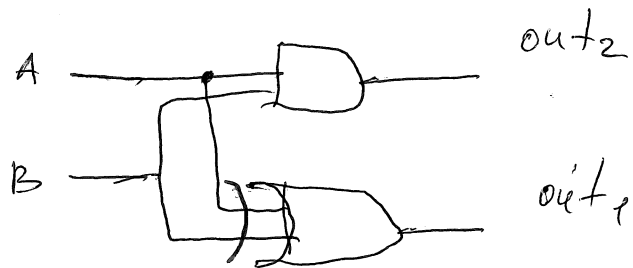

# Physical implementation


How to get High / low

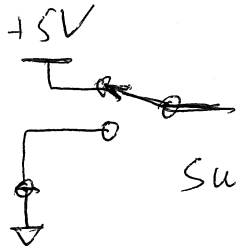


switch

but this requires a double throw switch

How about

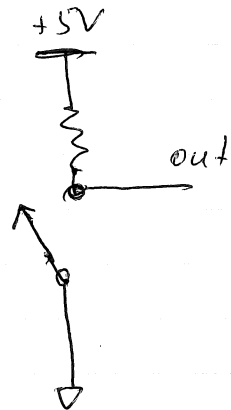

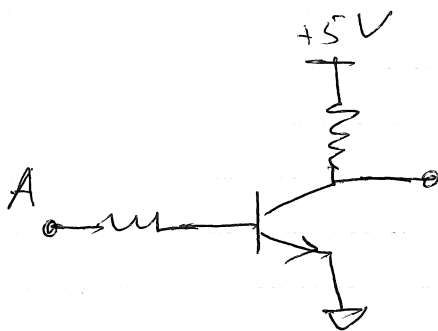someone has to physically close this switch





out =  $\bar{A}$

this is actually inverter

NOR gate  $\overline{A+B}$

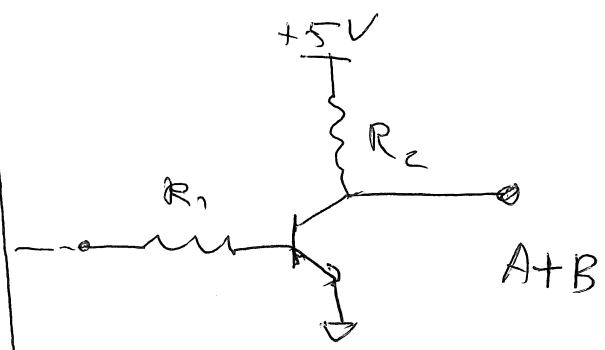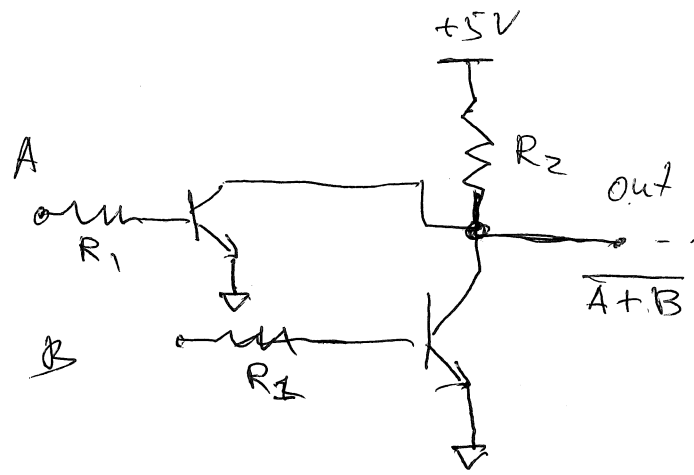
OR gate  $A+B$   
just adding an inverter



transistors must be in saturation

i.e.  $\beta \cdot I_B \gg \frac{5V}{R}$

$R_1 = 680 \Omega, R_2 = 470 \Omega$

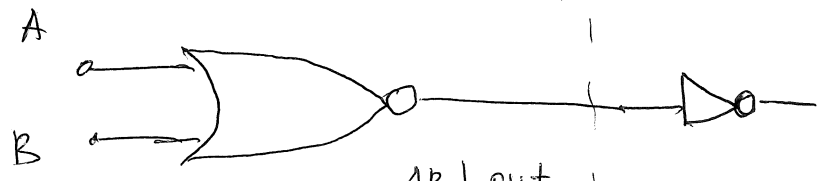

AB	out
00	1
01	0
10	0
11	0


Above is an example of Resistor-Transistor Logic (RTL)

Current implementations are quite different.


See TTL (transistor transistor logic) and CMOS series

One gate type can be built from others.

For example

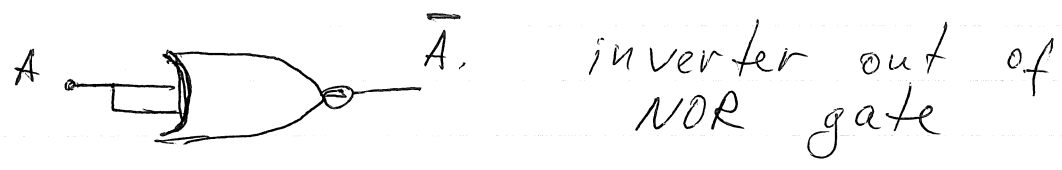

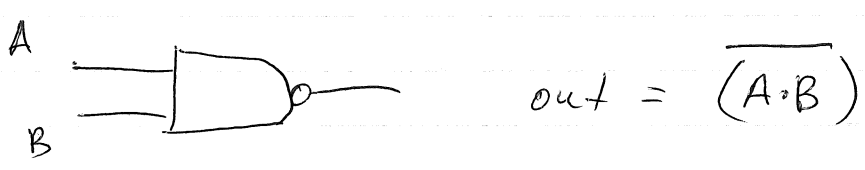There is also NAND gate which is very useful too



It can be shown that you can construct any gate ( inverter, OR, AND, XOR ) from a combination of either NOR or NAND, or obviously mix of NOR and NAND

HW 1

Using only a NOR gate show schematics for OR, AND, and XOR. you can use inverter since we know how to build it with NOR

HW 2 ~~Be~~ Construct 3 bit adder:  $A+B+C$  <sup>arithmetic</sup> with gates of your choice. Note  $1+1+1 = 11$  in binary