

# Full network analysis.

Eugeniy E. Mikhailov



WILLIAM & MARY

CHARTERED 1693

Lecture 02

# Kirchhoff's Laws

## Kirchhoff's Current Law

The algebraic sum of currents entering and exiting a node equals zero

Convention (quite arbitrary): currents going into the nodes are positive, the ones which go out of the node are negative.


## Kirchhoff's Voltage Law

The algebraic sum of all voltage changes (aka voltage drops) in a loop equals zero

Notes:

- chose a direction along which you travel a network. If you go over a resistor and current runs the same way then voltage change is negative, otherwise its positive.
- If you go over a voltage source from the negative terminal to the positive terminal the voltage change is positive, otherwise negative.

# Example

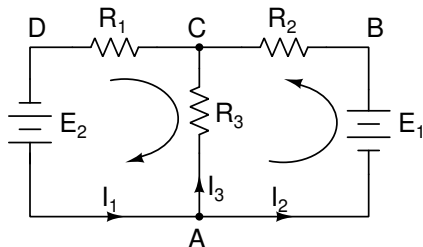

**our goal is to find  $I_1$ ,  $I_2$ , and  $I_3$**

We chose  $V_A = 0$  for node A.

It is our reference/grounded node

$$I_1 - I_2 - I_3 = 0 \quad (1)$$

We need 2 more **independent** equations.

For this we will go over 2 small loops as indicated by arrows.

$$V_{DC} + V_{CA} + V_{AD} = 0 \quad (2)$$


$$V_{AB} + V_{BC} + V_{CA} = 0 \quad (3)$$

Notice:

$$V_{AB} = +E_1, \quad V_{BC} = -R_2 \times I_2, \quad V_{CA} = +R_3 \times I_3,$$

$$V_{DC} = +R_1 \times I_1, \quad V_{AD} = -E_2.$$

## Example (continued)

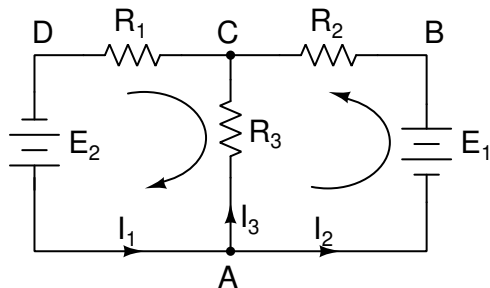

$$I_1 - I_2 - I_3 = 0$$

$$V_{DC} + V_{CA} + V_{AD} = 0$$

$$V_{AB} + V_{BC} + V_{CA} = 0$$

→

$$I_1 - I_2 - I_3 = 0$$

$$R_1 \times I_1 + R_3 \times I_3 - E_2 = 0$$

$$E_1 - R_2 \times I_2 + R_3 \times I_3 = 0$$

# Solving system of equation

So we need to find the unknowns  $I_1$ ,  $I_2$ , and  $I_3$  from the system of equations

$$\begin{aligned}I_1 - I_2 - I_3 &= 0 \\R_1 \times I_1 + R_3 \times I_3 - E_2 &= 0 \\E_1 - R_2 \times I_2 + R_3 \times I_3 &= 0\end{aligned}$$

Let's reshape above equations to the canonical linear algebra form (move terms without unknown variables to the right)

$$\begin{aligned}I_1 - I_2 - I_3 &= 0 \\R_1 \times I_1 + R_3 \times I_3 &= E_2 \\-R_2 \times I_2 + R_3 \times I_3 &= -E_1\end{aligned}$$
$$\begin{bmatrix} 1 & -1 & -1 \\ R_1 & 0 & R_3 \\ 0 & -R_2 & R_3 \end{bmatrix} \times \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ E_2 \\ -E_1 \end{bmatrix}$$

Equations form

Matrix form

# Computer assisted symbolic solvers: WolframAlpha (Mathematica)

$$\begin{aligned}I_1 - I_2 - I_3 &= 0 \\R_1 \times I_1 + R_3 \times I_3 - E_2 &= 0 \\E_1 - R_2 \times I_2 + R_3 \times I_3 &= 0\end{aligned}$$

With WolframAlpha we can input

```
Solve[
{I_1 - I_2 - I_3 == 0, R_1*I_1 + R_3*I_3 - E_2 == 0, E_1 - R_2*I_2 + R_3*I_3 == 0},
{I_1, I_2, I_3}
]
```

the results can be seen by following **WolframAlpha link**, which gives solution

$$\begin{aligned}I_1 &= (E_1 R_3 + E_2 (R_2 + R_3)) / (R_2 R_3 + R_1 (R_2 + R_3)) \\I_2 &= (E_2 R_3 + E_1 (R_1 + R_3)) / (R_2 R_3 + R_1 (R_2 + R_3)) \\I_3 &= (E_2 R_2 - E_1 R_1) / (R_2 R_3 + R_1 (R_2 + R_3))\end{aligned}$$

# Computer assisted symbolic solvers: Matlab

I would not recommend to use Matlab as symbolic solver, but it can be done

```
>> syms I_1 I_2 I_3 E_1 E_2 R_1 R_2 R_3; % declare symbols
>> S = solve( [I_1 - I_2 - I_3 == 0,
             R_1*I_1 + R_3*I_3 - E_2 == 0,
             E_1 - R_2*I_2 + R_3*I_3 == 0],
            [I_1, I_2, I_3]);
>> S.I_1
ans=(E_1*R_3 + E_2*R_2 + E_2*R_3)/(R_1*R_2 + R_1*R_3 + R_2*R_3)
>> S.I_2
ans=(E_1*R_1 + E_1*R_3 + E_2*R_3)/(R_1*R_2 + R_1*R_3 + R_2*R_3)
>> S.I_3
ans=-(E_1*R_1 - E_2*R_2)/(R_1*R_2 + R_1*R_3 + R_2*R_3)
```

# Linear algebra solution for system of equations

Let's look at the Matrix form

$$\begin{bmatrix} 1 & -1 & -1 \\ R_1 & 0 & R_3 \\ 0 & -R_2 & R_3 \end{bmatrix} \times \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ E_2 \\ -E_1 \end{bmatrix}$$

Short notation  $A \times I = B$ , where  $I$  is a vector of unknown currents.  
Currents can be found as  $I = \text{inv}(A) * B$



# Computer assisted numerical solvers: Matlab

Matlab is better suited for a numerical solutions, we will lose a general solution but a specific one is easy. In Matlab this is done as

```
>> R_1 = 10; R_2= 5; R_3= 15; E_1=10; E_2=15;
```

```
>> A = [ 1 -1 -1; R_1 0 R_3; 0 -R_2 R_2]
```

```
A =
```

```
    1    -1    -1
   10     0    15
    0    -5     5
```

```
>> B = [ 0; E_2; -E_1]
```

```
B =
```

```
    0
   15
  -10
```

```
>> I=inv(A)*B
```

```
I =
```

```
    1.7143
    1.8571
   -0.1429
```

Note that  $I_3 = -0.1429$ , i.e. it ends up negative. No need to worry, this means that direction of  $I_3$  is opposite to the one which we selected in our schematic.

# Computer assisted symbolic solvers: Maple

`solve({I1 - I2 - I3 = 0, E1 - R2·I2 + R3·I3 = 0, R1·I1 + R3·I3 - E2 = 0}, [I1, I2, I3])`

$$\left[ \left[ I1 = \frac{R3 E1 + R3 E2 + R2 E2}{R3 R1 + R1 R2 + R3 R2}, I2 = \frac{R3 E1 + R3 E2 + R1 E1}{R3 R1 + R1 R2 + R3 R2}, I3 = -\frac{R1 E1 - R2 E2}{R3 R1 + R1 R2 + R3 R2} \right] \right]$$


(1)

# Thévenin's and Norton's equivalent circuit theorems

Any combination of voltage sources, current sources and resistors with two terminals is electrically equivalent

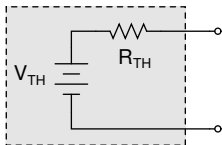
## Thévenin's theorem

to a single voltage source  $V_{TH}$  and a single series resistor  $R_{TH}$  connected in series.


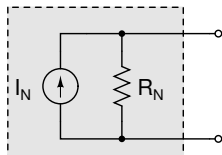
## Norton's theorem

to a single current source  $I_N$  and a single series resistor  $R_N$  connected in parallel.



Note above circuits are equivalent to each other when

$$R_{TH} = R_N \text{ and } I_N = V_{TH}/R_{TH}$$