
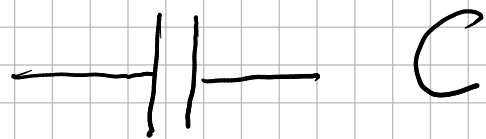


# Reactive elements: capacitors and inductors

## Capacitors

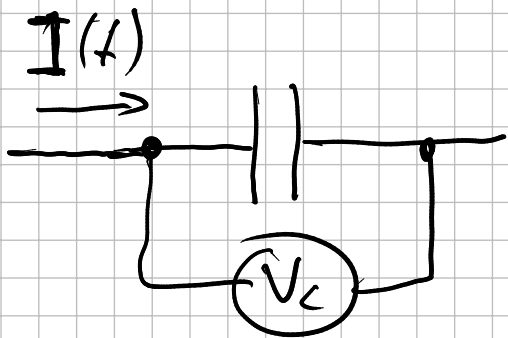


$$Z_C = \frac{1}{i\omega C}$$




$$V_C = \frac{q}{C} = \frac{\int_{-\infty}^t I(t') dt'}{C}$$

capacitance  $\uparrow$

## Inductors

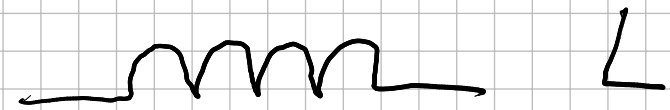


$$Z_L = i\omega L$$

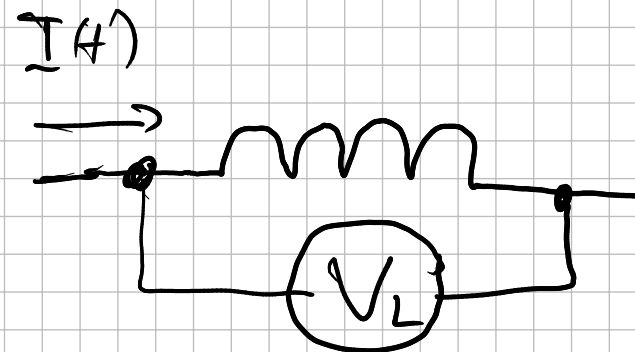

$$V_L = L \cdot \frac{dI(t)}{dt}$$


induction  $\uparrow$

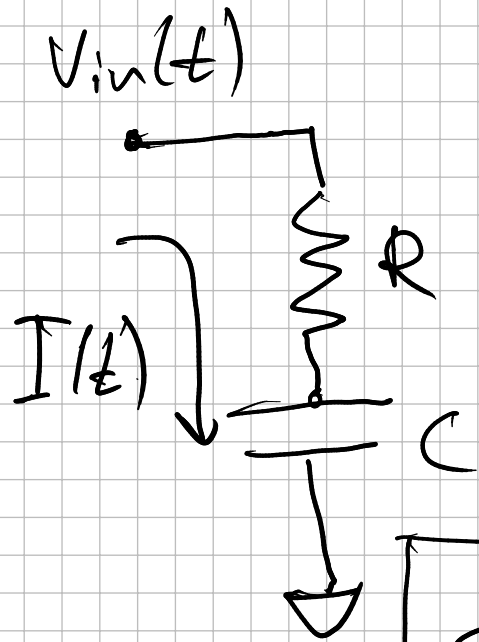

$$\begin{aligned}
 V_{in} &= V_R + V_C \\
 &= I \cdot R + \frac{q(t)}{C} \\
 &= I \cdot R + \frac{\int I(t') dt'}{C}
 \end{aligned}$$

$$\frac{dV_{in}}{dt} = \frac{dI(t)}{dt} \cdot R + I(t) \cdot \frac{1}{C}$$

Example: Charging capacitor

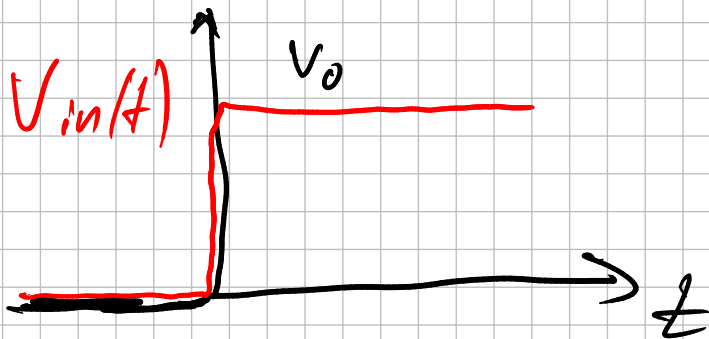

$$\frac{dV_{in}}{dt} = 0 \quad (\text{except } t=0)$$

$$0 = \frac{dI}{dt} R + I \frac{1}{C} \Rightarrow \frac{dI}{I} = - \frac{dt}{R \cdot C}$$

$$d(\ln I) = -d\left(\frac{t}{RC}\right) \Rightarrow \ln I = -\frac{t}{RC} + \text{Const}$$

" "  
 $\ln I_0$

$$\ln \frac{I}{I_0} = -\frac{t}{RC} \Rightarrow \boxed{I(t) = I_0 e^{-t/RC}}$$

$$V_C = \frac{1}{C} \int I(t) dt = \frac{1}{C} \underbrace{I_0 (-RC)}_{= I(t)} \cdot \underbrace{e^{-t/RC}}_{= I(t)} + V_{\text{const}}$$

$$\boxed{V_C(t) = -R I(t) + V_{\text{const}}}$$

Boundary conditions:

$$V_{\text{in}}(t = \infty) = R \underbrace{I(t = \infty)}_{0''} = R \underbrace{I(t = \infty)}_{0''} + V_{\text{const}}$$

$$V_{\text{const}} = V_0$$

What about  $I_0$  - ?  $\leq 0, t=0$


Recall  
at  $t=0$

$$V_{in} = I(t)R + \frac{q(t)}{C}$$
$$V_{in} = V_0 = \underbrace{I_0}_{I, t=0} \cdot R$$



$$I_0 = \frac{V_0}{R}$$

$\Rightarrow$  Capacitor  
is equivalent  
to a short (" $R_c = 0$ ")  
for abruptly changing  
signals.
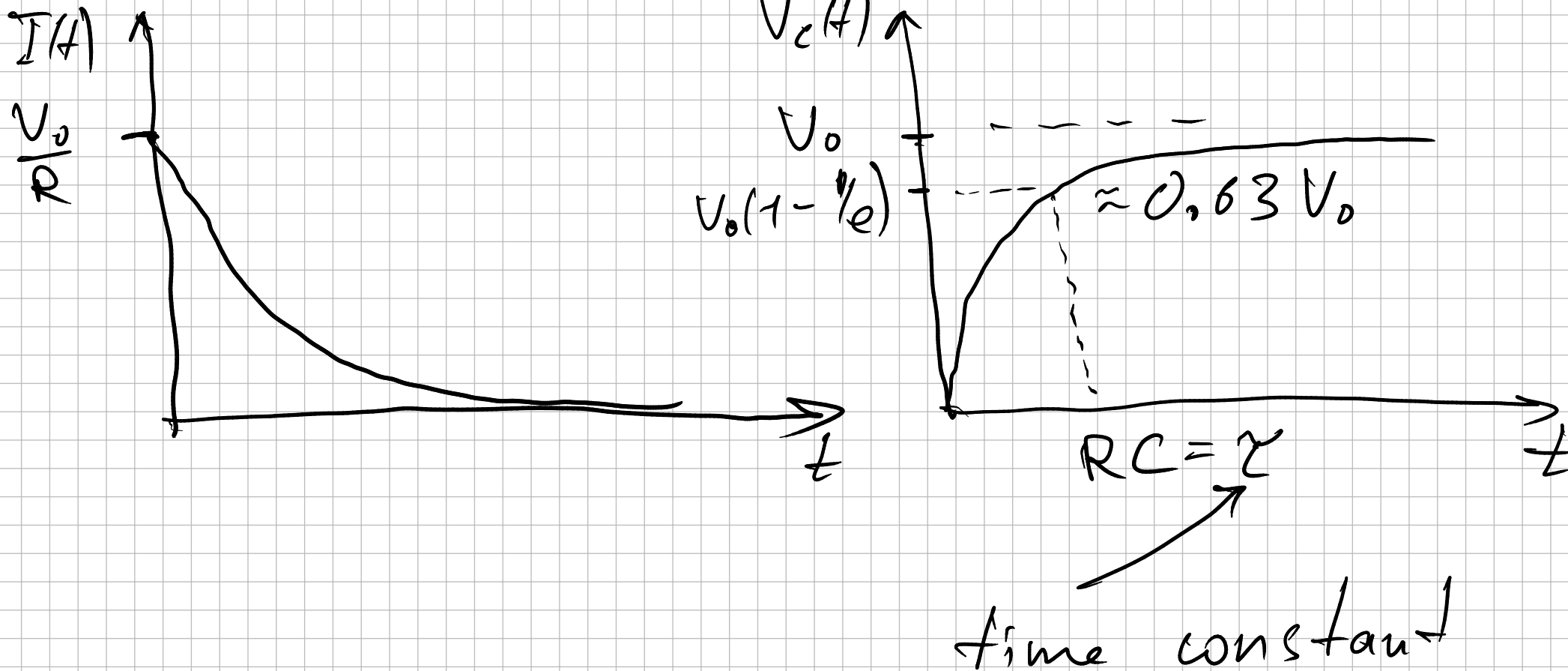
$$I(t) = \frac{V_0}{R} e^{-t/RC}, \quad V_c = V_0 (1 - e^{-t/RC})$$



RC driven by periodic square signals.

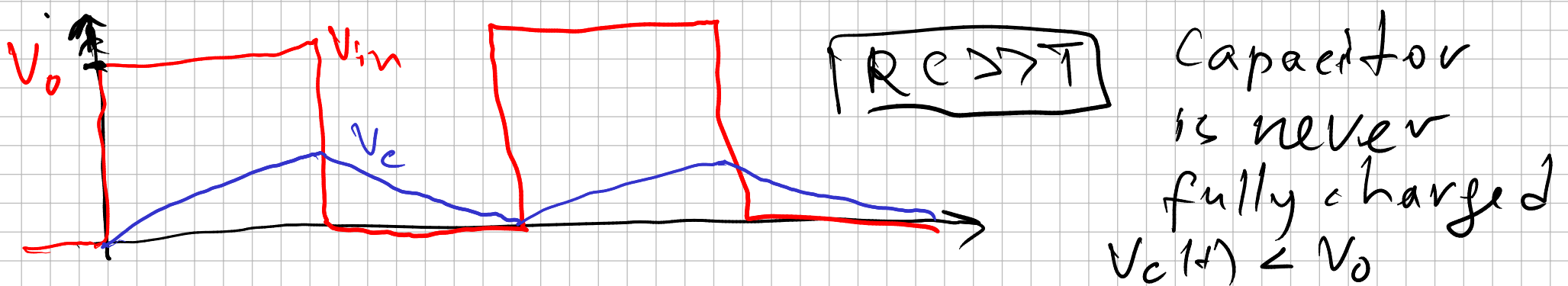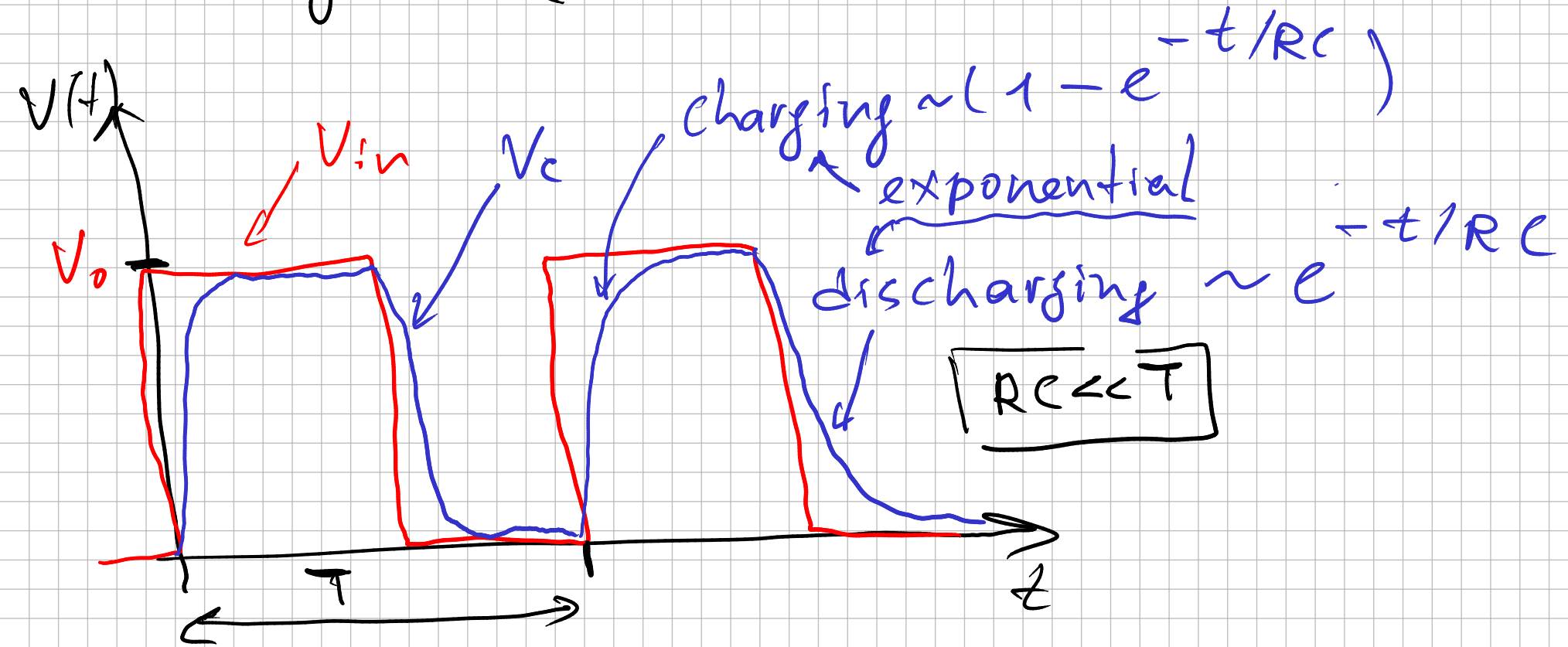

# Complex impedance



$$V_{in}(t) = I(t)R + \frac{1}{C} \int I(t) dt$$

This is hard

What if our input is in the form

$$V_{in}(t) = V_{\omega} \cdot e^{i\omega t}$$

We will seek solution in the form  $I(t) = I_{\omega} e^{i\omega t}$


$$\cancel{V_{\omega} e^{i\omega t}} = \cancel{I_{\omega} e^{i\omega t}} R + \frac{1}{C} \frac{I_{\omega}}{i\omega} \cancel{e^{i\omega t}}$$

$$V_{\omega} = I_{\omega} \boxed{R} + \boxed{\frac{1}{i\omega C}} I_{\omega} \Rightarrow V_{\omega} = (Z_R + Z_C) I_{\omega}$$

$\underbrace{\hspace{1.5cm}}_{Z_R} \quad \underbrace{\hspace{1.5cm}}_{Z_C}$

$$\boxed{Z_C = \frac{1}{i\omega C}}$$

# Simple network analysis

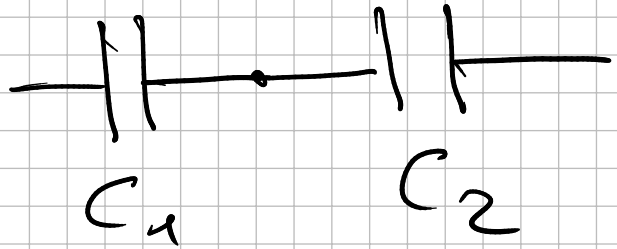

$$Z_{C_1} = \frac{1}{i\omega C_1}$$

$$Z_{C_2} = \frac{1}{i\omega C_2}$$

Impedance follows the same rules as resistors.

$$Z_{\text{total}} = Z_{C_1} + Z_{C_2} \quad (\text{serial connection})$$

$$= \frac{1}{i\omega C_1} + \frac{1}{i\omega C_2} = \frac{1}{i\omega} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) =$$

$$= \frac{1}{i\omega C_T} \Rightarrow \boxed{C_T = \frac{C_1 \cdot C_2}{C_1 + C_2}}$$