
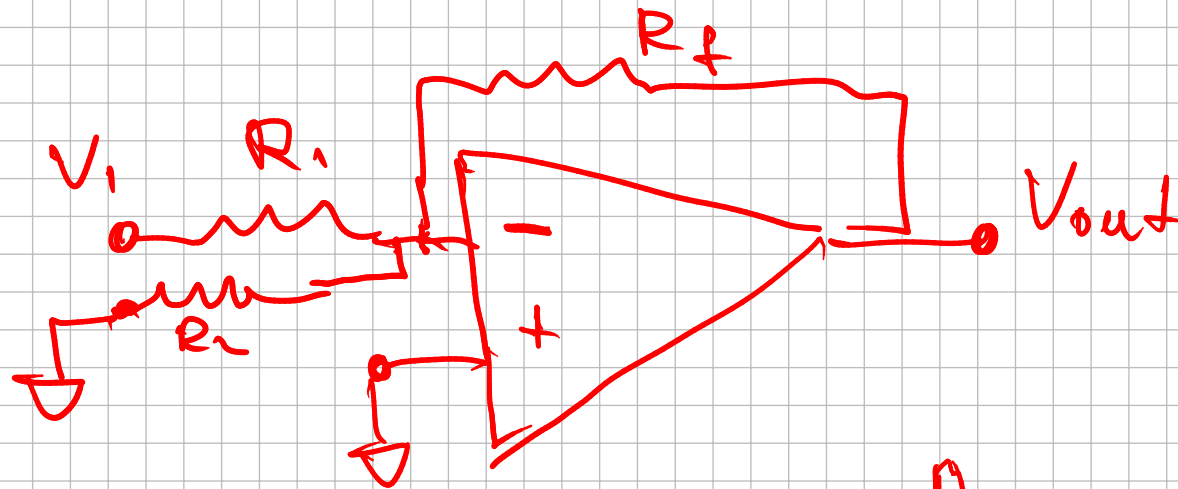


Variable bandwidth amplifier

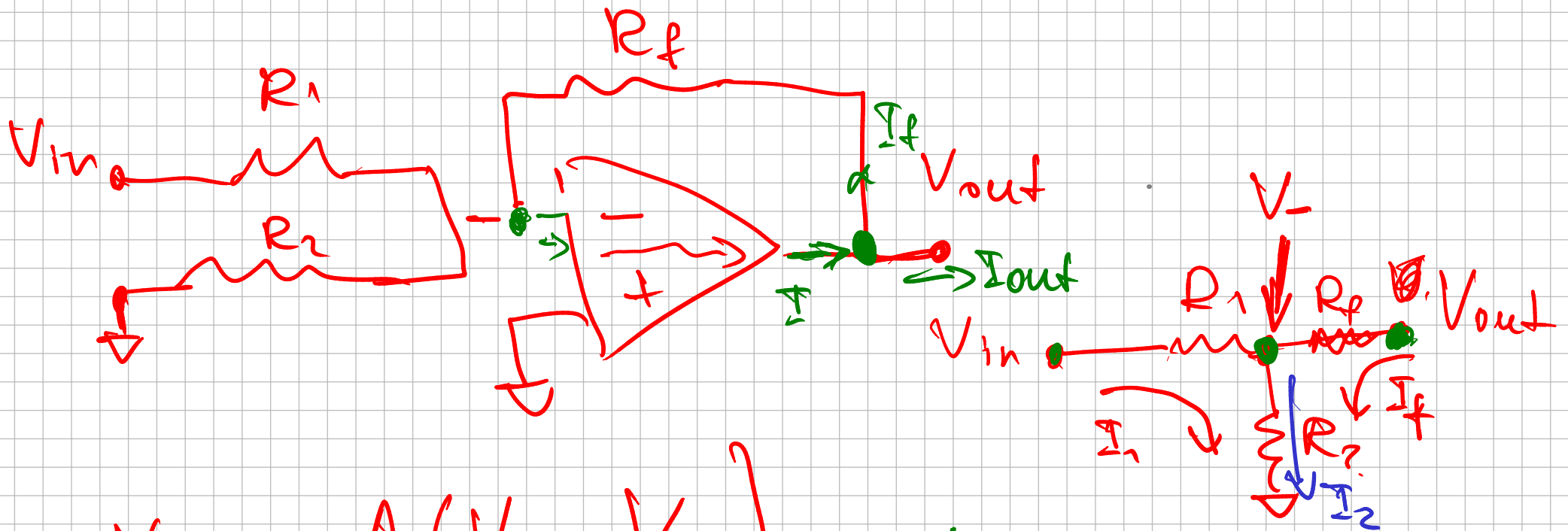

$$V_{out} = -\frac{R_f}{R_i} V_i + V_2 \left(1 + \frac{R_f}{R_{i||2}} \right)$$

↑ True only if $A \rightarrow \infty$




$$V_{out} \approx A(V_{+} - V_{-})$$

$$I_1 + I_f = I_2$$

$$V_{-} = V_{in} - I_1 R_1$$

$$\left\{ \begin{array}{l} V_{out} = A_0 (-V_{-}) \quad (1) \\ V_{-} = V_{in} - I_1 R_1 \quad (2) \\ I_1 + I_f = I_2 = \frac{V_{-}}{R_2} \quad (3) \Rightarrow \\ V_{-} = V_{out} - I_f R_f \quad (4) \end{array} \right.$$

$G_{final}(f)$

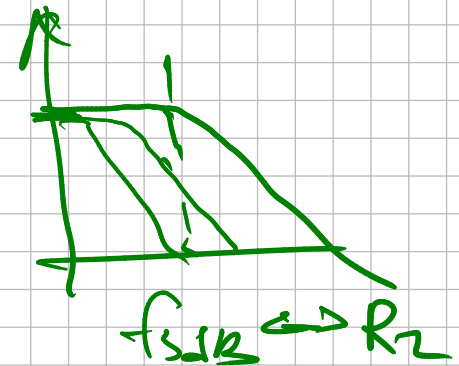

eq. 1:

$$I_1 = \frac{V_{in} - V_-}{R_1}$$

eq. 4:

$$I_f = \frac{V_{out} - V_-}{R_f}$$

eq. 3:

$$I_1 + I_f = \frac{V_{in} - V_-}{R_1} + \frac{V_{out} - V_-}{R_f} = \frac{V_-}{R_2}$$


$$\boxed{V_-} \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_f} \right) = \frac{V_{in}}{R_1} + \frac{V_{out}}{R_f}$$

eq. 1

$$V_{out} = -A_o V_- = - \frac{A_o \left(\frac{V_{in}}{R_1} + \frac{V_{out}}{R_f} \right)}{\left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_f} \right)}$$

$$V_{out} = -A \left(V_{in} \frac{R_f}{R_1} + V_{out} \right) \frac{1}{\left(\frac{1}{R_2} + \frac{1}{R_f} + \frac{1}{R_1} \right) R_f}$$
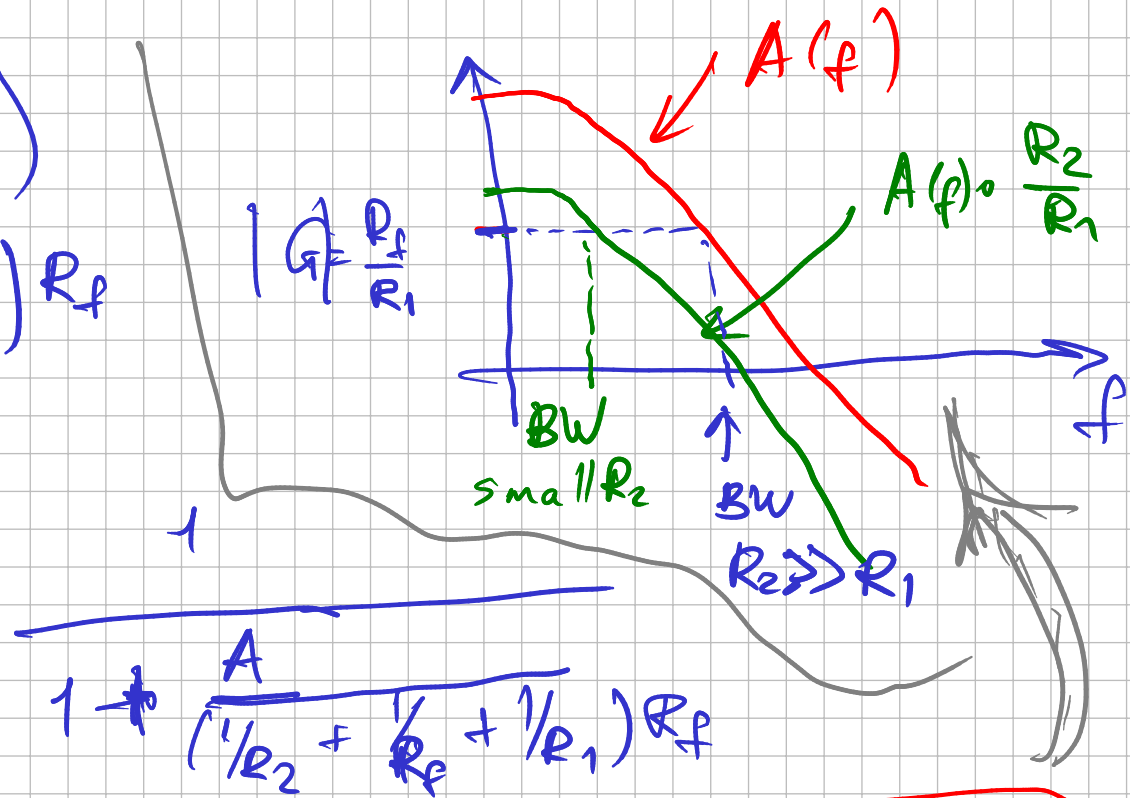
$$V_{out} = \frac{-A_0 \frac{R_f}{R_1} \cdot V_{in}}{\left(\frac{1}{R_2} + \frac{1}{R_f} + \frac{1}{R_1} \right) R_f}$$



$$1 + \frac{A}{\left(\frac{1}{R_2} + \frac{1}{R_f} + \frac{1}{R_1} \right) R_f}$$

$$V_{out} = \frac{-A_0 \frac{R_f}{R_1} V_{in}}{R_f \left(\frac{1}{R_2} + \frac{1}{R_f} + \frac{1}{R_1} \right) + A}$$

$A \rightarrow \infty$

$$G_{final} = \frac{R_f}{R_1}$$

$\frac{R_f}{R_2} \rightarrow 0$
 $\frac{R_f}{R_2} \rightarrow A(f)$

$$G_{final} = \left(A_0 \frac{R_2}{R_f} \right) \cdot \frac{R_f}{R_1} = -A \frac{R_2}{R_1}$$