
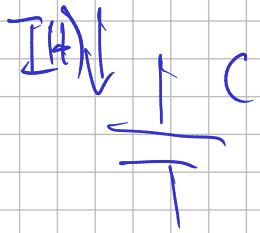


Integrator and differentiator

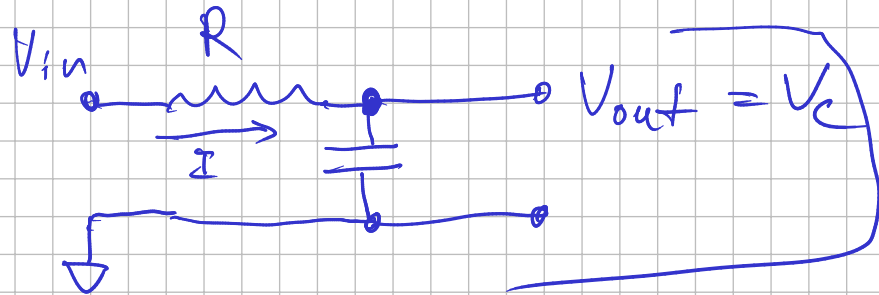

$$Q(t) = \int_{-\infty}^t I(t') dt'$$



$$I_{in} = \frac{V_{in} - V_c}{R} \approx \frac{V_{in}}{R}, \text{ if } \underline{\underline{V_c \approx 0}}$$

$$V_{out} = V_c = \int \frac{I dt}{C} \approx \int \frac{V_{in}(t)}{R \cdot C} dt$$

$$V_{out}(t) \sim \int_{-\infty}^t V_{in}(t') dt'$$

$$f(t) = \int_{-\infty}^{\infty} \boxed{f_{\omega}} \cdot e^{i\omega t} d\omega$$

$$F(t) = \int_{-\infty}^t f(t') dt' = \int_{-\infty}^t \left[\int_{-\infty}^{\infty} f_{\omega} e^{i\omega t'} d\omega \right] dt' = \int_{-\infty}^{\infty} d\omega f_{\omega} \int_{-\infty}^t e^{i\omega t'} dt'$$


$$\approx \int_{-\infty}^{\infty} d\omega f_{\omega} \frac{e^{i\omega t}}{i\omega}$$

$$= \int_{-\infty}^{\infty} \boxed{\frac{f_{\omega}}{i\omega}} e^{i\omega t} d\omega$$

$$F(t) \approx \int_{-\infty}^{\infty} \overset{\updownarrow}{F_{\omega}} e^{i\omega t} d\omega$$

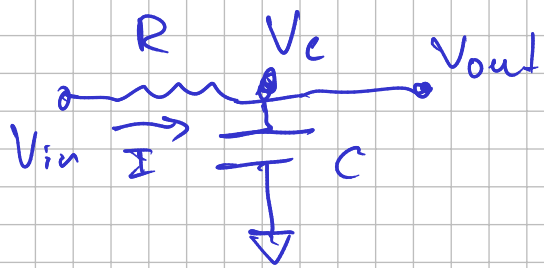
$$\boxed{F_{\omega} \approx \frac{f_{\omega}}{i\omega}}$$





$$V_{out}(\omega) = \frac{1}{R + \frac{1}{i\omega C}} \cdot \frac{1}{i\omega C} \cdot V_{in}(\omega)$$

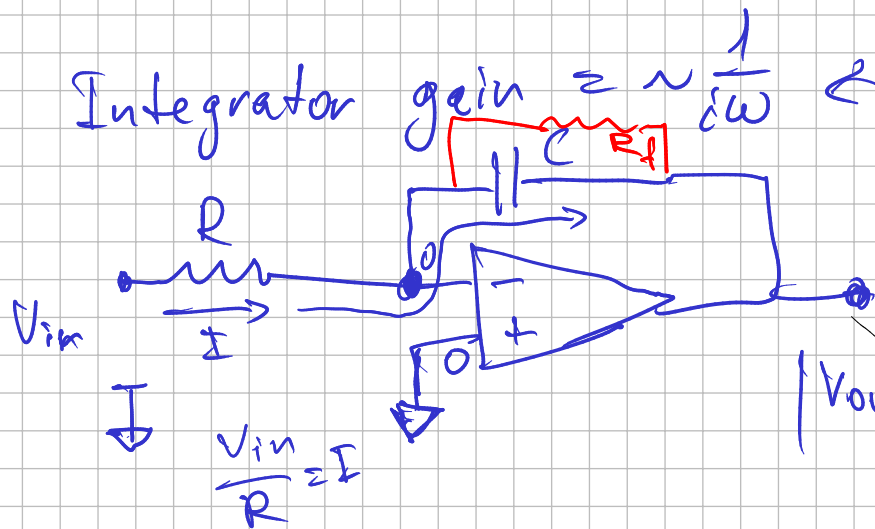
$$= \boxed{\frac{1}{1 + i\omega RC}} V_{in}(\omega)$$



$$G(\omega) \approx -\frac{Z_f}{Z_{in}} = -\frac{1}{i\omega C R}$$

$$|V_{out}| \approx \frac{1}{\omega(RC)}$$

$$G(0) \approx -\frac{R_f}{R}$$

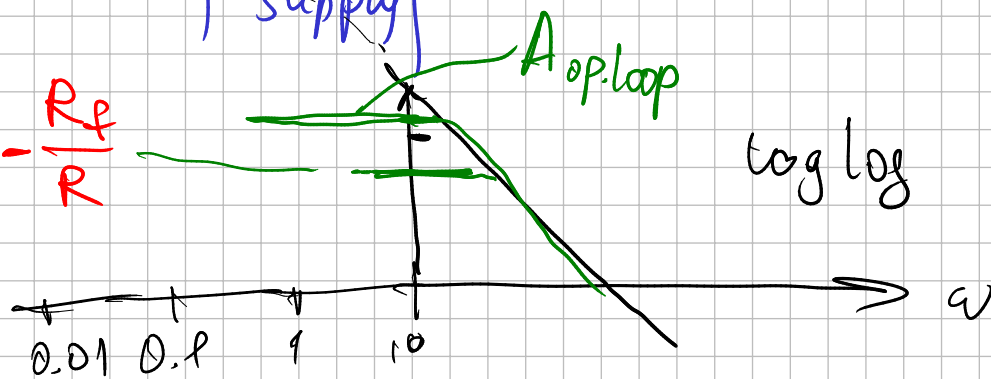


differentiator

$$V_{out} \sim \frac{dV_{in}(t)}{dt}$$

$$F(\omega) = \frac{d}{dt} f(t) = \frac{d}{dt} \int_{-\infty}^{\infty} f(\omega) e^{i\omega t} d\omega = \int_{-\infty}^{\infty} f(\omega) \left(\frac{d}{dt} e^{i\omega t} \right) d\omega$$
$$= \int_{-\infty}^{\infty} f(\omega) i\omega e^{i\omega t} d\omega$$

$F(\omega) = i\omega f(\omega)$




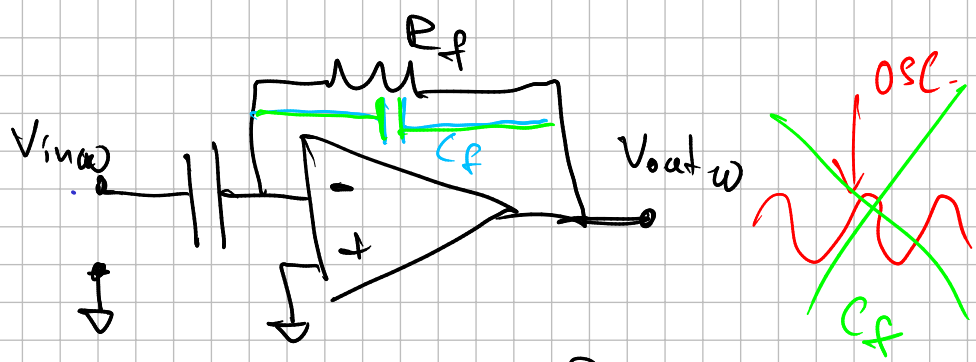


$$G = -\frac{Z_f}{Z_{in}} = -\frac{R_f}{1/j\omega C}$$

$$= -R_f C \cdot j\omega$$

V_{in}

V_{out}

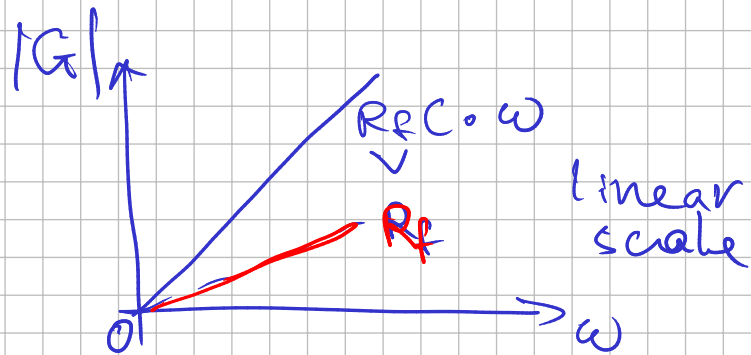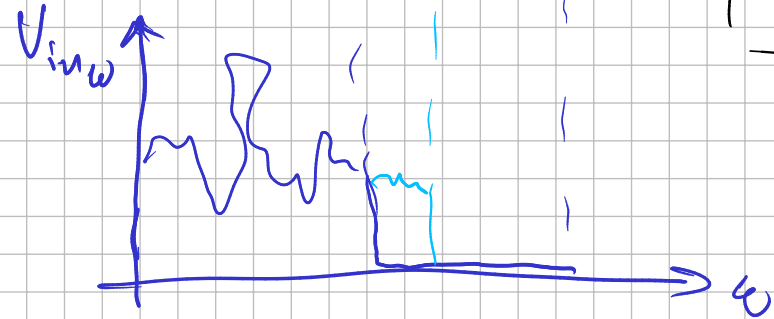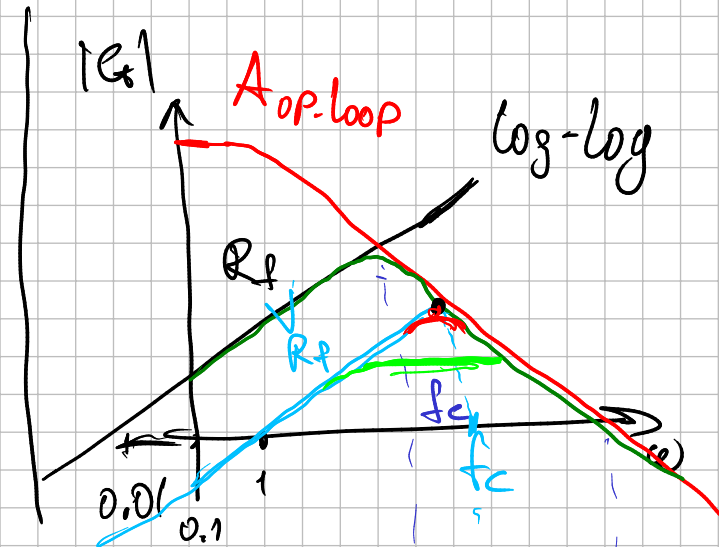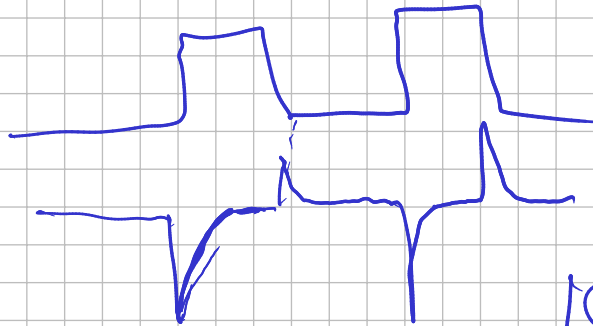

$f_e = ?$

$$GBW = \text{const}$$

$$R_f C \cdot f_c = \text{const}$$

$$f_c = \frac{GBW}{R_f C}$$