
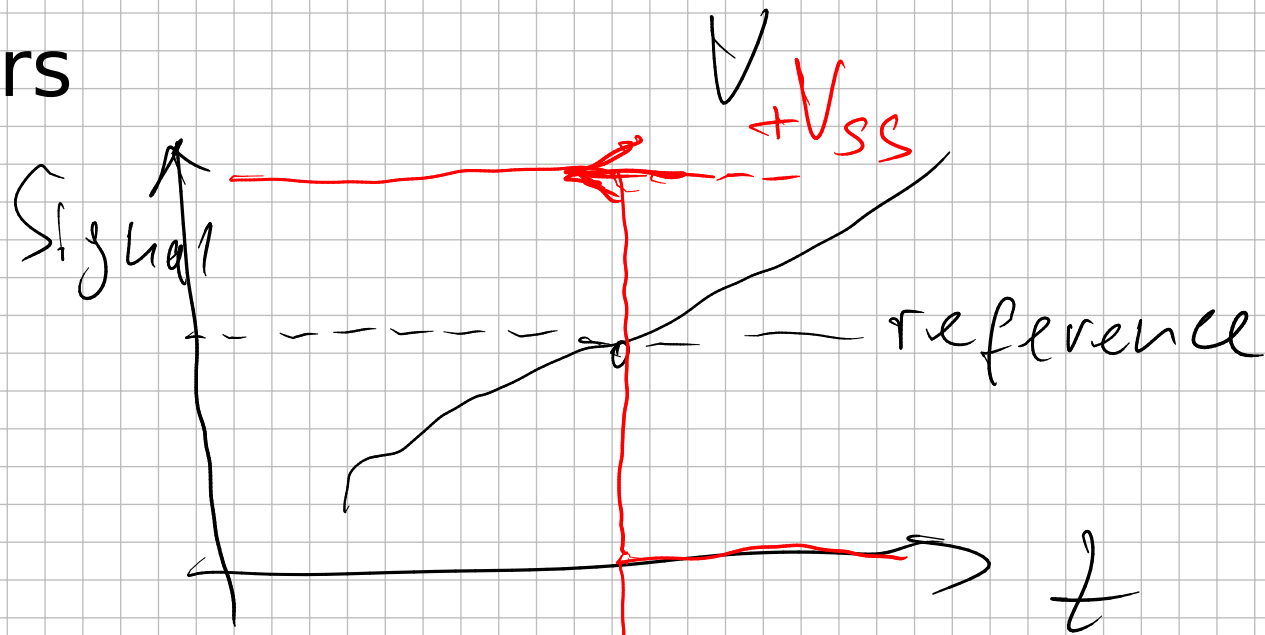


Comparators

$$V_{out} \approx A (V_+ - V_-)$$

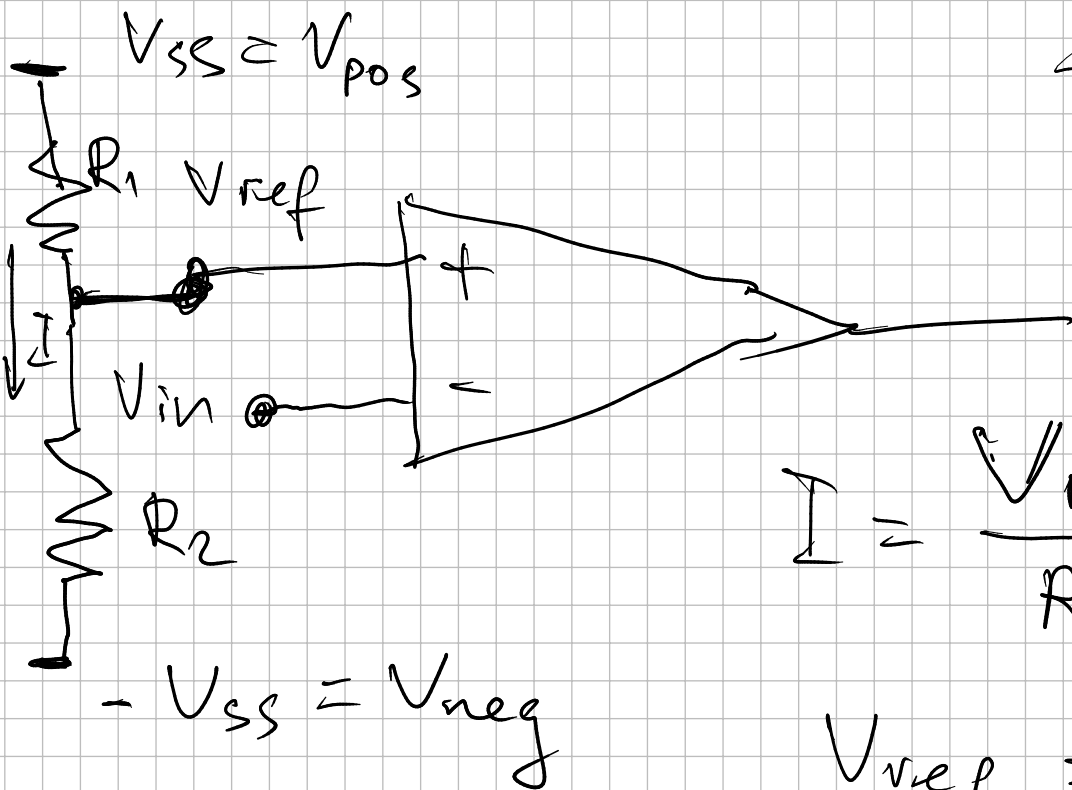


$$I = \frac{V_{pos} - V_{neg}}{R_1 + R_2}$$


$$I \approx 1 \mu A$$

$$V_{ref} = I \cdot R_2 + V_{neg} \approx V_{pos} - I R_1$$

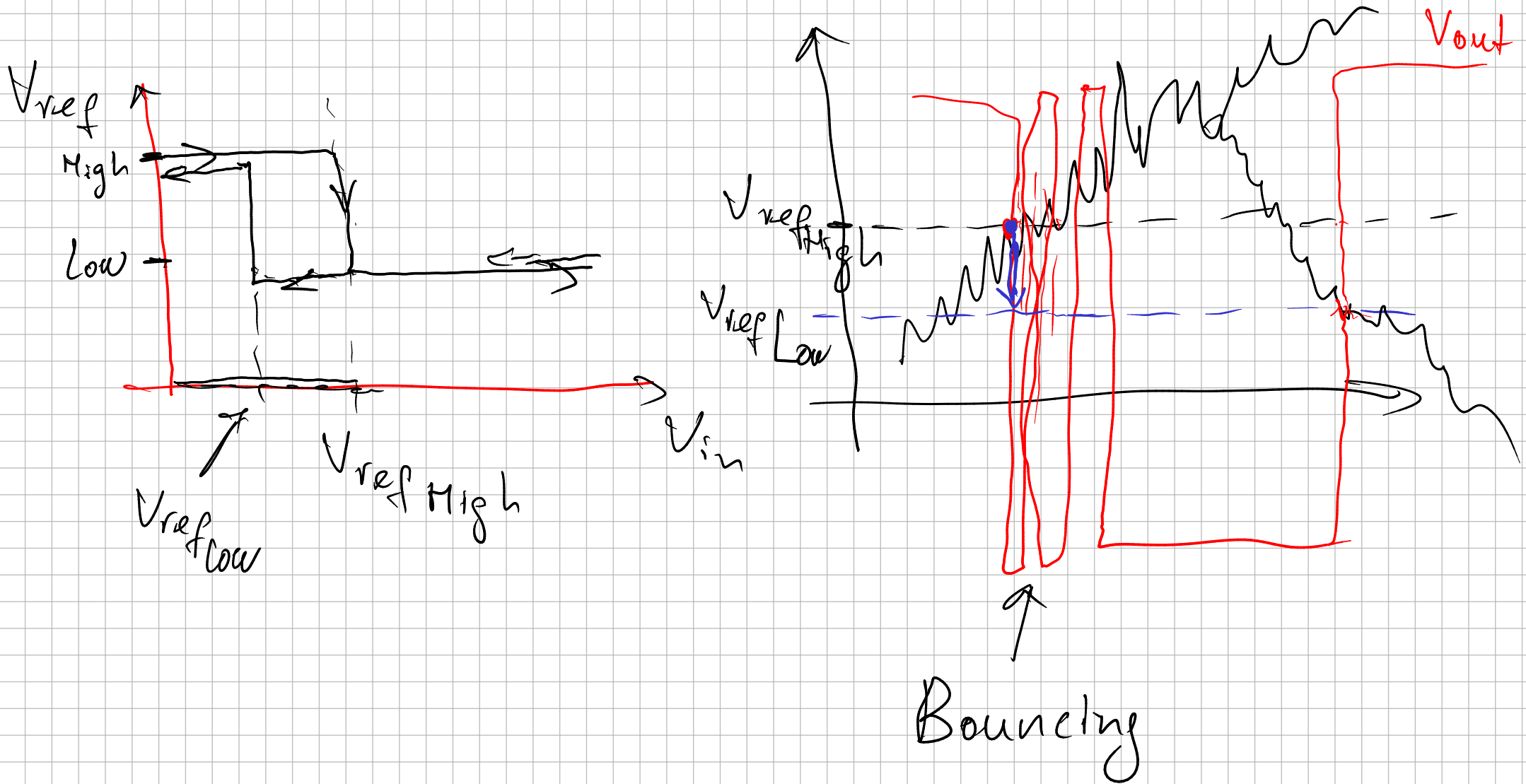
Comparator with hysteresis: Schmitt trigger



De bouncing circuit

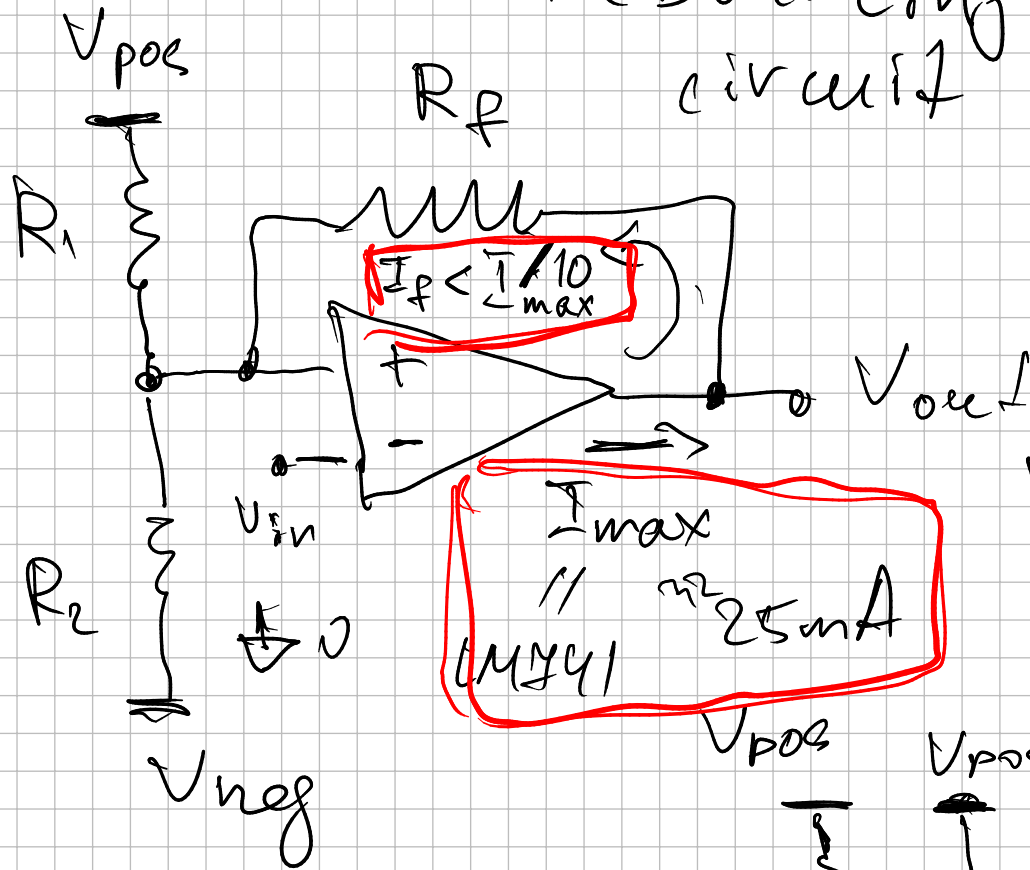


$V_{in} < V_{ref}$

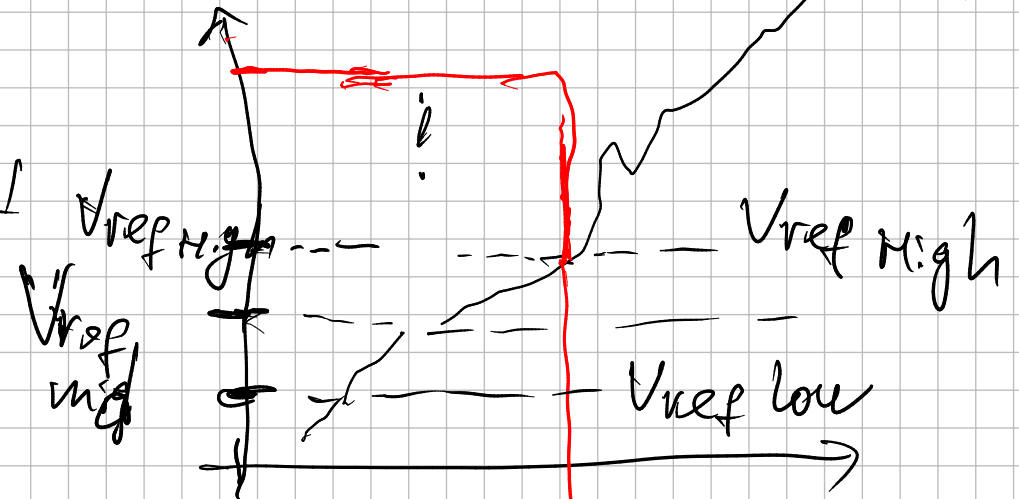

$V_{in} < V_{ref}$

"typical"

$R_f > 10 (R_1 \text{ or } R_2)$
 weak

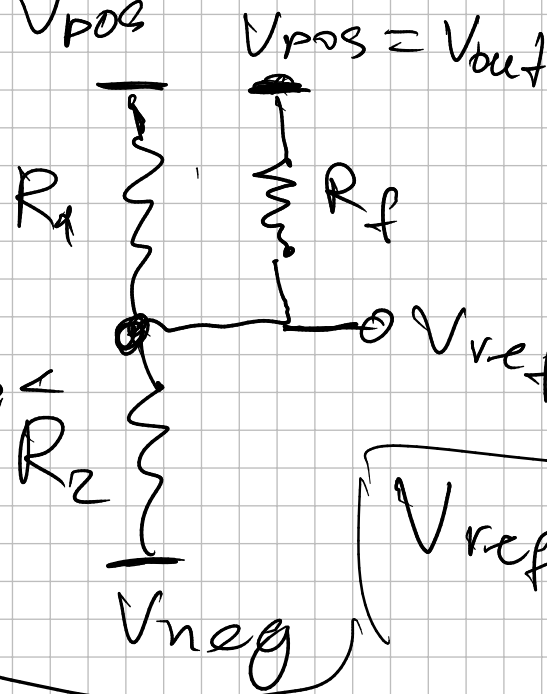


$$V_{ref} = \frac{V_{pos} - V_{neg}}{R_2 + R_1 \parallel R_f} \cdot R_2 + V_{neg}$$

$V_{ref\ high} - V_{ref\ low} \approx 1V$
 $< V_{pos}$


$$V_{in} > V_{ref}$$

$$V_{out} = V_{neg}$$

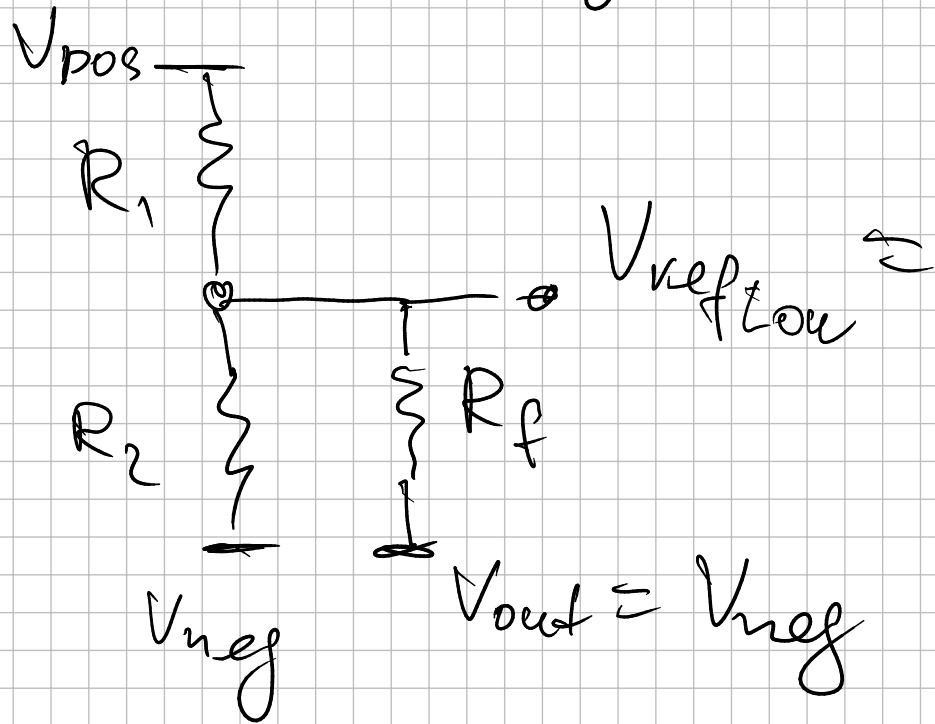


$$V_{ref\ low} = \frac{V_{pos} - V_{neg}}{R_1 + R_2 \parallel R_f} \cdot (R_2 \parallel R_f) + V_{neg}$$


Simple Comparator = 0 or High

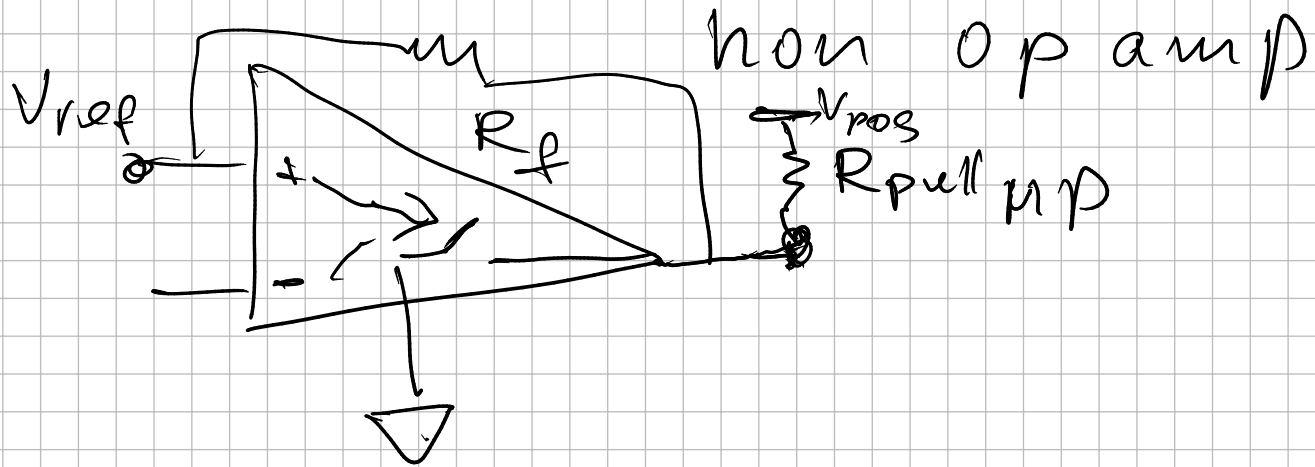

Relaxation oscillator

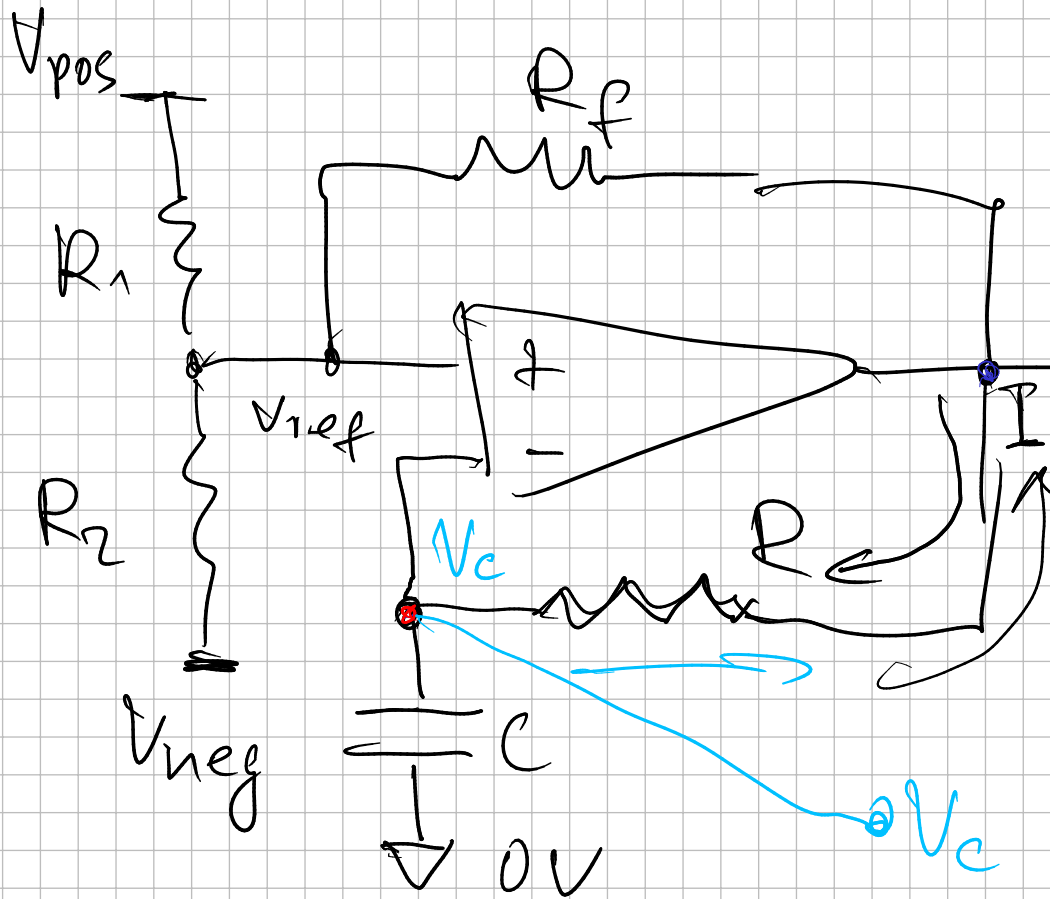

$V_{ref\ high}$

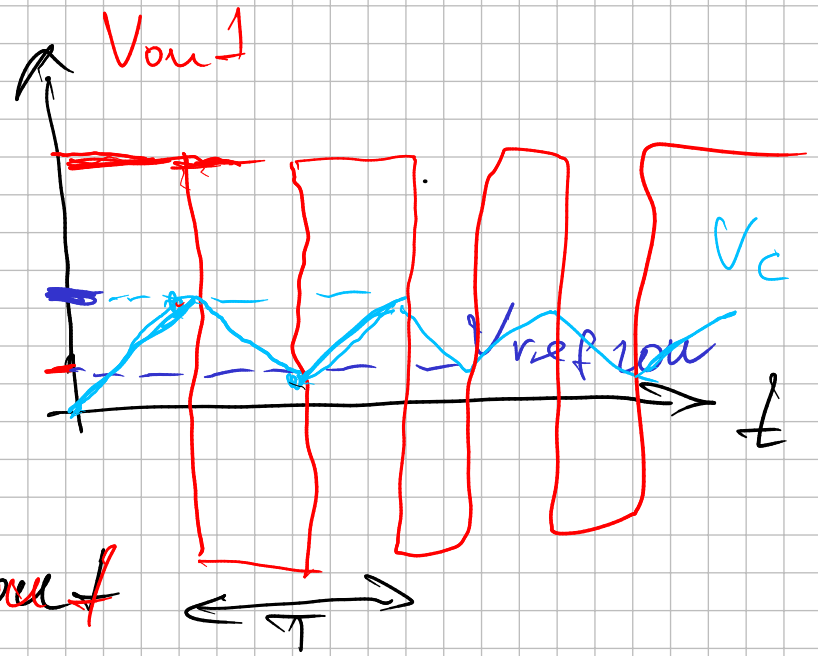

$t, V_{out} = V_{pos}$

Period of oscillations

$$T = 2RC \cdot \ln\left(\frac{V_{ref\ high} - V_{neg}}{V_{ref\ low} - V_{neg}}\right)$$