
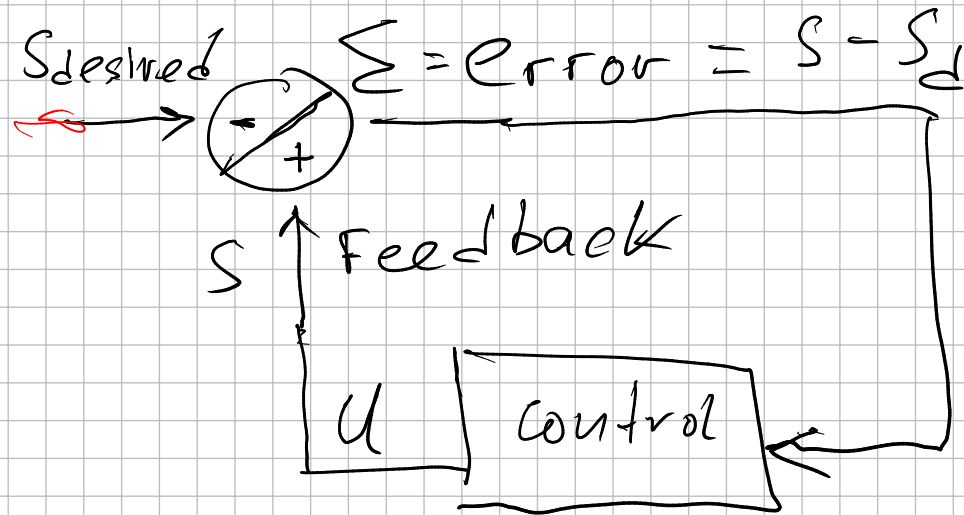


Feedback

Previous view

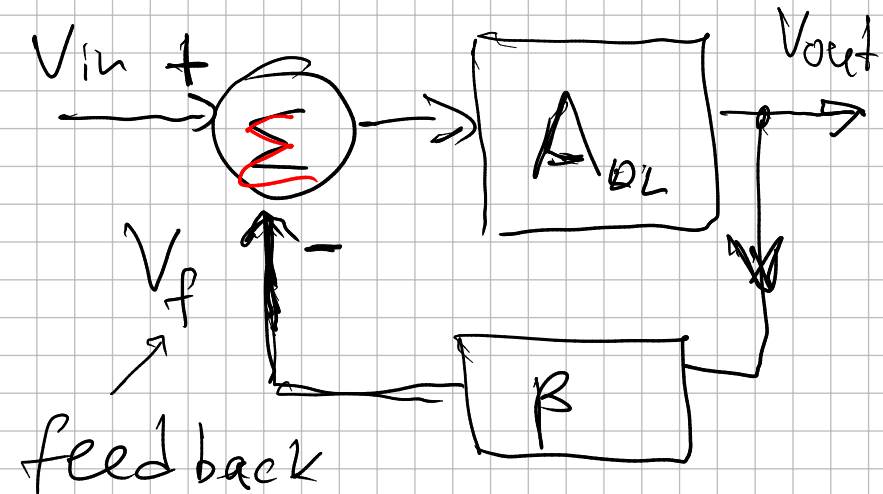

Electrical engineers notation



$$V_f = \beta \cdot V_{out}$$

β - feedback gain

A - open loop gain

$$V_{out} = (V_{in} - V_f) \cdot A_{OL}$$

\nearrow
 $\beta \cdot V_{out}$

$$V_{out} = (V_{in} - \beta V_{out}) \cdot A_{OL}$$


$$\boxed{\frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}}} = G = A_{CL}$$

\nearrow close loop

$\beta A_{OL} < 0$, positive gain

$\beta A_{OL} > 0$, negative feedback

$\beta A_{OL} = -1$ Danger point

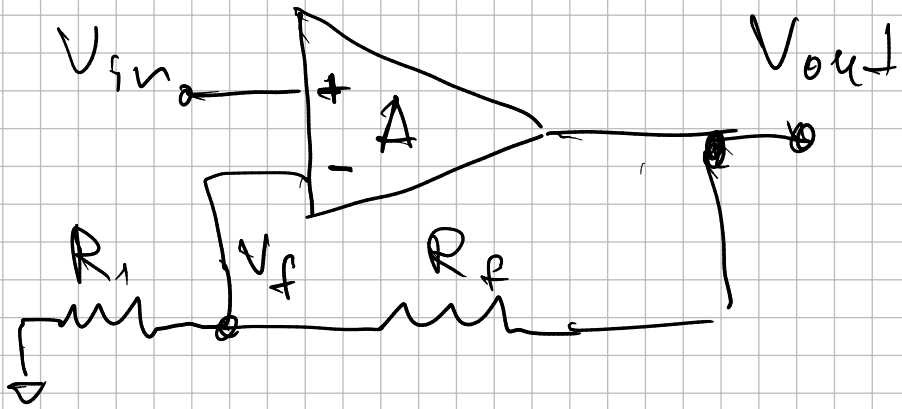

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + \frac{R_1}{R_1 + R_f} \circ A}$$


$$V_f = V_{out} \cdot \left(\frac{R_f}{R_1 + R_f} \right) = \beta$$

$$V_{out} = \frac{A}{1 + \beta A} \circ \underline{V_{in}}$$



$$\xrightarrow{A \rightarrow \infty}$$

$$\frac{A}{\beta \circ A} = \frac{1}{\beta} = \frac{R_1 + R_f}{R_1}$$

Buffers

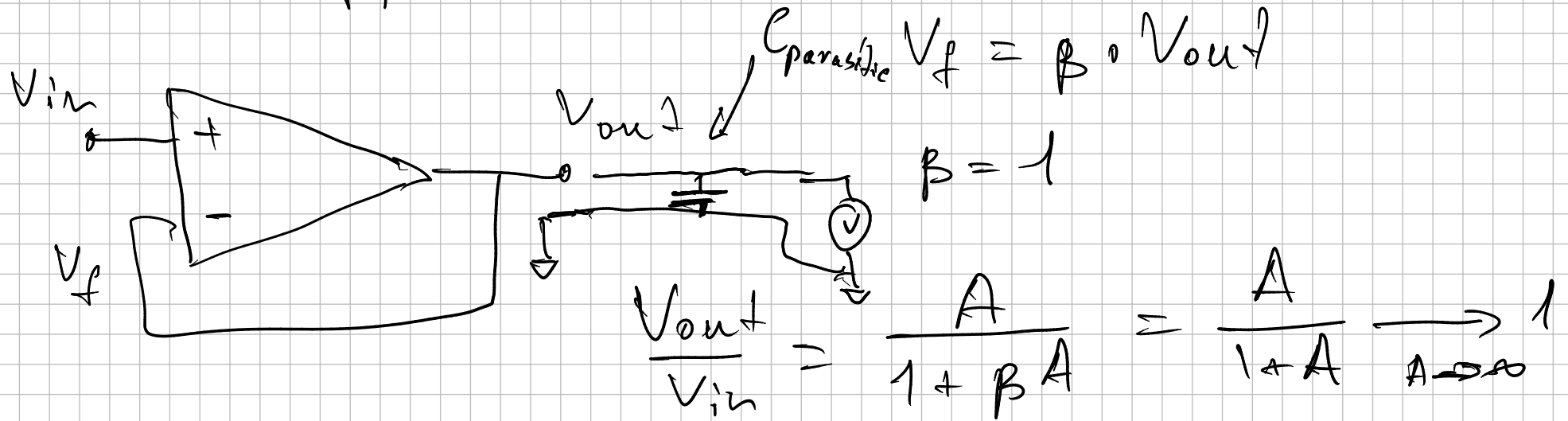

Real Op Amps have output resistance

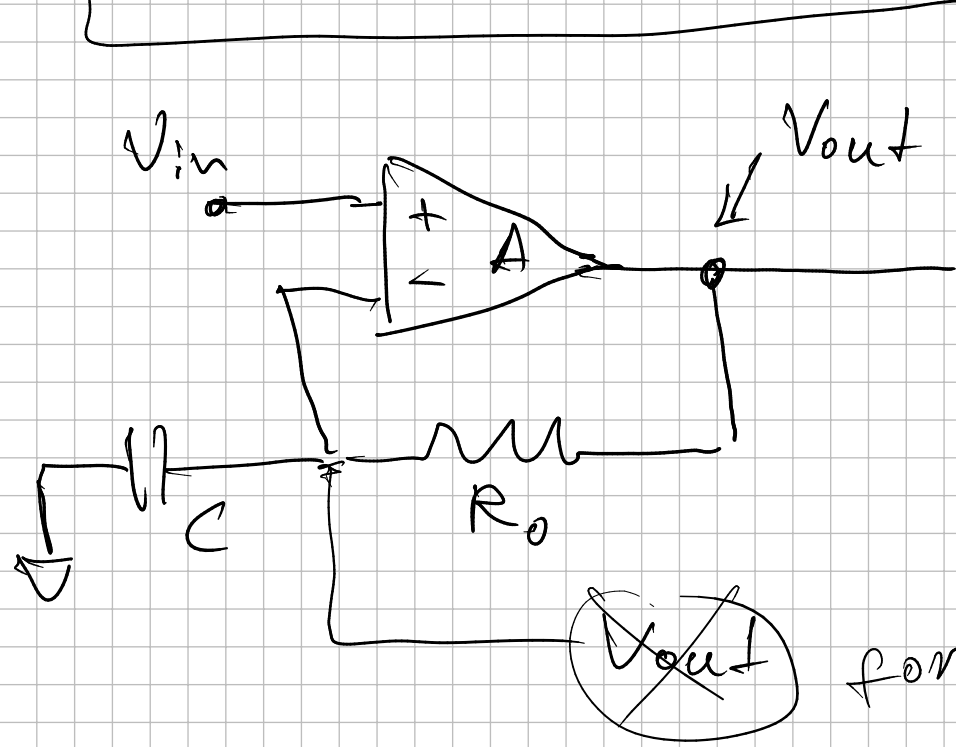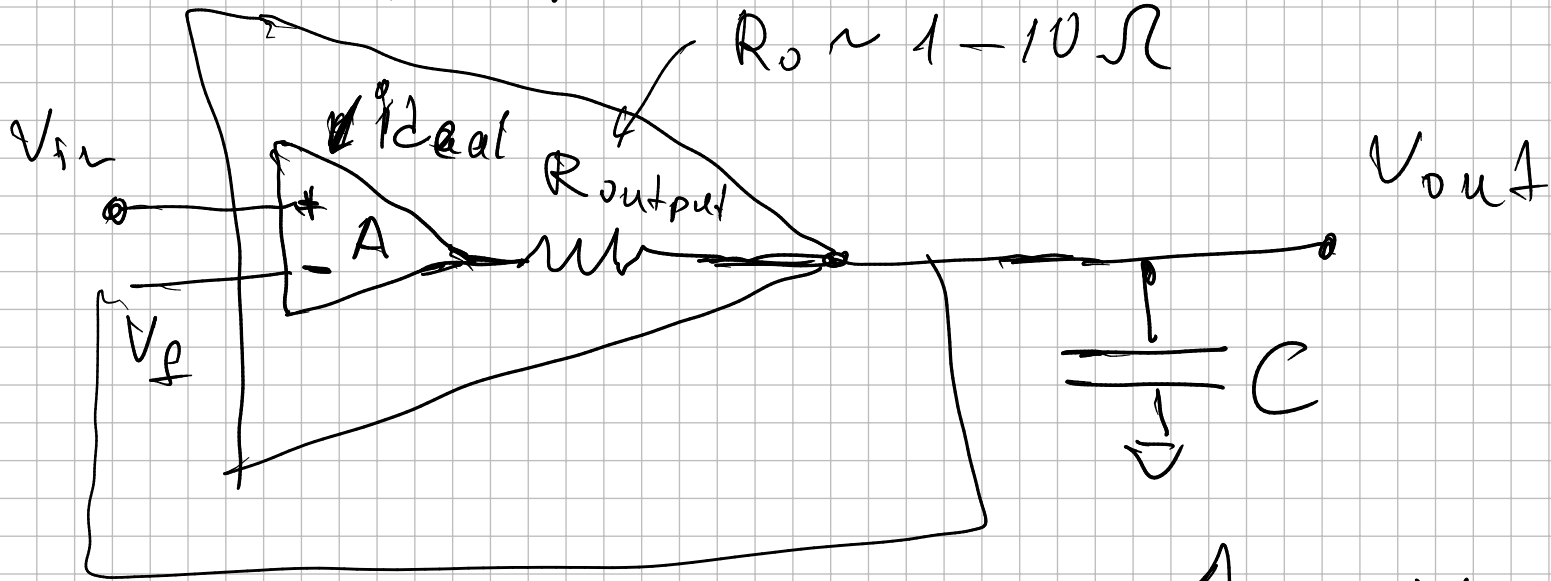

$$V_{out} = \frac{A}{1+BA} \cdot V_{in}$$


$$B = \frac{Z_c}{R_o + Z_c} = \frac{1}{1 + i \frac{\omega}{\omega_{3dB}}}$$

~~V_{out}~~ for the circuit.

Stability condition

$$B \cdot A > 1 \iff \text{negative feedback}$$

$$B \cdot A \neq -1$$

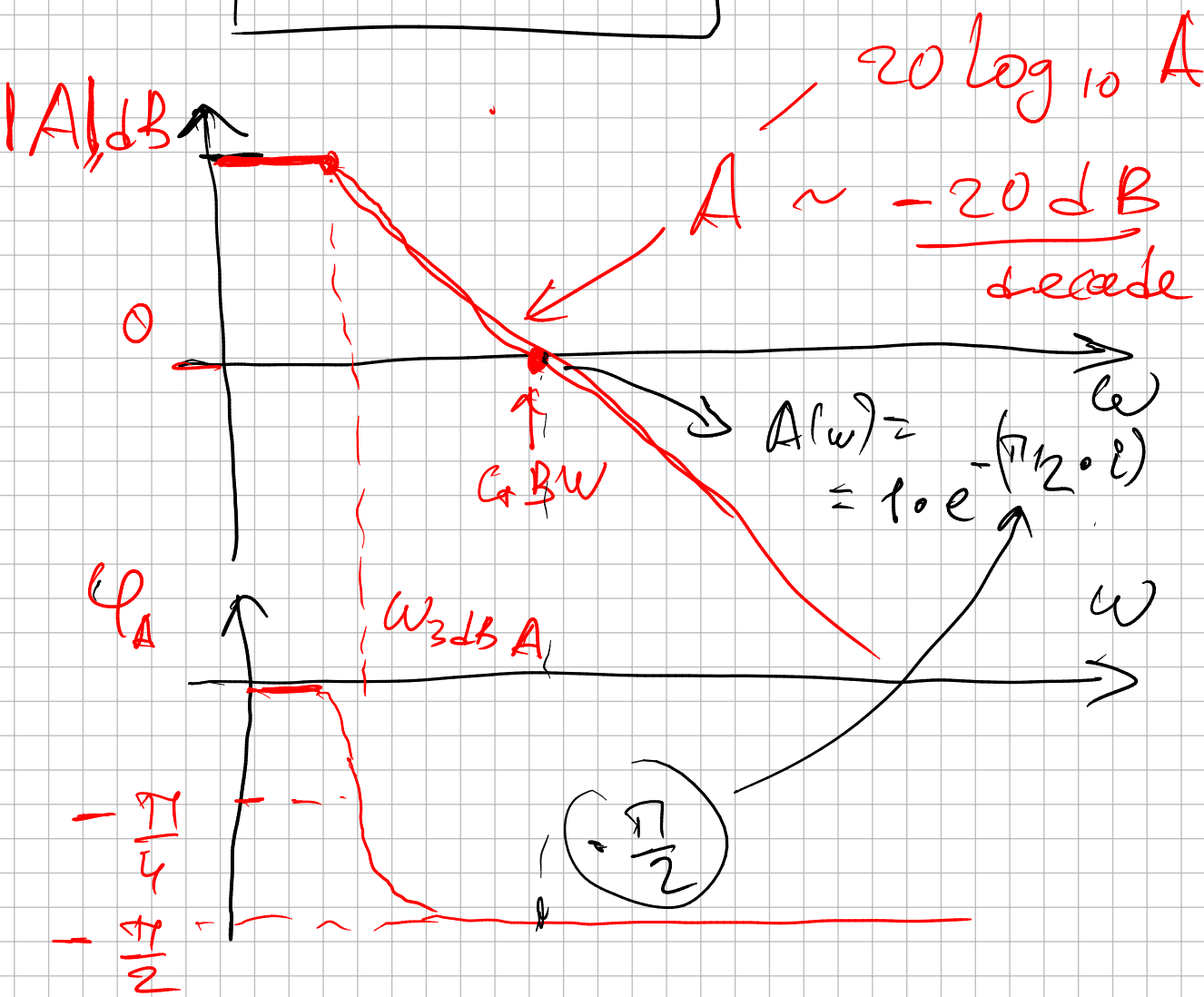


$$20 \log_{10} 1 = 0$$

$$\text{if } B(\omega) = 1$$


$$e^{j\pi} = -1$$

φ of danger is π

β - consideration

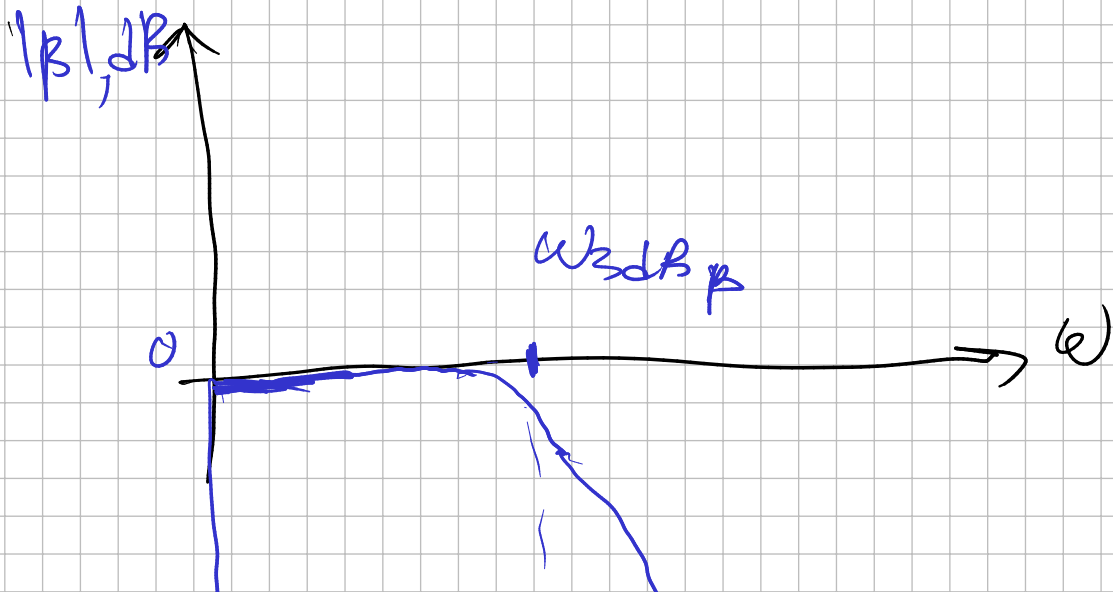

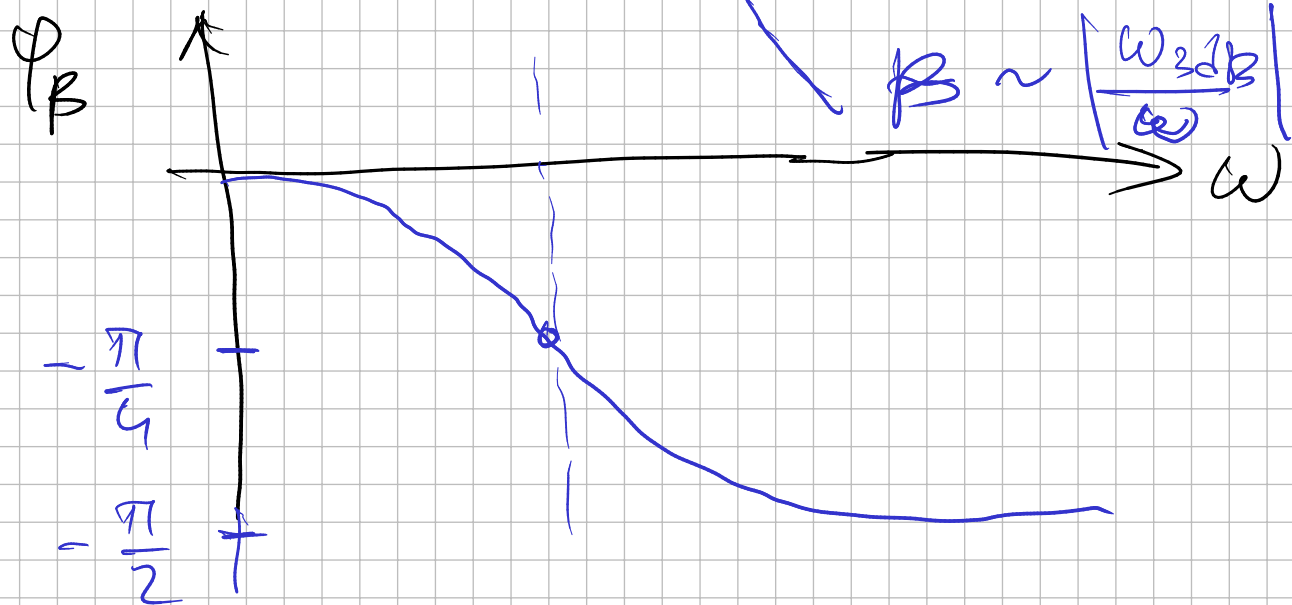$\sim \frac{20 \text{ dB}}{\text{decade}}$



$$\beta \sim \left| \frac{\omega_{3dB}}{\omega} \right| \cdot e^{-\frac{\pi}{2} \epsilon}$$

$$\frac{1}{\sqrt{2}} = e^{-\frac{\pi}{2} \epsilon}$$

$$\beta \circ A \approx -1$$

$$\omega \rightarrow \infty$$

$$\beta \sim \frac{\omega_{3dB\beta} \beta_0}{\omega} e^{-i \frac{\pi}{2}}$$

$$A \sim \frac{\omega_{3dB A}}{\omega} e^{-i \frac{\pi}{2}}$$

$$BA \sim \frac{\omega_{3dB\beta} \omega_{3dB A} \beta_0}{\omega^2}$$



$$e^{-i\pi} = -1$$

$$A \approx \frac{1}{\beta}$$


$$\omega \rightarrow \infty$$

$$20 \log_{10}(|A|) = 20 \log_{10}\left(\left|\frac{1}{\beta}\right|\right)$$

$$|A|_{dB} = -|\beta|_{dB}$$

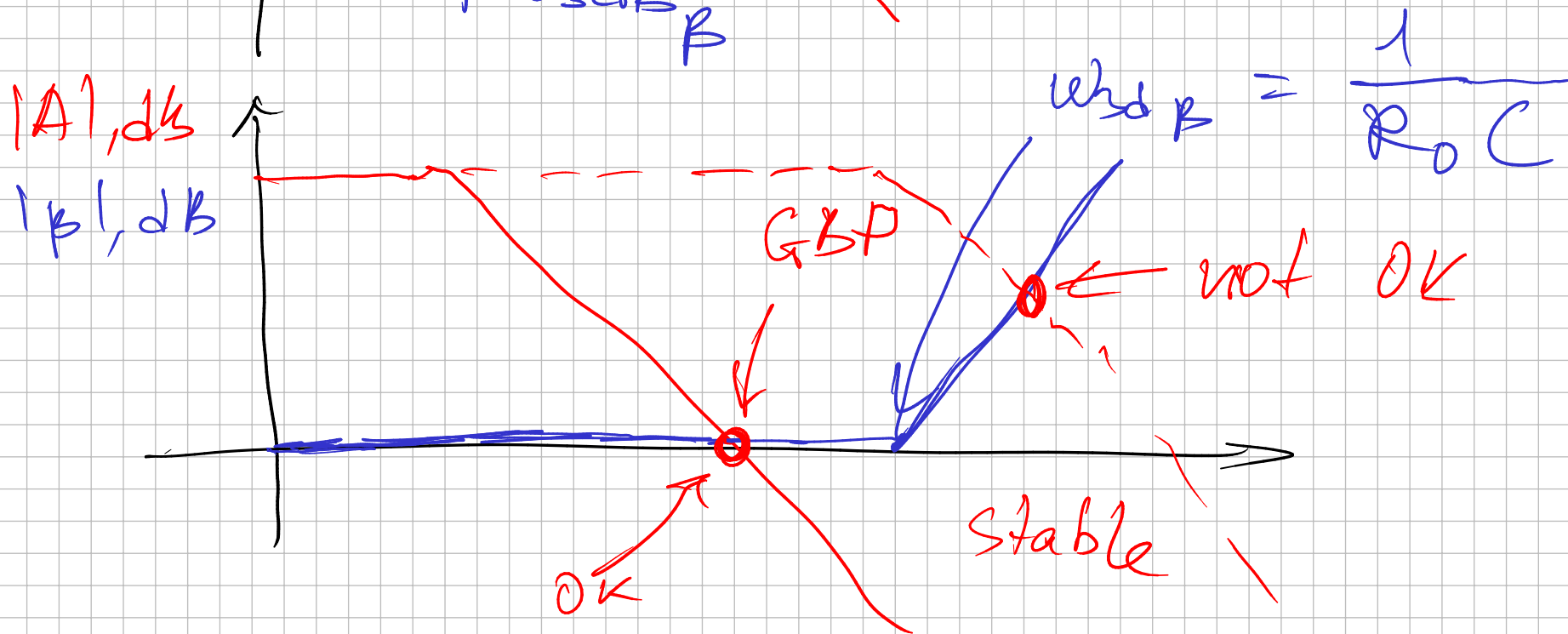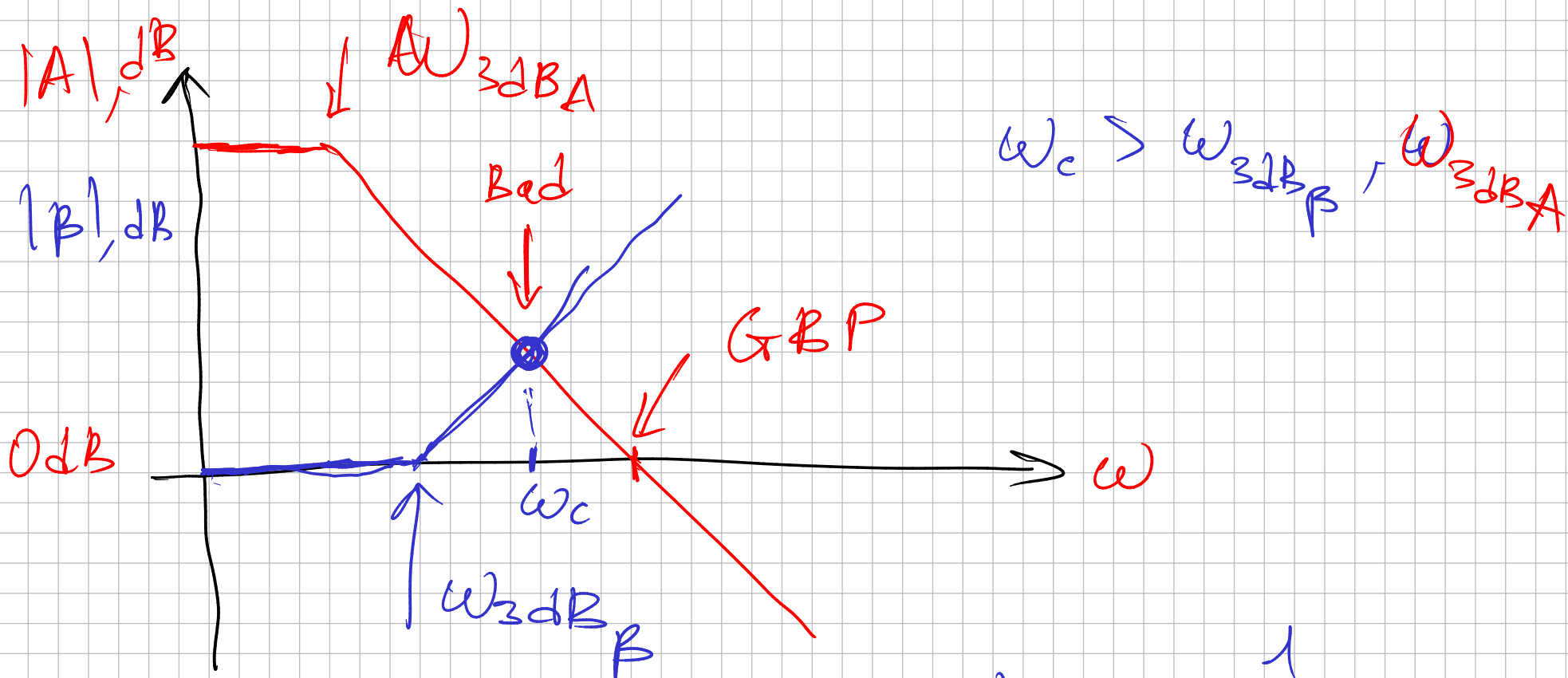

How to stabilize

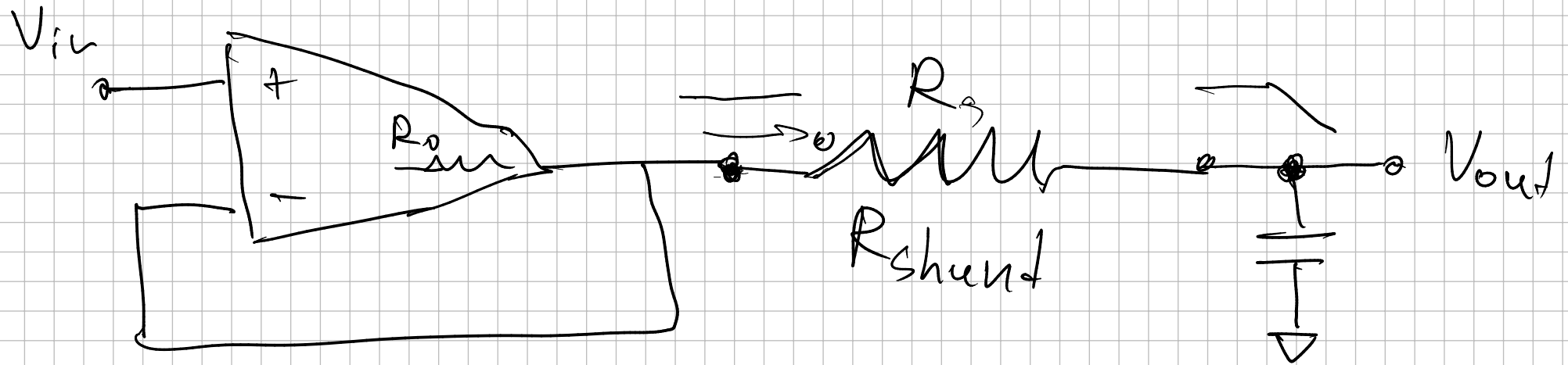

Price to pay

$$GBW \Rightarrow BW = \frac{1}{R_s \cdot C}$$

$$Z_{out} = R_s + R_o$$