

Transistors applications: AC amplifiers


Eugeniy E. Mikhailov

The College of William & Mary



Week 7


Summary of simple emitter follower

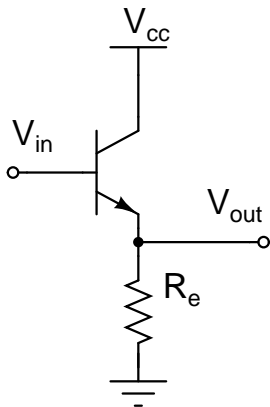

Advantages

- input impedance increase $Z_{in} = \beta R_e$
- power/current gain
- output does not depend on β
- simple

Summary of simple emitter follower

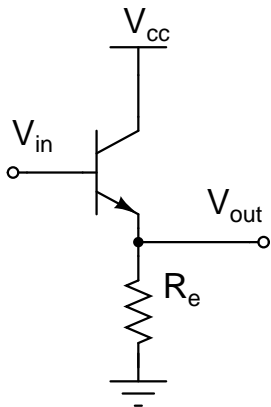

Advantages

- input impedance increase $Z_{in} = \beta R_e$
- power/current gain
- output does not depend on β
- simple

Disadvantages

- input signal must be positive
 - even more it should be above 0.6 V
- no voltage gain

Real life signal

In real life signals usually swing around zero.

Real life signal

In real life signals usually swing around zero.

We need to do something with our simple emitter follower.

Real life signal

In real life signals usually swing around zero.

We need to do something with our simple emitter follower.

Solution 1: Push-Pull follower

Real life signal

In real life signals usually swing around zero.


We need to do something with our simple emitter follower.

Solution 1: Push-Pull follower

Solution 2: AC-coupled biased-amplifier



NPN and PNP emitter follower

NPN emitter follower

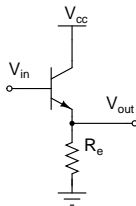



NPN and PNP emitter follower

NPN emitter follower

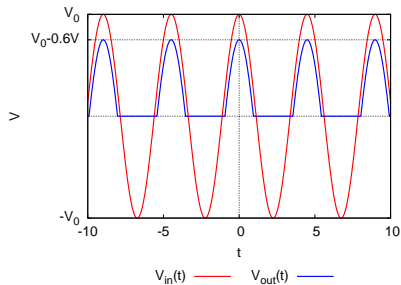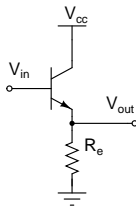


NPN and PNP emitter follower

NPN emitter follower

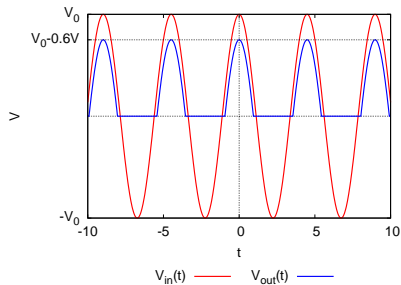
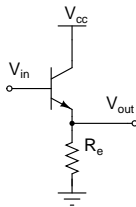


PNP emitter follower


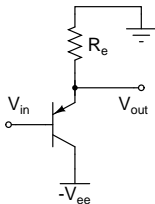


NPN and PNP emitter follower


NPN emitter follower

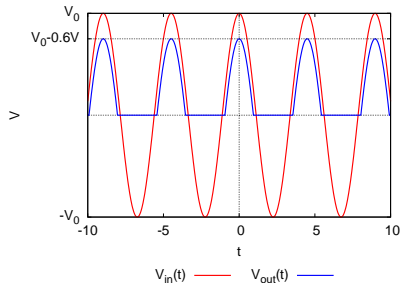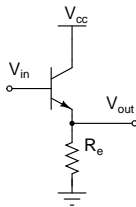



PNP emitter follower

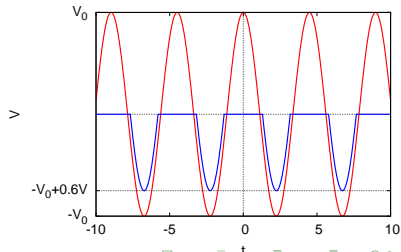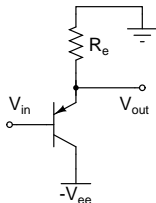


Push-Pull emitter follower

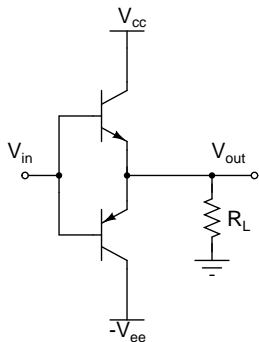

Push-Pull emitter follower

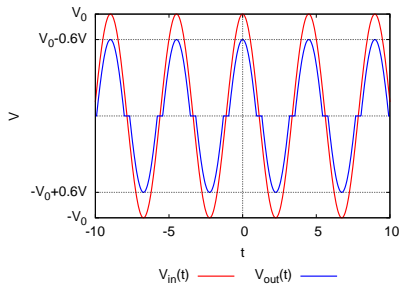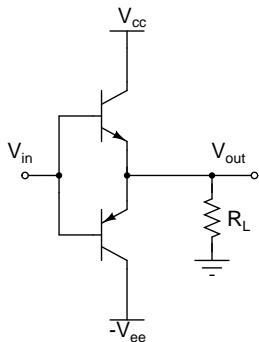


Push-Pull follower crossovers

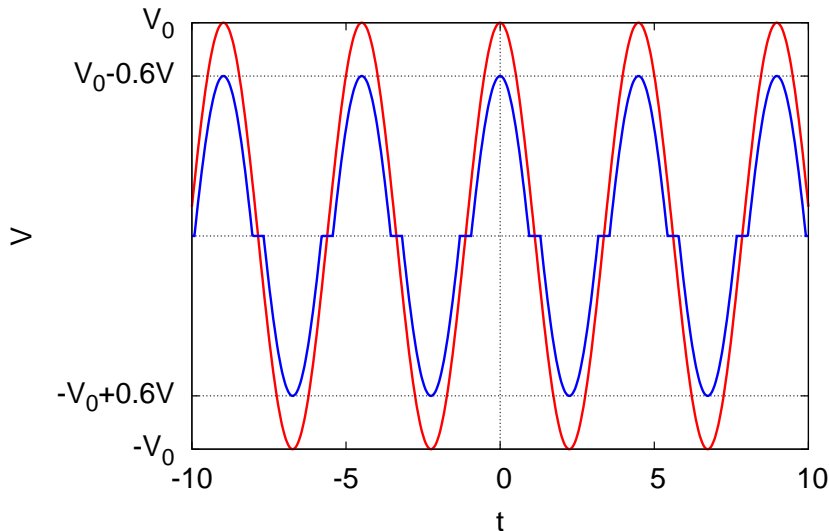


$V_{in}(t)$ ——— $V_{out}(t)$ ———


Push-Pull follower crossovers

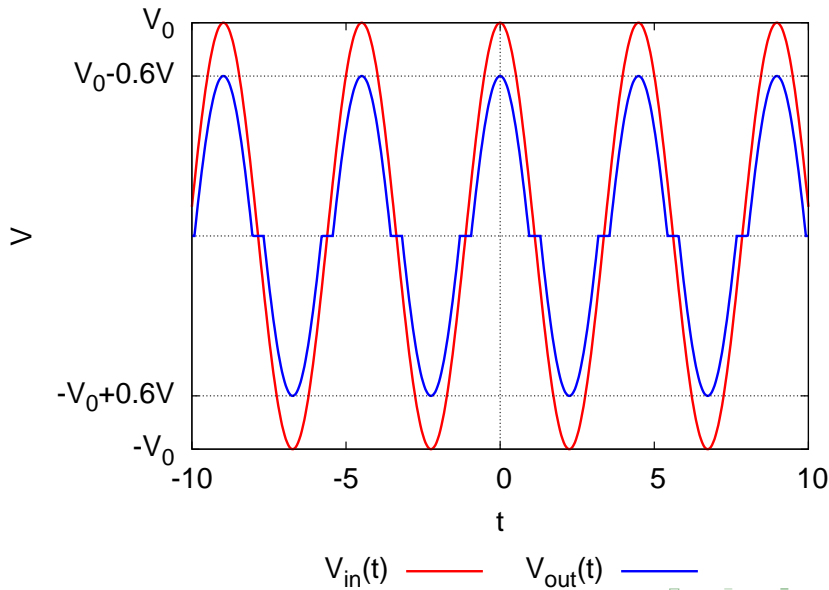



Push-Pull follower crossovers

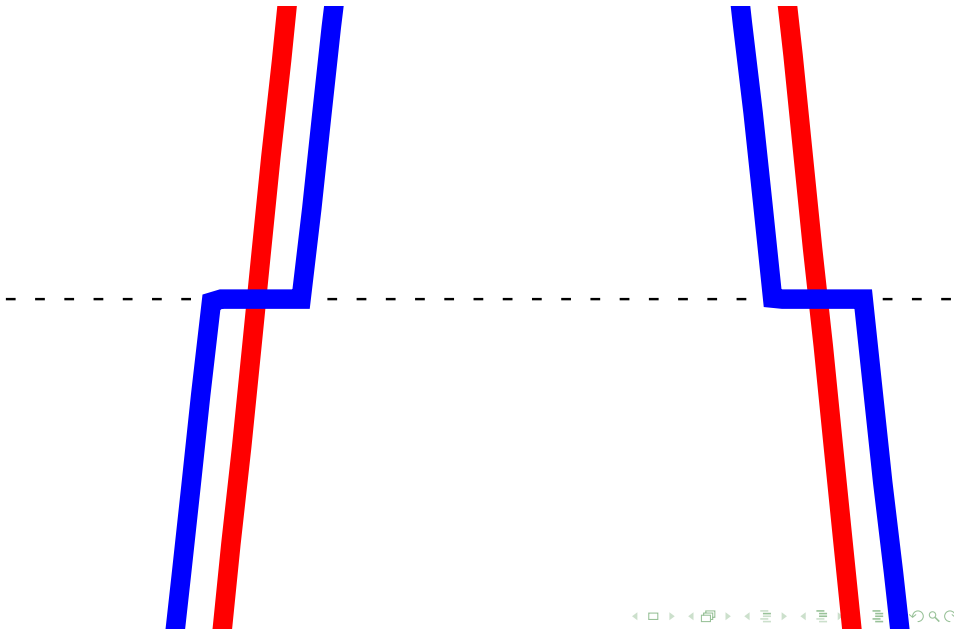


Push-Pull emitter follower improved

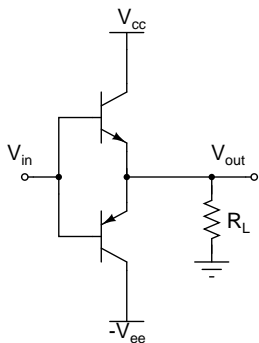


Push-Pull emitter follower improved

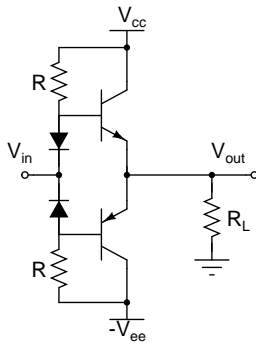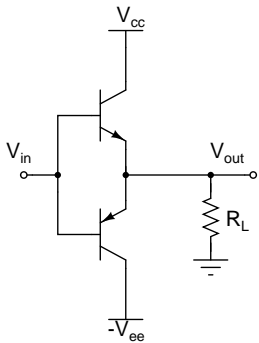

AC-coupled emitter follower

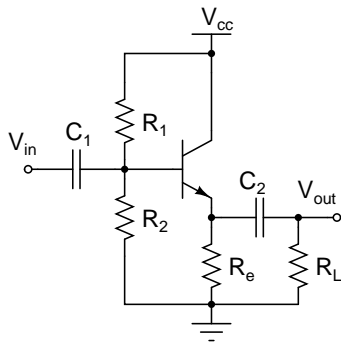

AC-coupled emitter follower

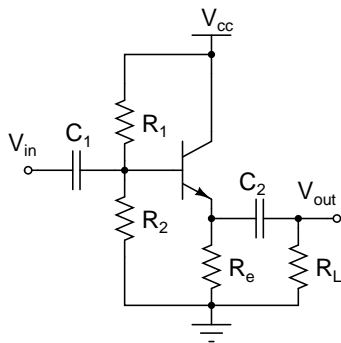


Design rules


- maximum output swing
 - $V_e = V_{cc}/2$
- disregarding $V_{be} = 0.6\text{ V}$
 - $V_b = V_e = V_{cc}/2$
 - thus $R_1 = R_2$
- quiescent current $I_e = V_e/R_e$
- we want $I_{R_1+R_2} \gg I_b$
 - factor of 10 for a safe margin
 - $I_{R_1+R_2} = 10I_b = 10I_e/\beta$
 - thus $R_1 = R_2 = R_e\beta/10$

AC-coupled emitter follower: capacitors choice

From AC point of view

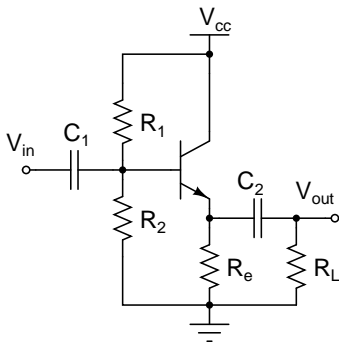


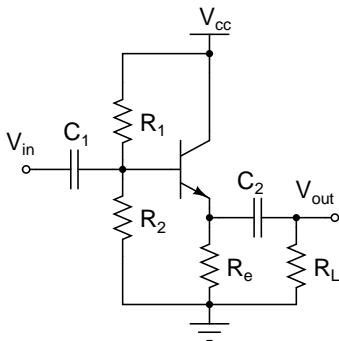AC-coupled emitter follower: capacitors choice





From AC point of view

- Input is RC high-pass
 - $C = C_1$
 - $R = R_1 || R_2 || \beta R_e$
 - $f_{3db} = \frac{1}{2\pi C_1 (R_1 || R_2 || \beta R_e)}$
 - with above rules $R \approx R_1/2$

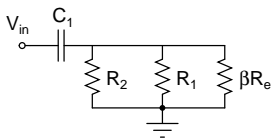

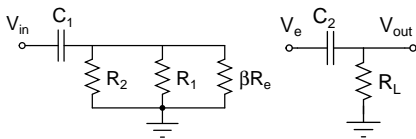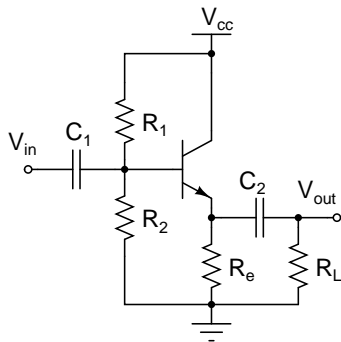
AC-coupled emitter follower: capacitors choice




From AC point of view

- Input is RC high-pass
 - $C = C_1$
 - $R = R_1 \parallel R_2 \parallel \beta R_e$
 - $f_{3db} = \frac{1}{2\pi} \frac{1}{C_1 (R_1 \parallel R_2 \parallel \beta R_e)}$
 - with above rules $R \approx R_1/2$
- Output is also RC high-pass
 - $C = C_2$
 - $R = R_L$
 - $f_{3db} = \frac{1}{2\pi} \frac{1}{C_2 R_L}$
 - for unloaded filter $R_L \gg R_e$
 - factor of 10 for a safe margin
 $R_L = 10R_e$

Common emitter (inverting) amplifier

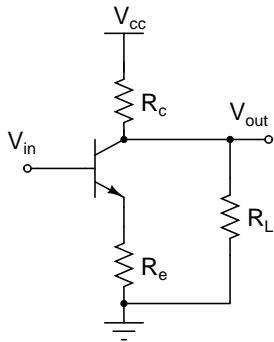


Common emitter (inverting) amplifier

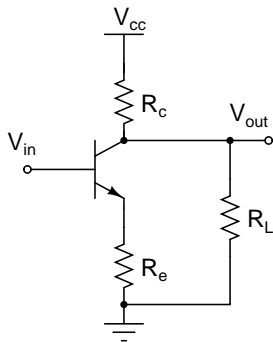


- $I_C = I_E = (V_{in} - 0.6V)/R_E$
- $V_{out} = V_{CC} - R_C I_C$
- $V_{out} = V_{CC} - R_C (V_{in} - 0.6V)/R_E$
- $V_{out} = (V_{CC} + (0.6V)R_C/R_E) - V_{in}R_C/R_E$
- gain $G = -R_C/R_E$
- attractive to put $R_E = 0$
 - transistor model fails
 - transistor emitter resistance
 $r_e = 25mV/I_C$
 - gain $G = -R_C/r_e$

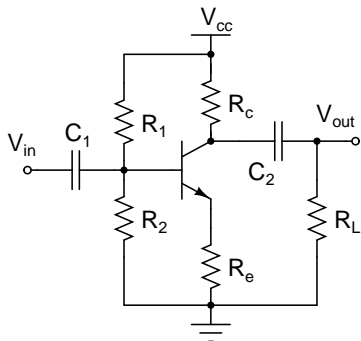AC-coupled common emitter (inverting) amplifier



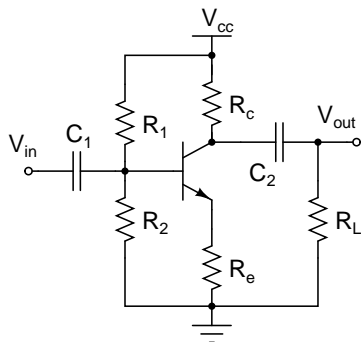AC-coupled common emitter (inverting) amplifier



Design rules

- chose gain $G = R_c/R_e$
- maximum output swing
 - $V_c = V_{cc}/2$
- quiescent current
 - $I_c = (V_{cc} - V_c)/R_c = V_{cc}/2R_c$
- $R_c = V_{cc}/(2I_c)$
- $R_e = R_c/G$
- we want $I_{R_1+R_2} \gg I_b$
 - factor of 10 for a safe margin
 - $I_{R_1+R_2} = 10I_b = 10I_c/\beta$
 - $R_1 + R_2 = V_{cc}\beta/(10I_c)$
- $V_b = V_e + 0.6$
- $R_2/(R_1 + R_2) = V_b/V_{cc}$