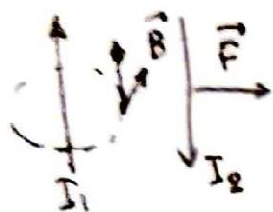


Homework 7


Problem 1

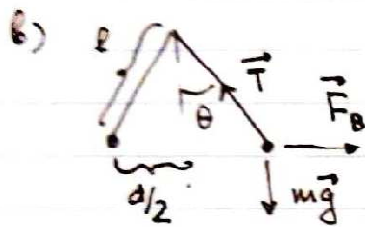- a) The magnetic field created by the first current acts on the second (and vice versa). If the two currents are counter propagating, this force is directed away from the first current.



$$B = \frac{\mu_0 I_1}{2\pi d} \quad F = L I_2 B = \frac{\mu_0 I_1 I_2}{2\pi d} L$$

$$F_B/L = \frac{\mu_0 I^2}{2\pi d} \quad I_1 = I_2$$



Equilibrium: $F_B - T \sin \theta = 0$

$$mg - T \cos \theta = 0$$

$$F_B = mg \tan \theta = \frac{\mu_0 I^2}{2\pi d} L$$

$$\theta = 8^\circ$$


$$d/2 = l \sin \theta$$

$$d = 2l \sin \theta = 1.67 \text{ cm}$$

$$\frac{m}{L} g \tan \theta = \frac{\mu_0 I^2}{2\pi d}$$

$$I = \sqrt{2\pi d g \tan \theta \cdot \frac{m}{L} \frac{1}{\mu_0}} = 67.8 \text{ A}$$

Q2

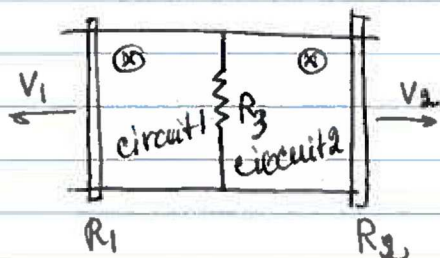

Circuit 1

$$\Delta \Phi_1 = B \cdot d \cdot v_1 \Delta t$$


$$\mathcal{E}_1 = \left| - \frac{\Delta \Phi_1}{\Delta t} \right| = B d v_1$$

Circuit 2

$$\Delta \Phi_2 = B d v_2 \Delta t$$

$$\mathcal{E}_2 = \left| - \frac{\Delta \Phi_2}{\Delta t} \right| = B d v_2$$

Equivalent circuit

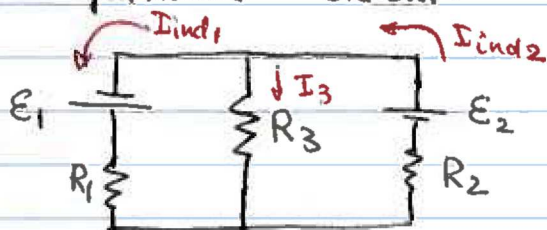

Kirchhoff's rules

$$\begin{cases} I_2 = I_1 + I_3 & (1) \\ \mathcal{E}_2 - I_3 R_3 - I_2 R_2 = 0 & (2) \\ \mathcal{E}_1 - R_1 I_1 + I_3 R_3 = 0 & (3) \end{cases}$$

$$I_1 = \frac{\mathcal{E}_1}{R_1} + I_3 \frac{R_3}{R_1} \quad \text{from (3)}$$

$$I_2 = \frac{\mathcal{E}_2}{R_2} - I_3 \frac{R_3}{R_1} \quad \text{from (2)}$$


$\mathcal{E}_{1,2}$ direction $\rightarrow$ from Lenz rule to reduce the flux

$$\text{from (1)} \quad \frac{\mathcal{E}_2}{R_2} - I_3 \frac{R_3}{R_2} = \frac{\mathcal{E}_1}{R_1} + I_3 \frac{R_3}{R_1} + I_3$$

$$\frac{\mathcal{E}_2}{R_2} - \frac{\mathcal{E}_1}{R_1} = I_3 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right)$$

$$I_3 = \frac{\mathcal{E}_2/R_2 - \mathcal{E}_1/R_1}{1 + \frac{R_3}{R_1} + \frac{R_3}{R_2}} = B \cdot d \cdot \frac{v_2/R_2 - v_1/R_1}{1 + R_3/R_1 + R_3/R_2}$$

Q3.

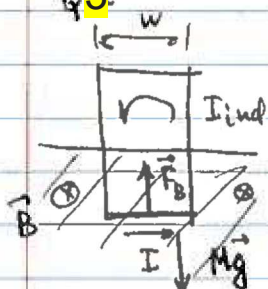

$$\frac{d\Phi_B}{dt} = Bw \cdot v = |\mathcal{E}_{\text{ind}}|$$


$$I_{\text{ind}} = \frac{\mathcal{E}_{\text{ind}}}{R} = \frac{Bwv}{R}$$

$$F_B = w \cdot B I_{\text{ind}} = \frac{B^2 w^2 v}{R}$$

In the beginning v is small, so the loop accelerates down $F_B - Mg = ma$ $a < 0$ (down)
 However, as v increases, F_B approaches Mg , and the velocity increase becomes smaller
 For the terminal velocity

$$Mg = F_B = \frac{B^2 w^2 v_t}{R} \Rightarrow v_t = \frac{MgR}{B^2 w^2}$$

Q4

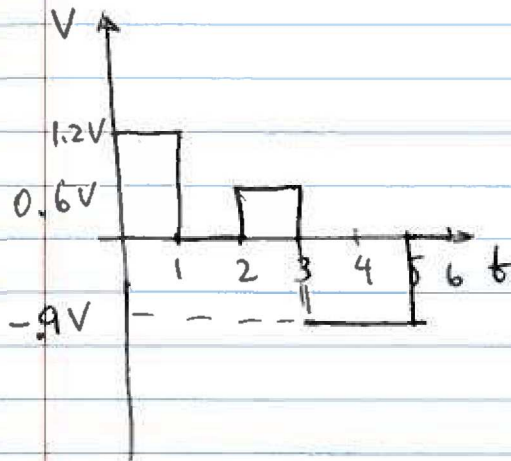

$$0-1s \quad \frac{dI}{dt} = -6A/s \quad V = -L \frac{dI}{dt} = 1.2V$$

$$1-2s \quad \frac{dI}{dt} = 0 \quad V = 0$$

$$2-3s \quad \frac{dI}{dt} = -3A/s \quad V = 0.6V$$

$$3-5s \quad \frac{dI}{dt} = 4.5A/s \quad V = -0.9V$$

$$5-6s \quad \frac{dI}{dt} = 0 \quad V = 0$$

Q5

Four possible capacitor configurations

$$C_1 = 6\mu F$$

$$C_2 = 3\mu F$$

in series $C_s = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} = 2\mu F$

parallel $C_p = C_1 + C_2 = 9\mu F$

$$\omega_1 = \frac{1}{\sqrt{LC_1}} = 4082 \text{ rad/s} = 2\pi \times 650 \text{ Hz}$$

$$\omega_2 = \frac{1}{\sqrt{LC_2}} = 5773 \text{ rad/s} = 2\pi \times 919 \text{ Hz}$$

$$\omega_s = \frac{1}{\sqrt{LC_s}} = 7071 \text{ rad/s} = 2\pi \times 1125 \text{ Hz}$$

$$\omega_p = \frac{1}{\sqrt{LC_p}} = 3333 \text{ rad/s} = 2\pi \times 531 \text{ Hz}$$