
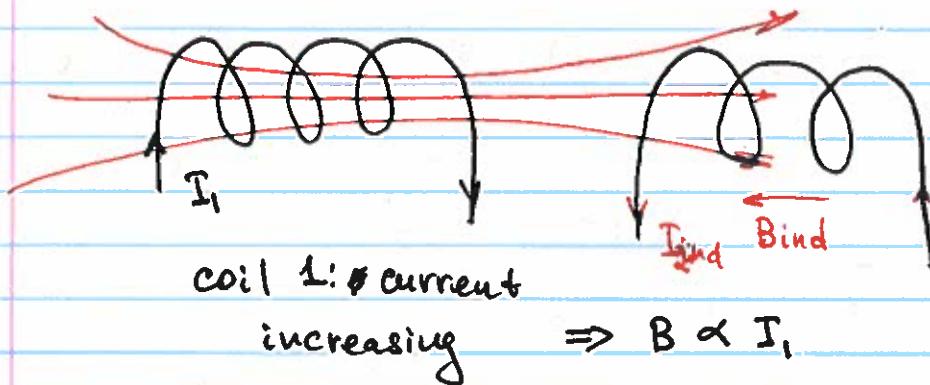


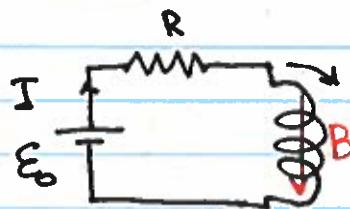Mutual induction: one current creates varying magnetic field that creates current in another circuit



$$I_2 \propto \frac{dB}{dt} \propto \frac{dI_1}{dt}$$

However, this occurs even in a single coil!



Coil length $\rightarrow l$
area $\rightarrow A$

$$B = \mu_0 \frac{N}{l} \cdot I$$

Total flux through the solenoid

$$\Phi = N \cdot \Phi_{\text{single loop}} = N \cdot B \cdot A = \frac{\mu_0 N^2 A}{l}$$

The ratio b/w the flux and current depends only on the geometry of the circuit. It is referred as inductance

$$L = \frac{\Phi}{I}$$

$$\text{For a coil } L = \frac{\mu_0 N^2 A}{l}$$

What if the current is changing?


That changes the flux; so an additional emf will be induced in the coil

$$E_{\text{ind}} = - \frac{d\Phi}{dt} = -L \frac{dI}{dt}$$

Current increasing \rightarrow induced E_{ind} is against E_0
decreasing \rightarrow induced E_{ind} is along E_0

Since the behavior of the inductance depends on how the electric current changes, it only manifest itself when something is changing.

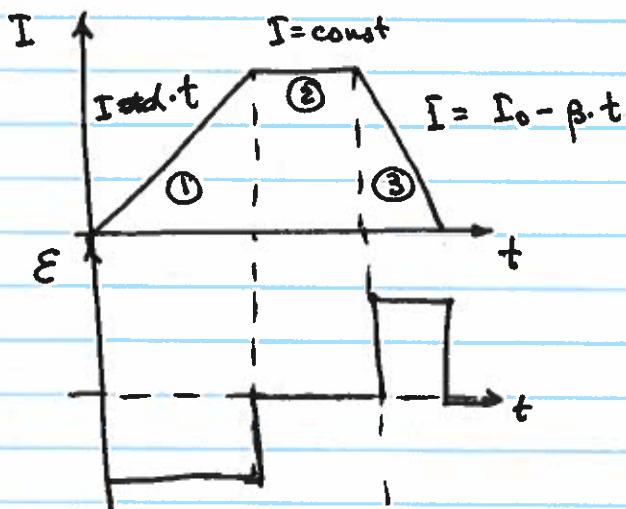Constant current \rightarrow any inductance is just a long wire, no role




$$\textcircled{1} \quad \mathcal{E}_1 = -L \frac{dI}{dt} = -\alpha \cdot L$$

$$\textcircled{2} \quad \mathcal{E}_2 = -L \frac{dI}{dt} = 0$$

$$\textcircled{3} \quad \mathcal{E}_3 = -L \frac{dI}{dt} = \beta \cdot L$$


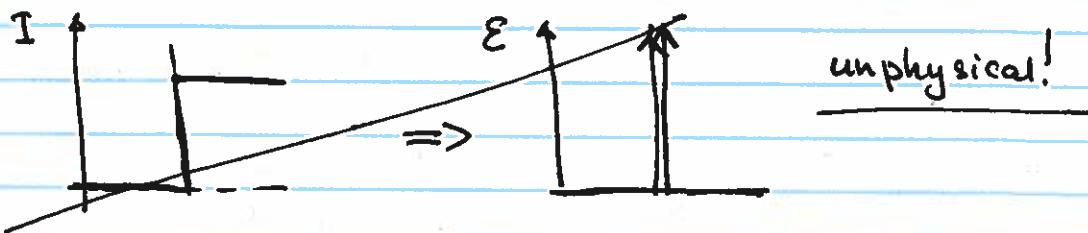
However, current through an inductance cannot change as a step \rightarrow infinite EMF





Thus, if something changes in a circuit, at the first moment the current through the induction does not change but develops an EMF to support the constant current.

Unlike a resistor, ~~the~~ whose voltage / current can change instantaneously.


Resistor:

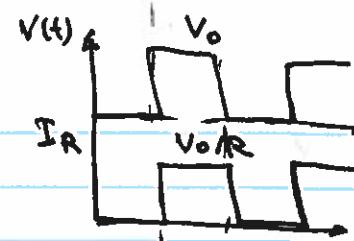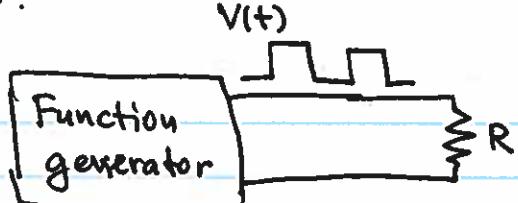

Inductor:

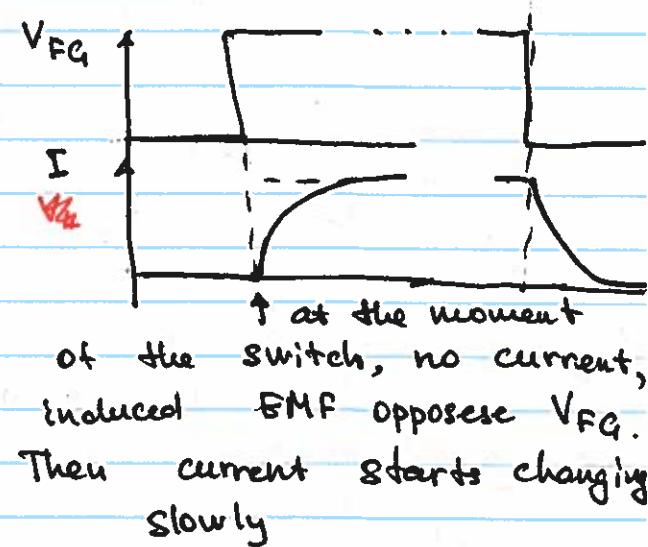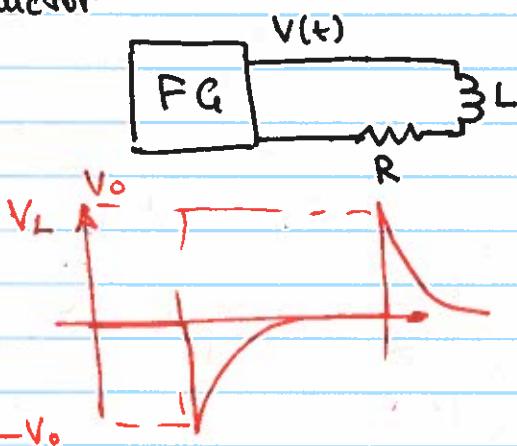

Example:

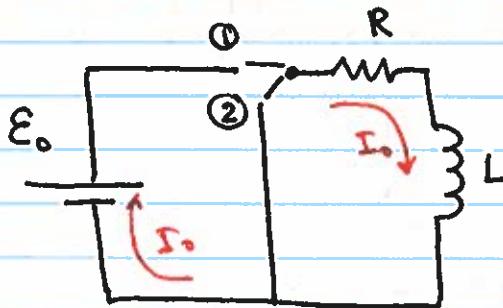

Switch in position 1



in steady state



no role in steady state

$$I_0 = \frac{E_0}{R}$$

Switch in position 2, $t=0+$



Current through L (and R) stays the same, I_0 .

$$E_{ind} = I_0 \cdot R \quad (\text{Kirchhoff rules})$$

-1k

As time goes by $E_{\text{ind}}(t) = I(t) \cdot R = 0$

$$-L \frac{dI}{dt} - I \cdot R = 0$$


$$\frac{dI}{dt} = -\frac{R}{L} I$$

Exponential solution $I(t) = I_0 e^{-t/\tau_{RL}}$


$$\frac{dI}{dt} = -\frac{1}{\tau_{RL}} I_0 e^{-t/\tau_{RL}} = -\frac{R}{L} I_0 e^{-t/\tau_{RL}}$$

$$\tau_{RL} = \frac{L}{R}$$

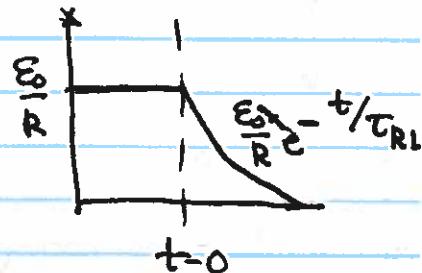
Current $I(t) = \frac{E_0}{R} e^{-R/L \cdot t}$




Switching from position 1 to position 2

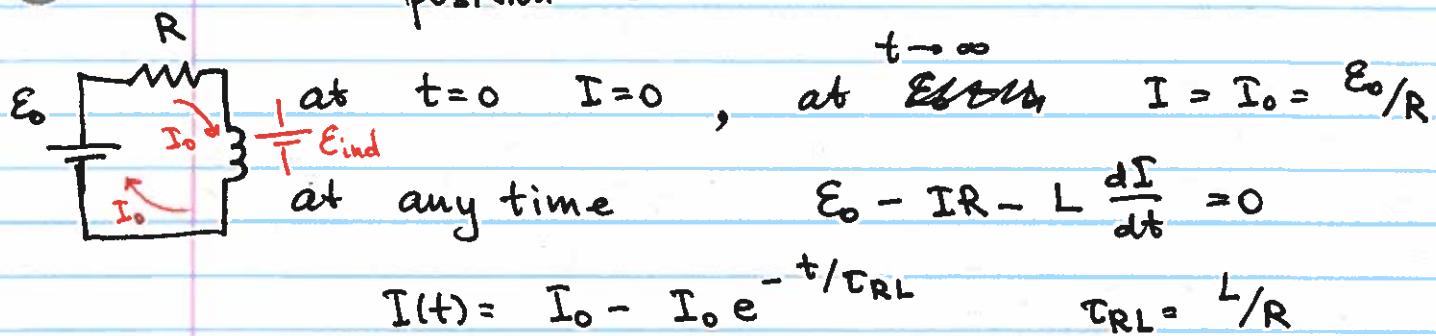

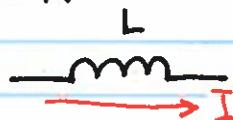The direction of the induced EMF always opposes the change of the current



Current increases

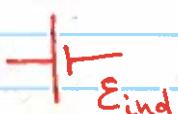

$$\text{value } E_{\text{ind}} = -L \frac{dI}{dt}$$

Current decreases



$$E_{\text{ind}}$$