
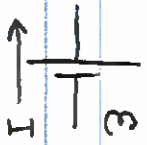


Circuits with capacitors

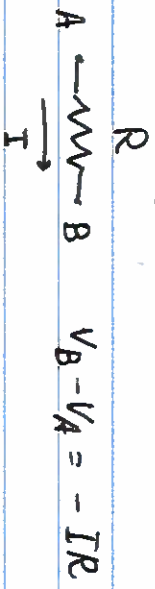Reminder: a battery provides emf to make electrons move




The voltage drop across the resistor always follows the Ohm's law




Switch closed $\mathcal{E} = IR$

Switch open $I_0 = 0$

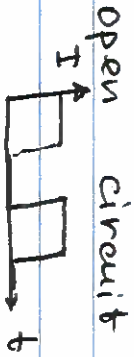

Switch closed $\mathcal{E} = I_0 \frac{R_1 R_2}{R_1 + R_2}$

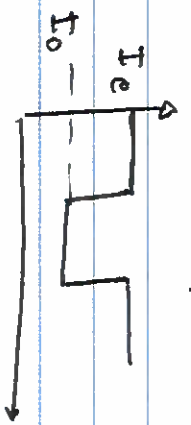Switch open $\mathcal{E} = I_0 \cdot R_1$




Current changes instantaneously and stays constant

(DC circuits)


Things are different for a capacitor since it charges \rightarrow its voltage changes

$$V = \frac{Q}{C}$$

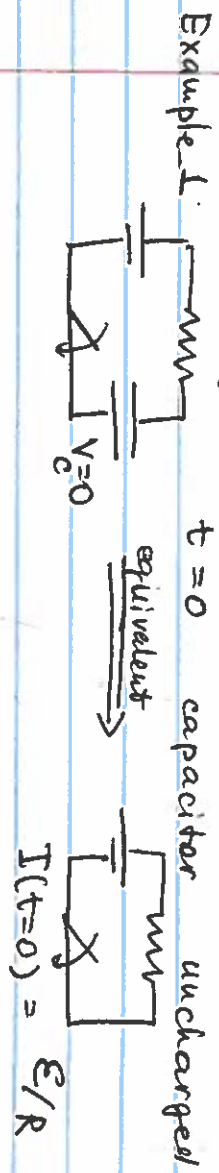no charge $Q=0 \Rightarrow V=0$ (like a wire!)



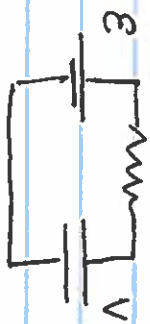
If we let the capacitor fully charge $t \rightarrow \infty$



Since charges would move until the voltage across the capacitor

matches the emf $V = E = Q/C$
 $I(t \rightarrow \infty) = 0$
 $Q = E \cdot C$

Example 2:

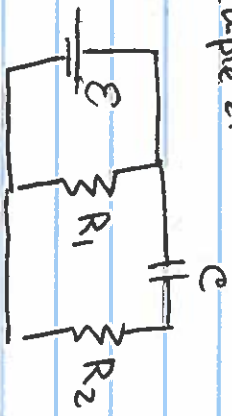

$t=0$ $V_c=0$ (= wire)




$$E = I(t=0) \cdot R_{eq}$$

$$I(t=0) = \frac{E(R_1 + R_2)}{R_1 R_2}$$


$t \rightarrow \infty$ capacitor is fully charged
 no current through C & R2

$$I(t \rightarrow \infty) = \frac{E}{R_1}$$


Example 3:

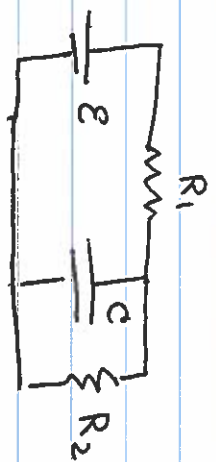

$$I(t=0) = \frac{\epsilon}{R_1}$$

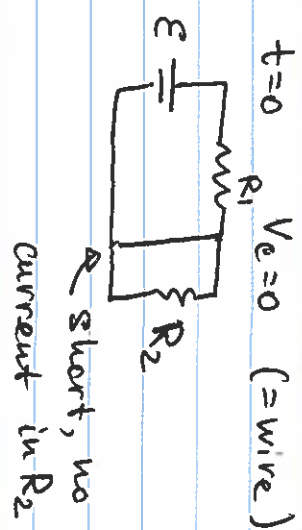

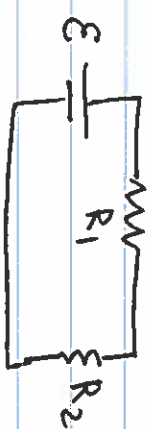Capacitor is fully charged, no current through C , $V_c = V_{R_2}$




$$I(t \rightarrow \infty) = \frac{\epsilon}{R_1 + R_2}$$

$$V_c = V_{R_2} = IR_2 = \frac{\epsilon R_2}{R_1 + R_2}$$

$$Q = V_c \cdot C = C \cdot \frac{\epsilon R_2}{R_1 + R_2}$$

How to calculate $I(t)$?

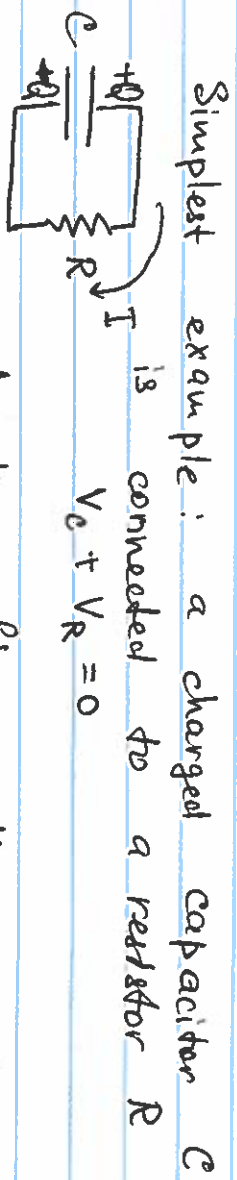

As time flows the capacitor charge diminishes, its voltage reduces, so the current becomes proportionally smaller

$$V_C = \frac{Q(t)}{C} \quad V_R = -I(t)R \quad I(t) = -\frac{dQ}{dt}$$

$$\frac{Q(t)}{C} = I(t) \cdot R = -R \frac{dQ(t)}{dt}$$

$$\frac{dQ(t)}{dt} = -\frac{1}{RC} Q(t)$$


$$Q(t) = Q(t=0) e^{-t/\tau} = Q_{max} e^{-t/\tau}$$

$$\frac{dQ}{dt} = -\frac{1}{\tau} Q_{max} e^{-t/\tau}$$


$$-\frac{1}{\tau} Q_{max} e^{-t/\tau} = -\frac{1}{RC} Q_{max} e^{-t/\tau}$$

$\tau = RC$ time constant of an RC circuit
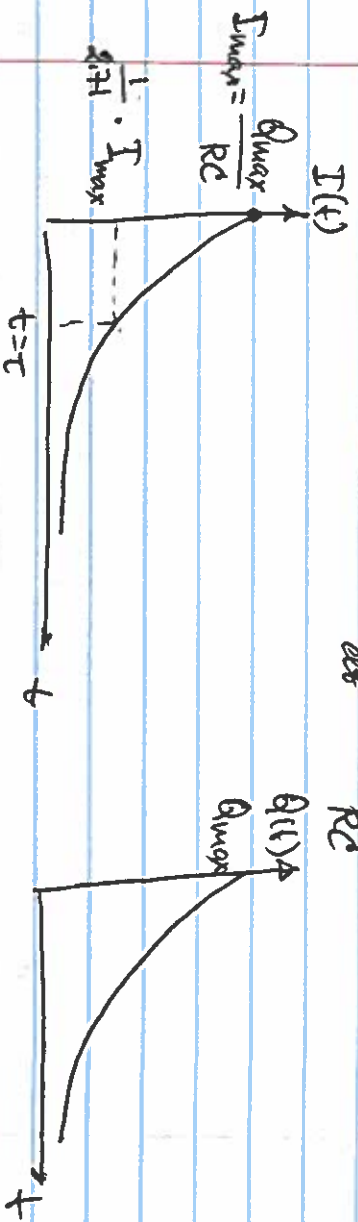
$$I(t) = -\frac{dQ}{dt} = \frac{Q_{max}}{RC} e^{-t/RC}$$



What about our previous examples?

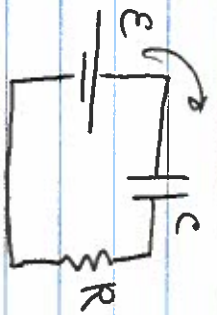

$$I(t=0) = \frac{\epsilon}{R}$$

$$I(t \rightarrow \infty) = 0$$

Capacitor is charging $\epsilon - \frac{Q(t)}{C} - IR = 0$

$$I = \frac{dQ}{dt} \quad \epsilon - \frac{Q}{C} - R \frac{dQ}{dt} = 0$$

$$\frac{dQ}{dt} = \frac{\epsilon}{R} - \frac{Q}{RC} = \frac{\epsilon \cdot C - Q}{RC}$$

$$\int_{Q(t=0)=0}^{+} \frac{dQ}{-\epsilon C + Q} = - \int_0^t \frac{dt}{RC}$$

$$\ln(Q - \epsilon C) \Big|_0^{Q(t)} = - \frac{t}{RC}$$


$$\ln\left(\frac{Q - \epsilon C}{-\epsilon C}\right) = \ln\left(\frac{\epsilon C - Q}{\epsilon C}\right) = - \frac{t}{RC}$$

$$\frac{\epsilon \cdot C - Q(t)}{\epsilon \cdot C} = e^{-t/RC}$$

$$Q(t) = \epsilon \cdot C - C \cdot \epsilon \cdot e^{-t/RC} = C \cdot \epsilon (1 - e^{-t/RC})$$


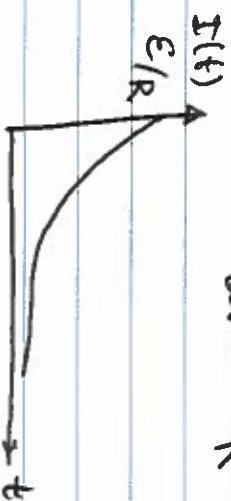
$$I(t) = \frac{dQ}{dt} = \frac{\epsilon}{R} e^{-t/RC}$$



A bit more complicated circuit



$$I(t=0) = \frac{R_1 + R_2}{R_1 R_2} \epsilon$$

$$I(t=\infty) = \epsilon / R_1$$

Kirchhoff's rule

$$I(t) = I_1(t) + I_2(t)$$

$$\epsilon = I_1 R_1 \quad I_1 = \frac{\epsilon}{R_1} \text{ at any time}$$

$$\epsilon - \frac{Q(t)}{C} - I_2(t) \cdot R_2 = 0$$

This is the same eqn we just solved!

$$I_2(t) = \frac{\epsilon}{R_2} e^{-t/R_2 C}$$

$$I(t) = \frac{\epsilon}{R_1} + \frac{\epsilon}{R_2} e^{-t/R_2 C}$$

From the same solution

$$Q(t) = C \cdot \epsilon (1 - e^{-t/R_2 C})$$

