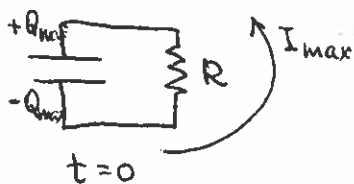


DC Circuits with capacitors

If a circuit consists of batteries and resistors only, all changes are (nearly) instantaneous, and values of currents & voltages does not depend on time.

It's not the case when capacitors are involved!

Example 1: charged capacitor connected to a resistor



as time flows
the charge on the capacitor
reduces, and energy gets
lost to heat on the resistor

$$I_{max} = \frac{V_{max}}{R} = \frac{Q_{max}}{CR}$$



After the long time
all charges are zero,
no current



$V_{capacitor} = V_{resistor}$ at any time

$$\frac{Q(t)}{C} = -I(t)R$$

but also $I(t) = \frac{dQ(t)}{dt}$

$$\frac{dQ(t)}{dt} = -\frac{1}{RC} Q(t)$$


Simple(st) differential equation

~~$$\frac{dy}{dx} = -\frac{1}{\tau} y \Rightarrow y(x) = y(0) e^{-x/\tau}$$~~

$$\frac{dy}{dt} = -\frac{1}{\tau} \cdot y \Rightarrow y(t) = y(0) e^{-t/\tau}$$

$$Q(t) = Q_{max} e^{-t/RC}$$

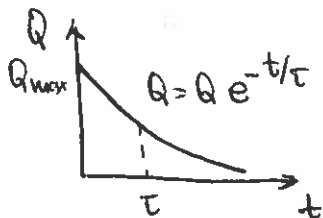$\tau = RC$ is a time constant of an RC circuit




$$I(t) = \left| \frac{dQ}{dt} \right| = \left| -\frac{Q_{max}}{RC} \right| e^{-t/RC} = I_{max} e^{-t/RC}$$

$\tau = RC$ is a characteristic time
for the capacitor to get
discharged.

So if you need to measure a voltage across a charged capacitor, you must ensure your voltmeter has high resistance!

Let's consider charging a capacitor

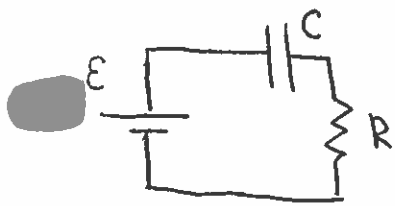


$$Q(t=0) = 0 \quad V_C(t=0) = 0$$

at $t=0$: $\epsilon - I(t=0) \cdot R = 0 \quad I_{t=0} = \frac{\epsilon}{R}$

Uncharged capacitor is equivalent to a straight wire!



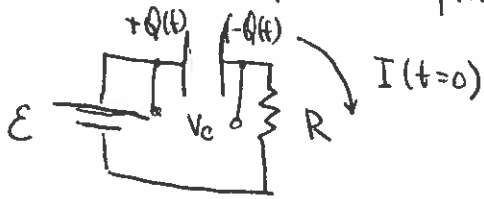As current flows, it starts "depositing" charges on the capacitor plates



$$V_C(t) = \frac{Q(t)}{C}$$

$$\epsilon - \frac{Q(t)}{C} - IR = 0$$

$$\epsilon - \frac{dQ}{C} - \frac{dQ}{dt} \cdot R = 0$$

$$\frac{dQ}{dt} = -\frac{Q}{RC} + \frac{\epsilon}{R} = -\frac{(Q - C\epsilon)}{RC}$$



$$\int_{Q(t=0)}^Q \frac{dQ}{Q - C\epsilon} = -\int \frac{dt}{RC}$$

$$\ln(Q(t) - C\epsilon) \Big|_0^{Q(t)} = \ln\left(\frac{C\epsilon - Q(t)}{C\epsilon}\right) = -\frac{t}{RC}$$

$$\frac{C\epsilon - Q(t)}{C\epsilon} = e^{-t/RC}$$

$$Q(t) = C \cdot \epsilon - C\epsilon \cdot e^{-t/RC} = C\epsilon(1 - e^{-t/RC})$$
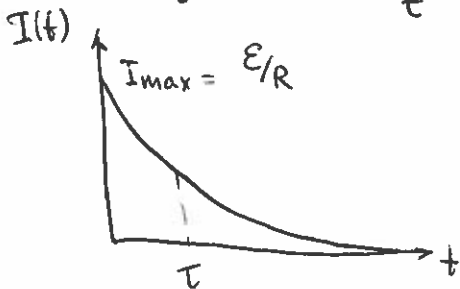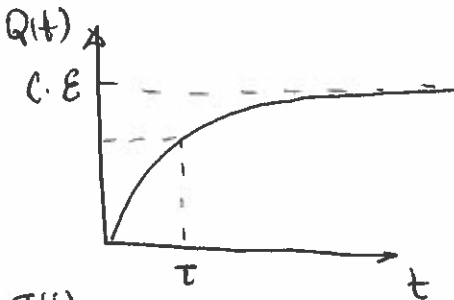
$$I(t) = \frac{dQ(t)}{dt} = C\epsilon \left(-\left(-\frac{1}{RC}\right)e^{-t/RC}\right) = \frac{\epsilon}{R} e^{-t/RC}$$




So after a long time, when capacitor is charged, it is equivalent to the circuit break.

What if we want to monitor the voltage across the capacitor using a voltmeter?

Ideal voltmeter has infinitely high resistance, but in reality it is just large $R_{int} \gg R$.

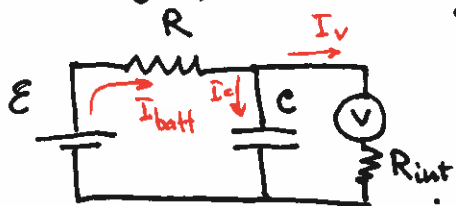Thus, there will be some current flowing through the meter even when the capacitor is fully charged, distorting the measurement



The voltmeter will show the voltage drop across the capacitor

$$I_{batt} = I_c + I_v \text{ at any moment of time}$$

$$\frac{Q}{C} = I_v \cdot R_{int}$$

$$I_c = \frac{dQ}{dt}$$

$$I_v = \frac{Q}{R_{int} \cdot C}$$

$$\epsilon - I_{batt} R - I_v \cdot R_{int} = 0$$

$$\epsilon - (I_c + I_v) \cdot R - I_v R_{int} = 0$$

$$\epsilon - I_c \cdot R - I_v \cdot (R + R_{int}) = 0$$

$$\epsilon - I_c \cdot R - \frac{Q}{R_{int} \cdot C} (R + R_{int}) = 0$$

$$\epsilon - \frac{Q}{C} \left(1 + \frac{R}{R_{int}}\right) - R \frac{dQ}{dt} = 0$$

$$\frac{dQ}{dt} = \frac{\epsilon}{R} - \frac{Q}{C} \left(\frac{1}{R} + \frac{1}{R_{int}}\right) = \frac{\epsilon}{R} - \frac{Q}{C R_{eq}} \Rightarrow \frac{dQ}{\frac{\epsilon}{R} - \frac{Q}{C R_{eq}}} = dt$$

correction due to measurements

$$\ln \left(\frac{\epsilon/R - Q(t)/C \cdot R_{eq}}{\epsilon/R} \right) = -\frac{t}{C R_{eq}}$$

$$R_{eq} = \frac{R \cdot R_{int}}{R + R_{int}}$$

$$Q(t) = EC \frac{R_{eq}}{R} (1 - e^{-t/C R_{eq}})$$


R_{eq} approaches R if $R \ll R_{int}$, but $R_{eq} < R$

when $t \rightarrow \infty$ the full capacitor charge is $Q_{final} = EC \frac{R_{eq}}{R}$

and the measured voltage $V_{final} = Q_{final} \cdot C = \epsilon \cdot \frac{R_{eq}}{R}$

So the measured voltage is smaller than ϵ by a factor of R_{eq}/R or $R_{int}/(R + R_{int})$

More examples

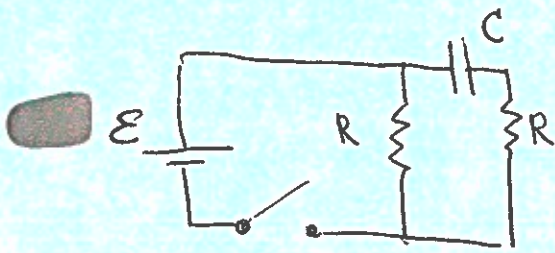

If the capacitor is not charged and a switch is closed at $t=0$
Immediately after the closing


$$t = 0^+$$



~~To~~ The current through the battery is
 $I = 2\epsilon/R$


After a very long time

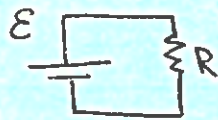$V_C = \epsilon$, capacitor is fully charged
no current flows through that branch



$$I = \epsilon/R$$

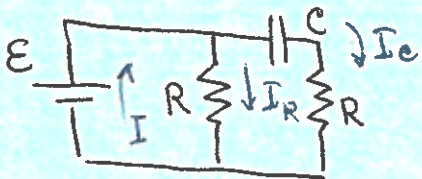If one needs to calculate how the charge changed in between one would use Kirchoff's rules (



$$I = I_R + I_C$$

$$\epsilon - I_R \cdot R = 0 \Rightarrow I_R = \epsilon/R$$

$$\epsilon - Q(t)/C - I_C R = 0 \quad I_C = \frac{dQ}{dt}$$

same equation we did already

$$Q_C(t) = \epsilon C (1 - e^{-t/RC})$$

$$I_C(t) = \frac{\epsilon}{R} e^{-t/RC}$$

The current through the battery

$$I = I_C + I_R = \frac{\epsilon}{R} + \frac{\epsilon}{R} e^{-t/RC}$$

