


$$\mathcal{E}_1 = L_1 \frac{dI}{dt}, \quad \mathcal{E}_2 = L_2 \frac{dI}{dt}$$

$$\mathcal{E}_3 = L_3 \frac{dI}{dt}$$

$$\mathcal{E}_{tot} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 = \underbrace{(L_1 + L_2 + L_3)}_{L_{eq}} \frac{dI}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3 \quad \text{for series connection}$$

Parallel connection

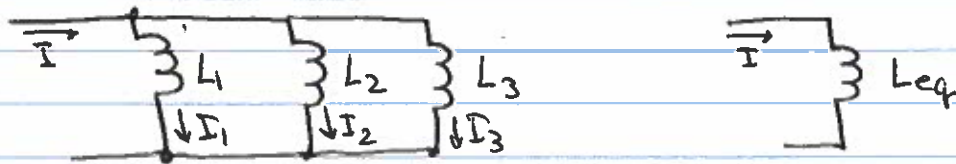


$$\mathcal{E}_{ind} = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} = L_3 \frac{dI_3}{dt}$$

$$\frac{dI_1}{dt} = \frac{\mathcal{E}}{L_1} \quad \frac{dI_2}{dt} = \frac{\mathcal{E}}{L_2} \quad \frac{dI_3}{dt} = \frac{\mathcal{E}}{L_3}$$


$$\frac{dI}{dt} = \frac{\mathcal{E}_{eq}}{L_{eq}} = \frac{d(I_1 + I_2 + I_3)}{dt}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \quad \text{for parallel connection}$$

Example 6 more complicated circuit

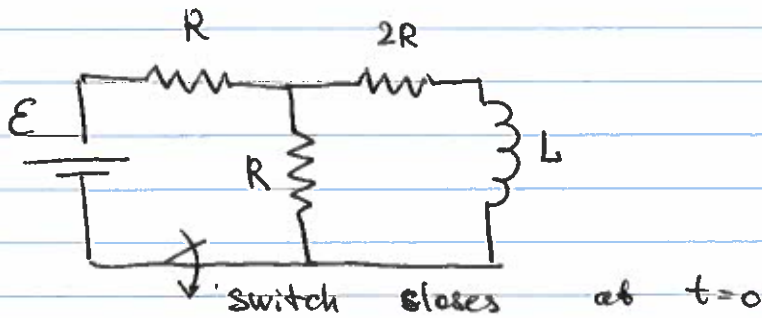

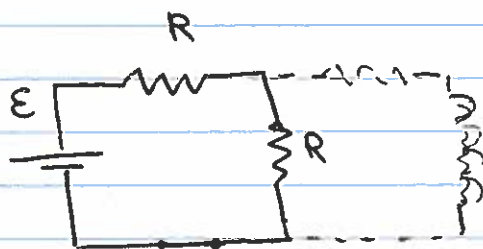
time $t=0^+$ → no current flows through the inductance



$$I_{\text{coil}} = 0$$

$$I_{\text{switch}} = \frac{\epsilon}{2R}$$

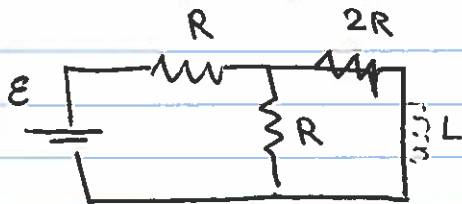time $t \rightarrow \infty$ current is stable, L is equivalent to a wire




$$R_{\text{eq}} = R + \frac{1}{\frac{1}{R} + \frac{1}{2R}} = \frac{5}{3}R$$

$$I_{\text{switch}} = \frac{3\epsilon}{5R}$$

$$I_{\text{coil}} = I_{2R} = \frac{1}{3} I_{\text{switch}} = \frac{\epsilon}{5R}$$

At any $t > 0$

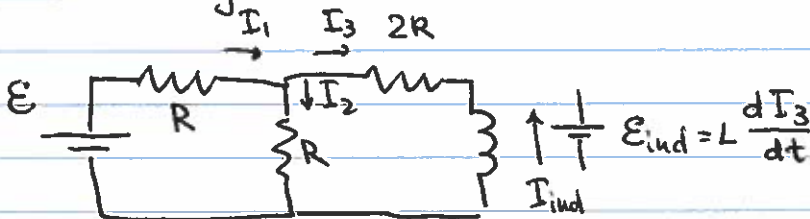

- Kirchhoff's rules:
- ① $I_1 = I_2 + I_3$
 - ② $\epsilon - I_1 R - I_2 R = 0$
 - ③ $\epsilon - I_1 R - 2I_3 R - L \frac{dI_3}{dt} = 0$

$$I_2 = I_1 - I_3$$

$$\mathcal{E} - I_1 R - (I_1 - I_3)R = 0 \quad R I_1 = (\mathcal{E} + R I_3) / 2$$

$$\mathcal{E} - \frac{\mathcal{E}}{2} - \frac{R I_3}{2} - 2 I_3 R - L \frac{d I_3}{dt} = 0$$

$$-L \frac{d I_3}{dt} - \frac{5}{2} R I_3 + \frac{\mathcal{E}}{2} = 0$$

We know the general solution form

$$I_3(t) = \text{~~reticula~~} A(1 - e^{-t/\tau}) \quad \text{since } I_3(t=0) = 0$$

moreover, since we know that $I_3(t \rightarrow \infty) = \mathcal{E}/5R$

we know that $A = \mathcal{E}/5R$, so we only

need to find τ

$$I_3 = \frac{\mathcal{E}}{5R} (1 - e^{-t/\tau})$$

$$\frac{d I_3}{dt} = \frac{\mathcal{E}}{5R} \frac{1}{\tau} e^{-t/\tau}$$

$$- \frac{L \mathcal{E}}{5R} \frac{1}{\tau} e^{-t/\tau} - \frac{5}{2} \frac{\mathcal{E}}{5R} (1 - e^{-t/\tau}) + \frac{\mathcal{E}}{2} = 0$$

$$- \frac{L \mathcal{E}}{5R} \frac{1}{\tau} e^{-t/\tau} - \frac{\mathcal{E}}{2} + \frac{\mathcal{E}}{2} e^{-t/\tau} + \frac{\mathcal{E}}{2} = 0$$



$$- \frac{L \mathcal{E}}{5R} \frac{1}{\tau} + \frac{\mathcal{E}}{2} = 0 \quad \Rightarrow \quad \tau = \frac{2L}{5R}$$

$$I_3 = \frac{\mathcal{E}}{5R} (1 - e^{-t/\tau})$$

~~$$I_1 = \frac{\mathcal{E}}{2R} + \frac{I_3}{2} = \frac{\mathcal{E}}{2R} + \frac{\mathcal{E}}{10R} - \frac{\mathcal{E}}{10R} e^{-t/\tau} =$$~~

$$I_1 = \frac{\mathcal{E}}{2R} + \frac{I_3}{2} = \frac{\mathcal{E}}{2R} + \frac{\mathcal{E}}{10R} - \frac{\mathcal{E}}{10R} e^{-t/\tau} =$$
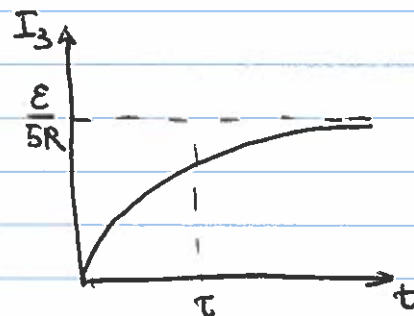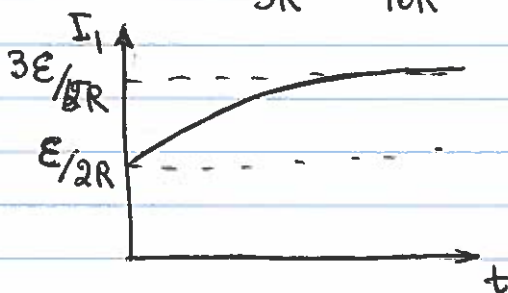
$$= \frac{3\mathcal{E}}{5R} - \frac{\mathcal{E}}{10R} e^{-t/\tau}$$



Basic circuit components

voltage drop across: a resistor

$$V_R = R \cdot I$$


an inductor

$$V_L = -L \frac{dI}{dt}$$

a capacitor

$$V_C = \frac{Q}{C} = \frac{1}{C} \int_0^t I(t') dt'$$

RC circuit

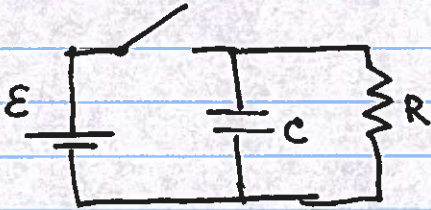

$$t < 0 \quad V_C = \varepsilon, \quad I_0 = \varepsilon/R$$


$$-IR + \frac{Q}{C} = 0 \quad I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} = -\frac{1}{RC} \cdot Q = 0$$

$$Q(t) = \varepsilon \cdot C e^{-t/\tau_{RC}}$$


$$\tau_{RC} = RC$$
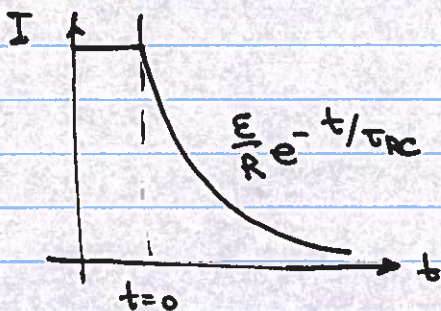
$$I(t) = -\frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/\tau_{RC}}$$



Charged capacitor works as a voltage source allowing current to run until it is discharged

RL circuit

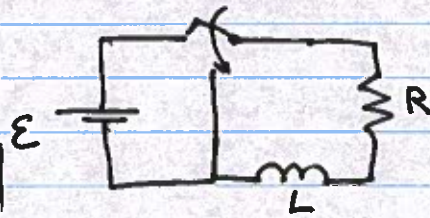

$$t < 0 \quad V_L = 0, \quad I_0 = \varepsilon/R$$


$$t = 0 \quad I_L = I_0$$

$$-IR - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} = -\frac{R}{L} I$$

$$I = I_0 e^{-t/\tau_{RL}}$$

$$\tau_{RL} = R/L$$

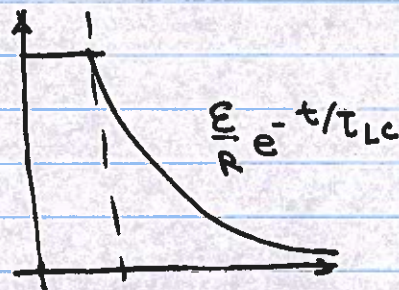

Magnetic energy stored in the coil is used to keep the current running for a while