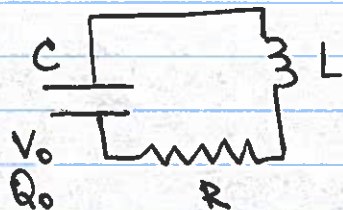


AC circuits — with complex numbers!

Let's get back to RLC circuit



$$\frac{Q}{C} + IR + L \frac{dI}{dt} = 0 \quad I = - \frac{dQ}{dt}$$

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

Hard to calculate : if $Q(t) = Q_0 \cos \omega t$
 $\frac{dQ}{dt} = -Q_0 \omega \sin \omega t$

doable with a lot of trig identities $\therefore$

Let's for a moment consider overdamped ~~src~~ circuit (large R) $\rightarrow$ no oscillations
 so we can guess $Q(t) = Q_0 e^{-\beta t}$ (decay)

$$\frac{d^2 Q}{dt^2} L \beta^2 (Q_0 e^{-\beta t}) - R \beta (Q_0 e^{-\beta t}) + \frac{1}{C} (Q_0 e^{-\beta t}) = 0$$

$$L \beta^2 - R \beta + \frac{1}{C} = 0$$

$$\beta_{1,2} = \frac{R \pm \sqrt{R^2 - 4L/C}}{2L}$$

If $R > \sqrt{4L/C}$ β is a real number
 (no oscillations, as expected)

But what if $R < \sqrt{4L/C}$? $\Rightarrow \sqrt{R^2 - \frac{4L}{C}} = i \sqrt{\frac{4L}{C} - R^2}$

$$\beta_{1,2} = \underbrace{\frac{R}{2L}}_{\text{real part}} \pm i \underbrace{\sqrt{\frac{1}{LC} - \frac{R^2}{4L}}}_{\text{imaginary part}}$$


if $R=0$ perfect oscillations $\beta_{1,2} = \pm \frac{i}{\sqrt{LC}} = \pm i \omega_L C$ $Q(t) \propto e^{\pm i \omega_L t}$

Why physicists love complex numbers


Euler formula $z = e^{i\varphi} = \cos\varphi + i\sin\varphi$
for any $|z|=1$ complex number

if $|z| = z_0 \Rightarrow z = z_0 e^{i\varphi} = z_0 \cos\varphi + i z_0 \sin\varphi$

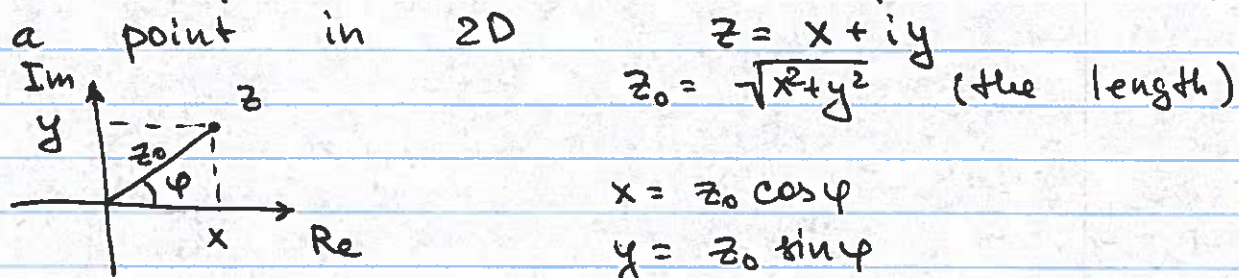A complex number can represent
a point in 2D



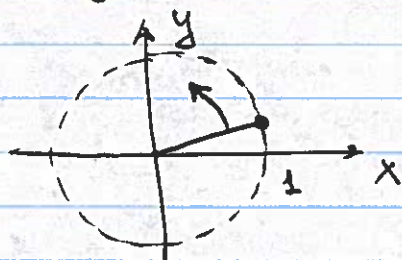Imagine a rotating point with frequency ω



$\varphi = \omega t$ if $x(t=0) = 1, y(t=0) = 0$
 $x(t) = \cos\omega t = \text{Re}[e^{i\omega t}]$
 $y(t) = \sin\omega t = \text{Im}[e^{i\omega t}]$



So for many problems with oscillations
or wave, it is convenient use complex
exponents instead of cos/sine functions,
and just take real part at the end

Alternatively, one can use

$$\cos\varphi = \frac{1}{2} (e^{i\varphi} + e^{-i\varphi})$$



$$\sin\varphi = \frac{1}{2i} (e^{i\varphi} - e^{-i\varphi})$$

Voltage and current
are in phase

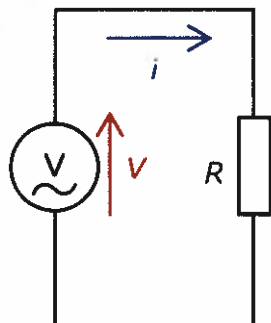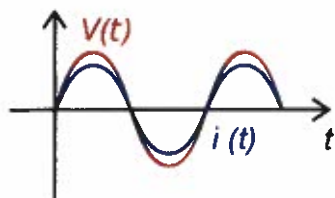



$$i(t) = \frac{V_{max}}{R} \sin \omega t$$

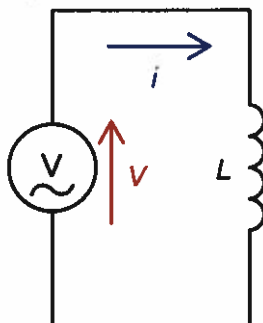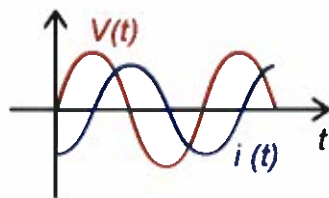The current lags behind the
voltage by a phase of 90°



$$i(t) = \frac{V_{max}}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

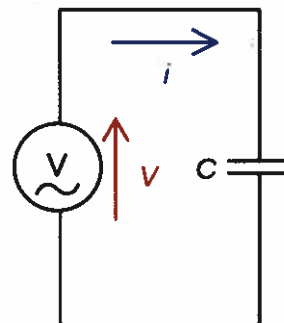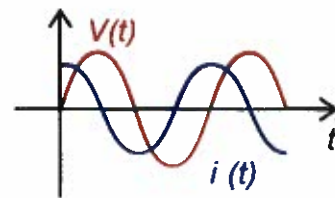The current leads the
voltage by a phase of 90°




$$i(t) = \omega C V_{max} \sin \left(\omega t + \frac{\pi}{2} \right)$$

AC circuit $\rightarrow$ with oscillating voltage source

①



$$V_{AC}(t) = V_{\max} \cos \omega t$$

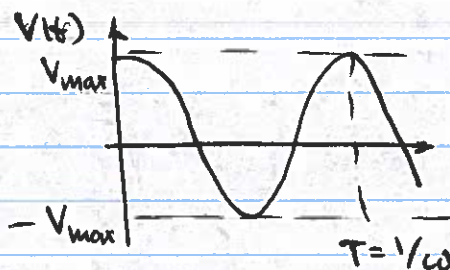

② If such source is connected to a resistor, what is the current through a resistor?
 $i_R(t) - ?$

$$V_{AC}(t) - i_R \cdot R = 0$$

$$i_R = \frac{V_{AC}(t)}{R} = \frac{V_{\max}}{R} \cos \omega t$$

in phase
with the
voltage source

②



$$V_{AC} - \frac{Q(t)}{C} = 0$$


$$Q(t) = C \cdot V_{AC}(t) = C \cdot V_{\max} \cos \omega t$$

$$V_{AC} = V_{\max} \cos \omega t$$

$$I(t) = \frac{dQ}{dt} = -C V_{\max} \omega \sin \omega t$$

$$I(t) = -(C\omega) \cdot V_{\max} \sin \omega t$$

③

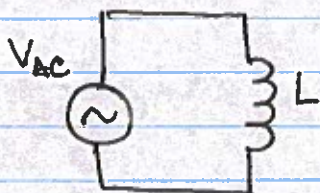

$$V_{AC}(t) - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} = \frac{1}{L} V_{AC}(t) = \frac{V_{\max}}{L} \cos \omega t$$

$$I(t) = \frac{V_{\max}}{L\omega} \sin \omega t$$

$$V_{Ac}(t) = V_{max} \cos \omega t \quad \rightarrow \quad I_R = \frac{1}{R} V_{max} \cos \omega t$$


same phase

$$\rightarrow I_C = \omega C \cdot V_{max} \cos(\omega t + \frac{\pi}{2})$$

a quarter cycle ahead of V_{Ac}
or $\pi/2$ ahead

$$\rightarrow I_L = \frac{1}{\omega L} V_{max} \cos(\omega t - \frac{\pi}{2})$$

a quarter cycle ($\pi/2$) behind

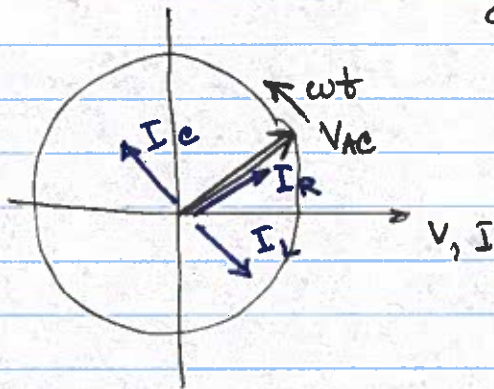

If $V_{Ac} = \text{Re} [V_{max} e^{i\omega t}]$

then $I_R = \text{Re} [\frac{V_{max}}{R} e^{i\omega t}]$

$$I_L = \text{Re} [\frac{V_{max}}{\omega L} e^{i\omega t} \cdot e^{-i\pi/2}]$$

$$I_C = \text{Re} [\omega C \cdot V_{max} e^{i\omega t} \cdot e^{i\pi/2}]$$

$$e^{i\pi/2} = \cos \pi/2 + i \sin \pi/2 = i$$

$$e^{-i\pi/2} = \cos \pi/2 - i \sin \pi/2 = -i = \frac{1}{i}$$

$$I_R = \text{Re} [\frac{V_{max}}{R} \cdot \frac{1}{R} \cdot V(t)]$$

$$I_C = \text{Re} [\underbrace{i\omega C}_{1/Z_C} \cdot V(t)] \quad I_L = \text{Re} [\underbrace{\frac{1}{i\omega L}}_{1/Z_L} V_{Ac}]$$

reactance $\rightarrow$ similar
to resistance, and

behaves the same way


$$Z_C = \frac{1}{i\omega C}$$

$$Z_L = i\omega L$$

Reactance Z behave just as normal resistance R in Ohm's law

$$V_R = R \cdot I \quad V_L = Z_L \cdot I = i\omega L \cdot I \quad V_C = Z_C \cdot I = \frac{1}{i\omega C} I$$
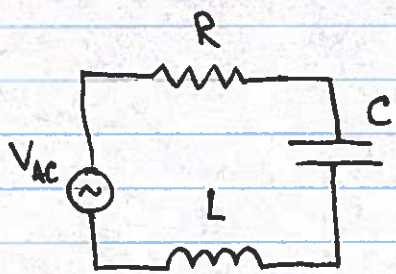
$$V_{AC}(t) = V_m \cos \omega t = \text{Re} [V_m e^{i\omega t}] \rightarrow \text{do calculations with } V_{AC}(t) = V_m e^{i\omega t}$$



$$V_{AC} - IR - \frac{Q}{C} - L \frac{dI}{dt} = 0$$

vs

$$V_{AC} - R \cdot I - Z_C \cdot I - Z_L \cdot I = 0$$

$$I = \frac{V_{AC}}{R + Z_C + Z_L} = \frac{V_m}{R + i\omega L + \frac{1}{i\omega C}} e^{i\omega t}$$

To calculate real current we need to take real part of I now

$$I(t) = \text{Re} \left[\frac{V_m}{R + i\omega L + \frac{1}{i\omega C}} e^{i\omega t} \right]$$

convert into polar form

$$x + iy = \sqrt{x^2 + y^2} (\cos \varphi + i \sin \varphi) = \sqrt{x^2 + y^2} \left[\underbrace{\frac{x}{\sqrt{x^2 + y^2}}}_{\cos \varphi} + i \underbrace{\frac{y}{\sqrt{x^2 + y^2}}}_{\sin \varphi} \right]$$

$$\tan \varphi = x/y$$

$$R + i\omega L + \frac{1}{i\omega C} = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} e^{i\varphi_{RLC}} \quad \varphi_{RLC} = \tan^{-1} \frac{R}{\omega L - \frac{1}{\omega C}}$$


$$I(t) = \text{Re} \left[\frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} e^{-i\varphi_{RLC}} e^{i\omega t} \right]$$

$$I(t) = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cos(\omega t - \varphi_{RLC})$$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

maximum amplitude
resonance @ $\omega L = \frac{1}{\omega C}$
 $\omega^2 = 1/LC = \omega_{LC}^2$

AC circuits terminology

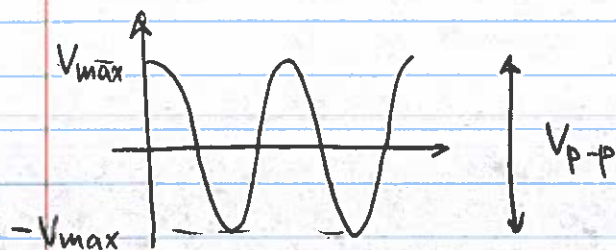

$$V_{AC}(t) = V_{max} \cos \omega t$$

V_{max} - amplitude

Peak-to-peak $V_{p-p} = 2V_{max}$

What is V_{RMS} ?


rms → root mean square



$$V(t) = V_{max} \cos \omega t$$

$$I(t) = V_{max}/R \cos \omega t$$

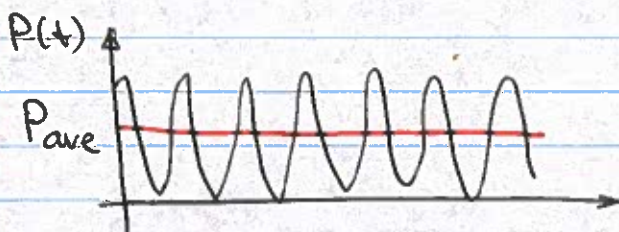Instantaneous power $P(t) = V \cdot I =$
 $= \frac{V_{max}^2}{R} \cos^2 \omega t$



When averaged over many oscillations

$$\langle \cos^2 \omega t \rangle = \frac{1}{2}$$

$$P_{ave} = \frac{1}{2} \frac{V_{max}^2}{R} = \frac{(V_{max}/\sqrt{2})^2}{R}$$

If we have a circuit with constant voltage source $E = V_{max}/\sqrt{2}$, it will put out the same power over the long time as AC circuit with amplitude V_{max}

$$V_{RMS} = \frac{V_{max}}{\sqrt{2}}$$

$$I_{RMS} = \frac{I_{max}}{\sqrt{2}}$$