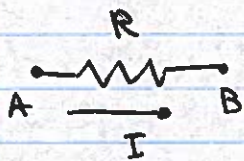


## Quick summary of circuit elements (so far)


— wire, no resistance, connects points with same potential



Ohm's law  $V_A - V_B = IR$  (voltage drop)


Power converted to heat

$$P = I^2 R = I \cdot V = V^2 / 2R$$

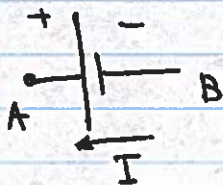

Ideal battery  $V_A - V_B = \mathcal{E}$  emf  
Source of constant potential difference

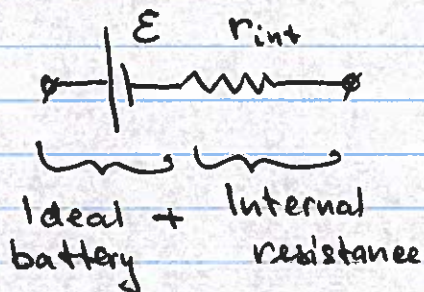Side note: real battery has non-zero resistance  
In a circuit we present it as



Actual voltage drop  
 $V_{\text{battery}} = \mathcal{E} - I \cdot r_{\text{int}}$


When a battery starts "dying", its internal resistance grows, effectively reducing voltage drops.

# Electric circuit: parallel and serial connections

## Important rules

- ① Points connected by an (ideal) ~~wire~~ wire have the same potential
- ② If elements are connected in series, the same current flows through all of them

## Series connection of resistors

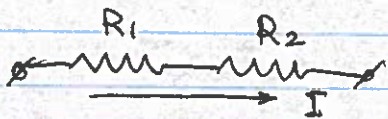


$$R_{eq} = R_1 + R_2 (+R_3)$$

Voltage drop

$$V_{R_1} = I \cdot R_1$$
$$V_{R_2} = I \cdot R_2$$
$$V_{tot} = V_1 + V_2$$

## Parallel connection

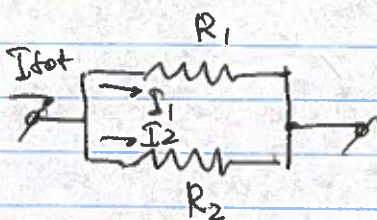

$$V_{R_1} = V_{R_2} = V$$
$$V_{R_1} = I_1 V$$
$$V_{R_2} = I_2 V$$
$$I_{tot} = I_1 + I_2$$
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} (+ \frac{1}{R_3} \dots)$$

## Poll Ev questions



$$I = \frac{E}{2R}$$


Power ~~em~~ emitted by one bulb (R)

$$P_1 = I^2 \cdot R = E^2/4R$$

Total light power  $P = 2P_1 = E^2/2R$

Alternatively  $P_{tot} = I^2 \cdot R_{eq} = \left(\frac{E}{2R}\right)^2 \cdot 2R = E^2/2R$

If the second bulb is shorted

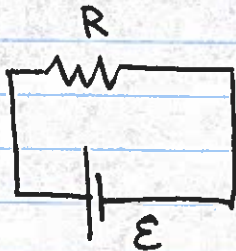


$$I = E/R$$

$$P = I^2 \cdot R = E^2/R$$

twice brighter than before

## Parallel connection

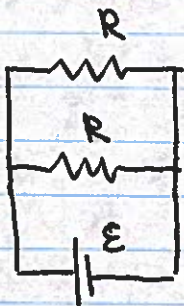

Current through each resistor  $I_1$

$$E = I_1 \cdot R \Rightarrow I_1 = E/R$$

Power dissipated ~~for~~ at each resistor

$$P_1 = I_1^2 \cdot R = E^2/R$$


$$P_{tot} = 2P_1 = 2E^2/R$$

Alternatively



$$R_{eq} = R/2$$

$$P = E^2/R_{eq} = 2E^2/R$$

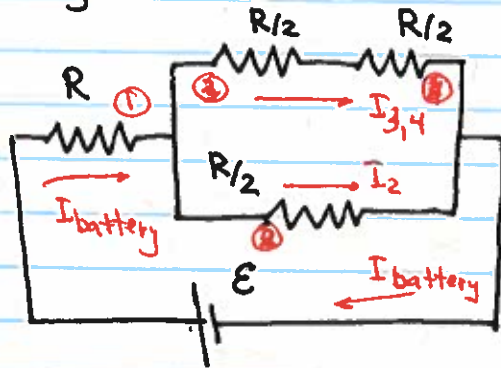Circuits with one battery and many resistors



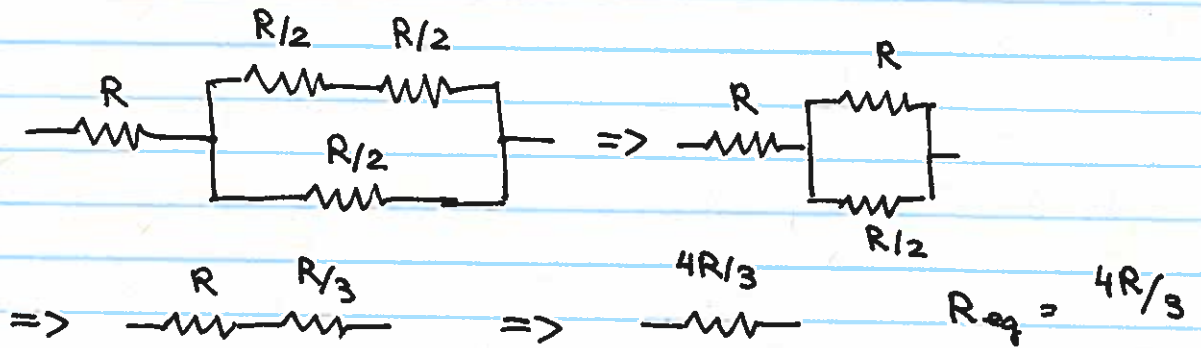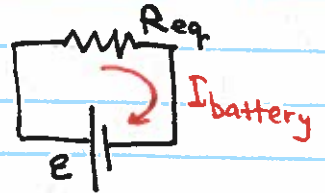1. Let's find  $I_{\text{battery}}$  by calculating the equivalent resistance




$$I_{\text{battery}} = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{3\mathcal{E}}{4R}$$

What is the current and the voltage drop on each of the resistors?

Resistor	Current	Voltage
1	$I_1 = I_{\text{battery}}$	$V_1 = R \cdot I_{\text{battery}} = 3\mathcal{E}/4$
2	$I_2 = \frac{V_2}{R/2} = \frac{\mathcal{E}}{2R}$	$V_2 = \mathcal{E} - 3\mathcal{E}/4 = \mathcal{E}/4$
3, 4	$I_{3,4} = I_{\text{battery}} - I_2 = \frac{\mathcal{E}}{4R}$	$V_3 = V_4 = I_{3,4} \cdot \frac{R}{2} = \frac{\mathcal{E}}{8}$

We can use similar logic to figure out the equivalent capacitance

Parallel connection

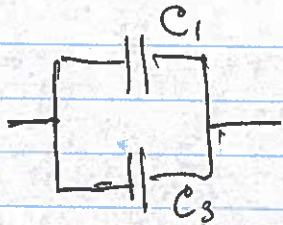

$$V_1 = V_2 = V_{tot}$$

$$Q_1 = V_1 \cdot C_1, \quad Q_2 = V_2 \cdot C_2$$

Total charge drawn from the battery:  $Q_{tot} = Q_1 + Q_2$

Equivalent capacitance:


$$V_{tot} = \frac{Q_{tot}}{C_{eq}} \Rightarrow C_{eq} = \frac{Q_{tot}}{V} = \frac{Q_1}{V} + \frac{Q_2}{V} = C_1 + C_2$$

~~$$C_{eq} = C_1 + C_2 + \dots$$~~

$$C_{eq} = C_1 + C_2 + (C_3 + \dots)$$


If originally the capacitors are not charged, each draws enough charge to ensure that voltages are the same.

Series connection

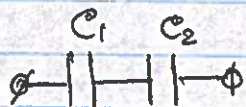

$$V_{tot} = V_1 + V_2$$

$$Q_{C1} = Q_{C2} = Q$$

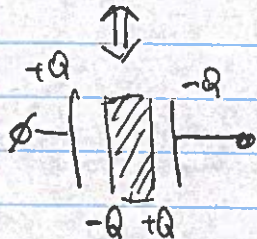

$$V_{tot} = \frac{Q}{C_{eq}} = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

Example 2

