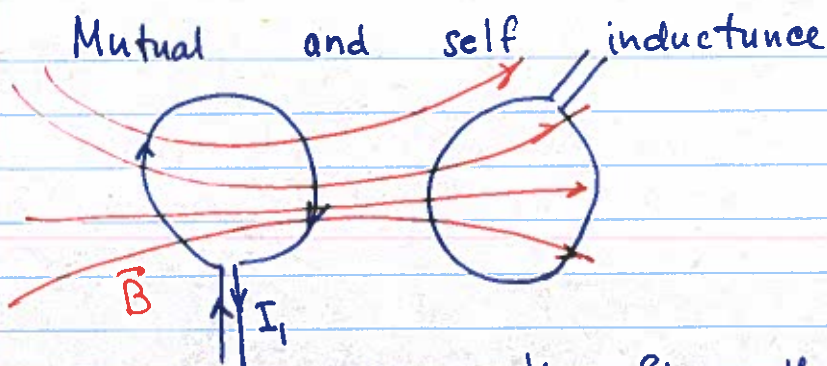





if I_1 is increasing, the flux through the second loop is increasing as well

$$\Phi = A \cdot B \propto I_1(t)$$

$$\mathcal{E}_{\text{ind}} = - \frac{d\Phi}{dt} \propto - \frac{dI_1(t)}{dt}$$

Mutual inductance

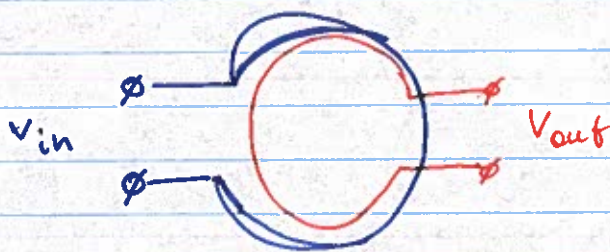Changing current in one loop creates Emf/voltage in the other, and vice versa.



$$\Phi_{\text{in}} = \Phi_{\text{out}}$$

for one loop

$$V_{\text{in}} |_{\text{one loop}} = - \frac{d\Phi_{\text{in}}}{dt}$$

||

$$V_{\text{out}} |_{\text{one loop}} = - \frac{d\Phi_{\text{out}}}{dt}$$

Φ flux for a single loop

Transformer

If we have different number of turns


$$V_{\text{in}} = - N_{\text{in}} \frac{d\Phi}{dt}$$

$$V_{\text{out}} = - N_{\text{out}} \frac{d\Phi}{dt}$$

$$\boxed{\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{N_{\text{out}}}{N_{\text{in}}}}$$

by changing the number of wraps, we can adjust output voltage

Induction coil / solenoid

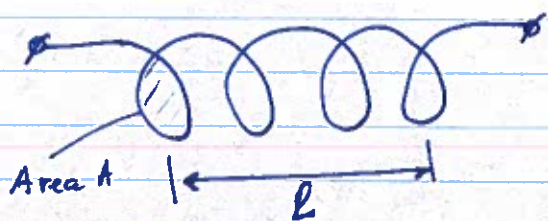

$$B = \mu_0 \frac{N}{l} \cdot I$$

N - # of turns
 l - length

Flux through the solenoid $\Phi = N \cdot A \cdot B$

$$\Phi = \underbrace{\frac{\mu_0 N^2 \cdot A}{l}}_{\text{set-up of the coil}} \cdot I = L \cdot I$$

$$L = \frac{\mu_0 N^2 \cdot A}{l} \quad \text{inductance}$$

$$L = \frac{\Phi}{I}$$

Changing current $I(t)$ changes the flux through the coil, producing additional EMF

$$\mathcal{E}_{\text{ind}} = \mathcal{E}_L = - \frac{d\Phi}{dt} = - L \frac{dI}{dt}$$


↑ Lenz rule again

EMF induced in a coil will oppose changes in current:

Current increases $\rightarrow$ induced $\mathcal{E}_L$ will ~~try~~ work against it

Current drops $\rightarrow$ induced $\mathcal{E}_L$ will work to prop it up

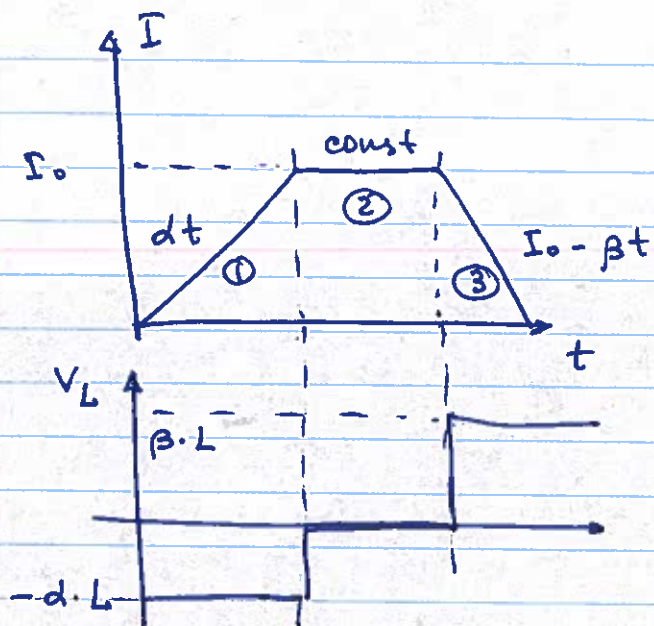Current constant $\rightarrow$ the coil behaves as a long piece of wire ($\mathcal{E}_L = 0$)




$$\textcircled{1} \quad \mathcal{E} = -L \frac{dI}{dt} = -dL$$


$$\textcircled{2} \quad \mathcal{E} = -L \frac{dI_0}{dt} = 0$$

$$\textcircled{3} \quad \mathcal{E} = -L \frac{d(I_0 - \beta t)}{dt} = \beta L$$

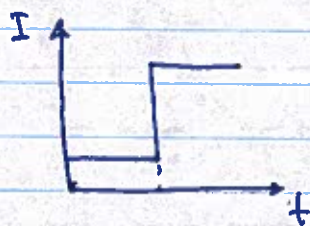It is impossible to change electric current through any inductor instantaneously



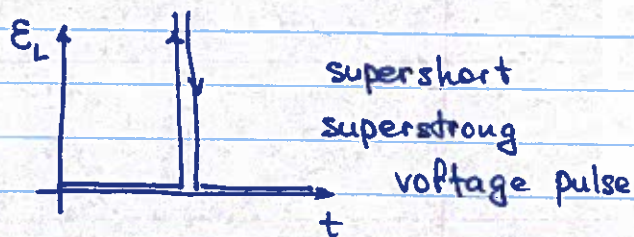
$$\mathcal{E}_L = -\frac{dI}{dt} \Rightarrow$$



(that's why we need surge protectors)

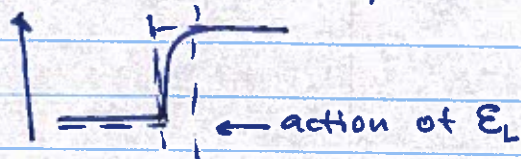Realistically, if ~~ever~~ anything changes in the circuit, the current won't change instantaneously, but develops EMF to maintain the previous current (for a moment), and then gradually adjusts.



(Unlike a resistor that reacts to voltage change instantly $V_R = R \cdot I$)

As time goes by $\mathcal{E}_{\text{ind}}(t) = I(t) \cdot R = 0$

$$-L \frac{dI}{dt} - I \cdot R = 0$$


$$\frac{dI}{dt} = -\frac{R}{L} I$$

Exponential solution $I(t) = I_0 e^{-t/\tau_{RL}}$

$$\frac{dI}{dt} = -\left(\frac{1}{\tau_{RL}}\right) I_0 e^{-t/\tau_{RL}} = -\left(\frac{R}{L}\right) I_0 e^{-t/\tau_{RL}}$$

$$\tau_{RL} = \frac{L}{R}$$

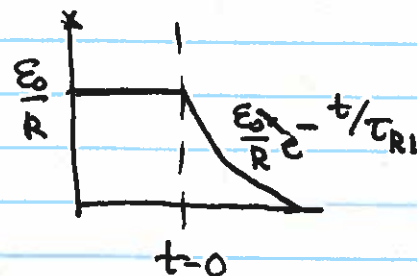Current $I(t) = \frac{\mathcal{E}_0}{R} e^{-R/L \cdot t}$



Switching from ~~position 1~~ to position 2 to




at $t=0$ $I=0$, at $t \rightarrow \infty$ $I = I_0 = \mathcal{E}_0/R$

at any time $\mathcal{E}_0 - IR - L \frac{dI}{dt} = 0$


$$I(t) = I_0 - I_0 e^{-t/\tau_{RL}} \quad \tau_{RL} = L/R$$

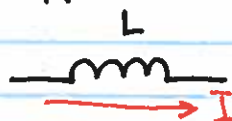The direction of the induced EMF always opposes the change of the current



Current increases

Current decreases

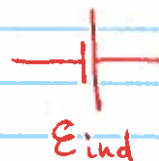

value $\mathcal{E}_{\text{ind}} = \left| -L \frac{dI}{dt} \right|$