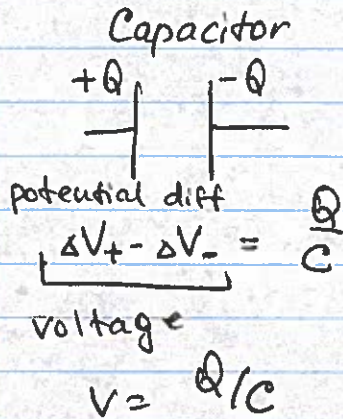


From electricity to electronics

Electricity (static)
 Electric field \vec{E}
 (stationary charges)
 Electric potential $V \Rightarrow \vec{E} = -\nabla V$

Electronics
 Electric current
 (moving charges)
 Potential difference - voltage

We know one element of the electronic circuit




Relations b/w voltage & charge
 $V = Q/C$

Energy stored in a capacitor
 $U_C = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{CV^2}{2}$

How to make charges move? We need a force

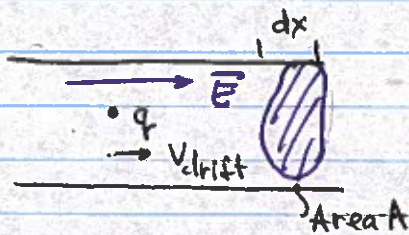Electric wire \rightarrow neutral conductor



$v_{drift} \propto E$
 (not obvious, discuss later)

To make it move, we need a force
 How much charge flow through A per unit time?

$$I = \frac{dQ}{dt} = \frac{q \cdot A \cdot n_q \cdot dx}{dt}$$

$$= q \cdot n_q \cdot A \cdot v_{drift} \propto \underbrace{q \cdot n_q \cdot A \cdot E}_{\text{depends on material}}$$

In general $I = A \cdot \sigma \cdot E = A \cdot \frac{1}{\rho} \cdot E$

σ - conductivity
 $\rho = \frac{1}{\sigma}$ - resistivity } material property

For historic reasons we consider current carrier positive charges

\vec{E} is constant inside the wire $E = \frac{V}{l}$

$$I = A \cdot \delta \cdot \frac{V}{l} \Rightarrow V = \frac{l}{A} I = I \left(\frac{\rho l}{A} \right)$$


R
resistance

Ohm's law $V = I \cdot R$

① We need voltage to create current

② If $R=0$ (ideal wires w/o resistance), $V=0$

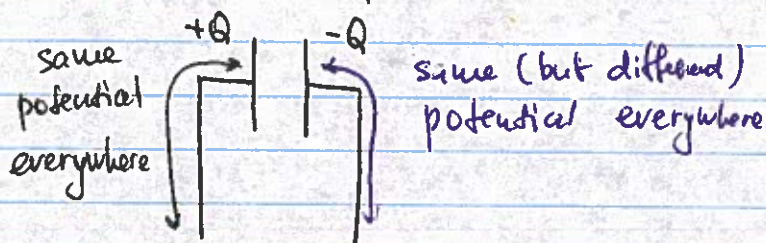Unless explicitly stated, we consider wires to have no resistance, so they connect points with same potential



To charge a capacitor we need to provide a source of electric force moving the charges

Electromotive force, or emf (ideal battery)


\mathcal{E} is the max constant voltage the battery provides

Common notation


$$V_A = V_B$$



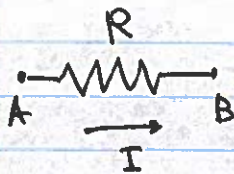- connecting wire. Normally no resistance, connects points with same potential



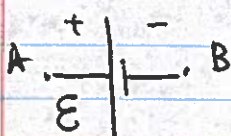- resistor; voltage drop across a resistor
 $V_A - V_B = IR$





- battery (emf)
 $V_A - V_B = E$


Some memory tricks I use!

1. "long" terminal of the battery is +, since one can break a longer stick in two pieces to make +

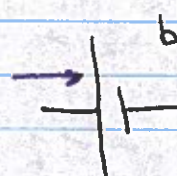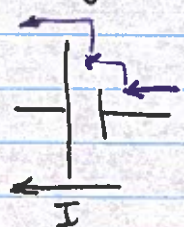2. The battery will try to push current from negative to positive terminal




A simplest circuit

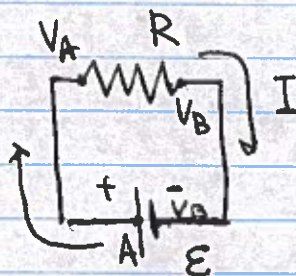

Since we (historically) assume positive current carriers, the current flows naturally from positive to negative terminal


$$V_B = V_A - IR$$

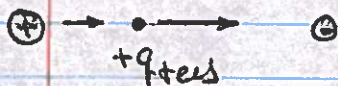

$$V_A = V_B + E = V_A - IR + E \Rightarrow IR = E$$

$$I = E/R$$

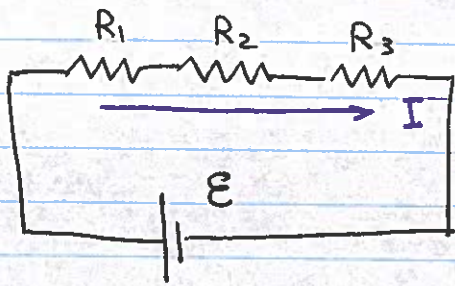If we have different resistors in series the current through all of them is the same




(because there is no other way for charges to go)

$$E = IR_1 + IR_2 + IR_3 = I(R_1 + R_2 + R_3)$$

voltage drop of each resistor


junction

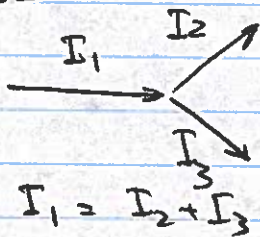

If a wire splits, currents add up
 $I_{\text{incoming}} = I_{\text{outgoing}}$

$$I_1 = I_2 + I_3$$

Parallel connection of resistors

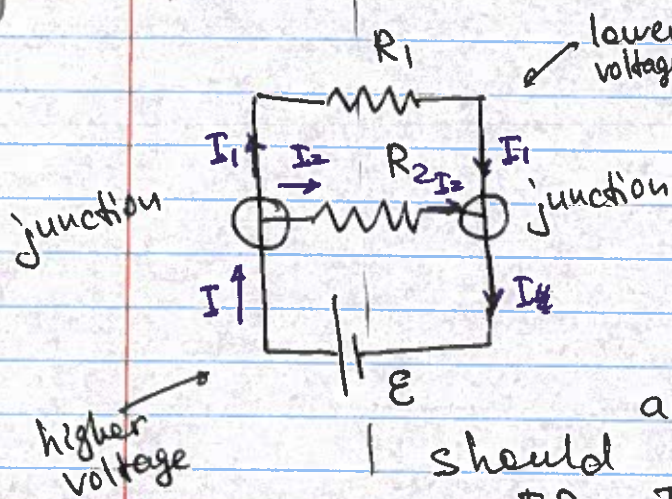

Here there is 3 different currents

On both junctions
 $I = I_1 + I_2$

Plus, voltage change across each element (here)

should be the same

$$I_1 R_1 = I_2 R_2 = E$$

$$I_1 = \frac{E}{R_1}$$

$$I_2 = \frac{E}{R_2}$$

$$I_{\text{tot}} = I_1 + I_2 = \frac{E}{R_1} + \frac{E}{R_2} = E \frac{R_1 R_2}{R_1 + R_2}$$