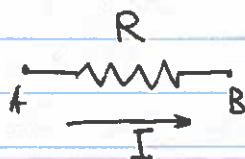


Basic circuit components


Resistor



$$V_R = V_B - V_A = -IR$$

voltage is proportional to current

Capacitor

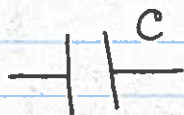


* empty capacitor = wire

$$V_C = Q/C = \frac{1}{C} \int_{-\infty}^t I(t') dt'$$

* full capacitor = no current
circuit break

Inductance

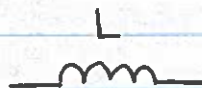


$$V_L = -L \frac{dI}{dt}$$

induced emf against current change

* immediately after - same current
current change (maintained by induced emf)

* in steady state = wire


Simple RL circuit

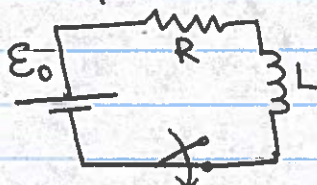

closed at $t=0$


$t = -0 \rightarrow$ no current

$t = +0 \rightarrow$ still no current

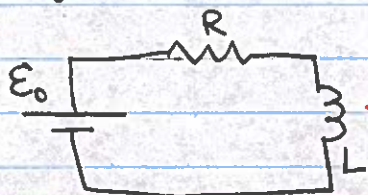


$$I(t=+0) = 0$$

$t \rightarrow \infty$

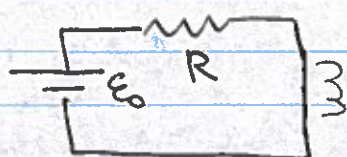
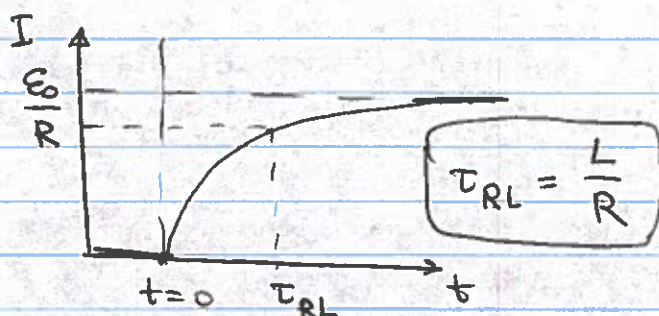
$$I(t \rightarrow \infty) = \frac{E_0}{R}$$



$$E_0 - IR - L \frac{dI}{dt} = 0$$

$$L \frac{dI}{dt} = E_0 - IR$$


$$\frac{L}{R} \frac{dI}{dt} = \frac{E_0}{R} - I$$

$$\int_0^{I(t)} \frac{dI}{\frac{E_0}{R} - I} = \int_0^t \frac{\frac{L}{R}}{\frac{L}{R}} dt$$

$$\ln \frac{\frac{E_0}{R} - I(t)}{\frac{E_0}{R}} = -\frac{R}{L} t$$


$$I(t) = \frac{E_0}{R} - \frac{E_0}{R} e^{-\frac{R}{L} t}$$

More complicated circuit

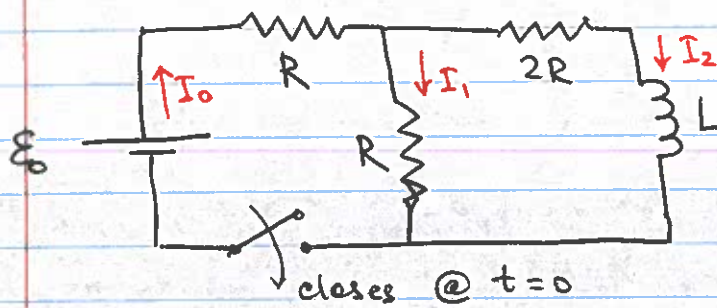


$$t < 0 \quad \begin{aligned} I &= 0 \\ I_1 &= 0 \\ I_2 &= 0 \end{aligned}$$

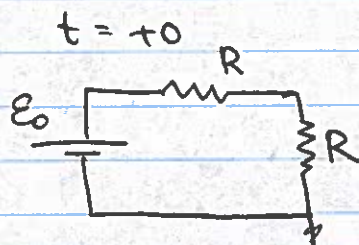Immediately after the switch is closed
 $I_2 = 0$ — no current in the second branch




$$I = I_1 = \epsilon_0 / 2R$$

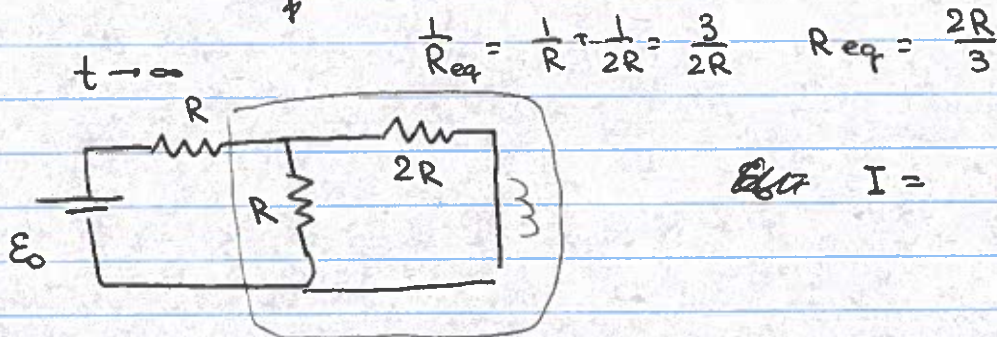

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{2R} = \frac{3}{2R} \quad R_{eq} = \frac{2R}{3}$$
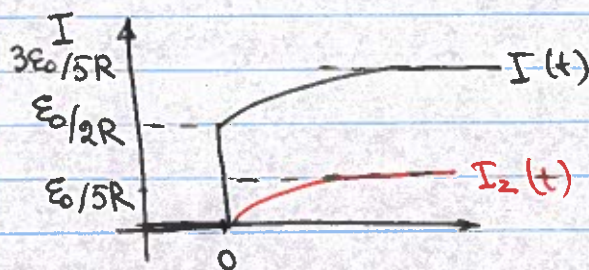
$$I = \frac{\epsilon_0}{R + \frac{2R}{3}} = \frac{3\epsilon_0}{5R}$$



Exact solution

- ① $I = I_1 + I_2$
- ② $\epsilon_0 - IR - I_1 R = 0$
- ③ $\epsilon - IR - I_2 \cdot 2R - L \frac{dI_2}{dt} = 0$


from ② $I_1 = \epsilon_0 / R - I$
 ① $I = \epsilon_0 / R - I + I_2 \Rightarrow I = \epsilon_0 / 2R + I_2 / 2$

$$-L \frac{dI_2}{dt} - \frac{5}{2} R I_2 + \frac{\epsilon_0}{2} = 0$$

$$I_2 = \frac{\epsilon}{5R} (1 - e^{-\frac{5R}{2L} \cdot t}) \quad \tau_{RL} = \frac{2L}{5R}$$

$$I = \frac{\epsilon_0}{2R} + \frac{1}{2} I_2 = \frac{3\epsilon_0}{5R} - \frac{\epsilon_0}{10R} e^{-t/\tau_{RL}}$$

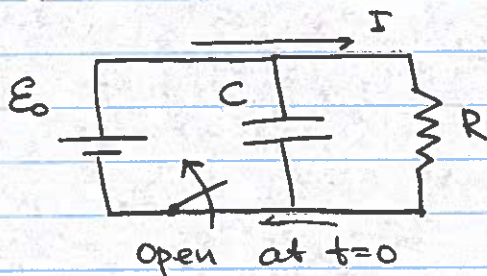Both a capacitor and an inductor serve as a storage of electric or magnetic energy that they release allows them ~~the~~ to delay the response to voltage or current change



$$t < 0 \quad I_R = E_0/R$$

$$V_C = E_0$$

no current through C

Once the battery is disconnected



$$V_C(t) - IR = 0$$


$$-IR + Q/C = 0$$

$$I = -dQ/dt$$



$$\tau_{RC} = RC$$

$$Q(t) = E_0 C e^{-t/\tau_{RC}}$$
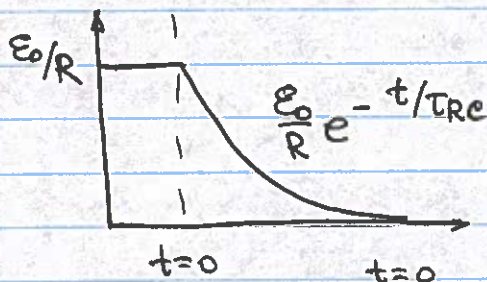
$$I(t) = \frac{E_0}{R} e^{-t/\tau_{RC}}$$



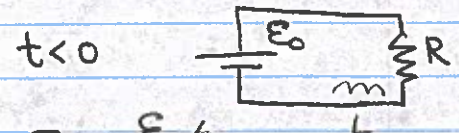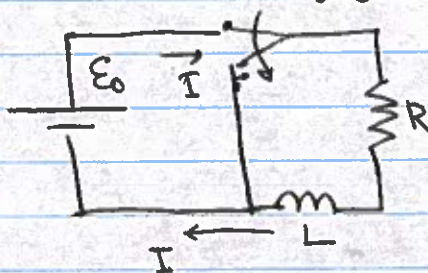
$$\frac{dQ}{dt} = -\left(\frac{1}{RC}\right) Q \quad 1/\tau_{RC}$$



$$I = E_0/R$$
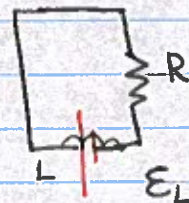
$$t = +0 \quad I = E_0/R \text{ still!}$$





$$E_L - IR = 0$$

$$-L \frac{dI}{dt} - IR = 0$$

$$\frac{dI}{dt} = -\left(\frac{R/L}\right) I \quad L/\tau_{RL}$$
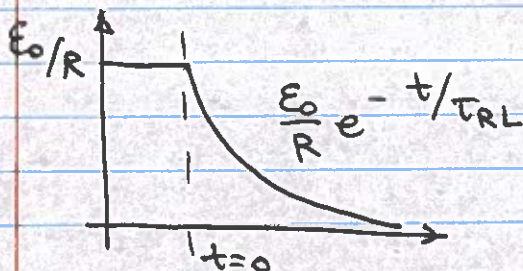
$$I(t) = \frac{E_0}{R} e^{-t/\tau_{RL}}$$



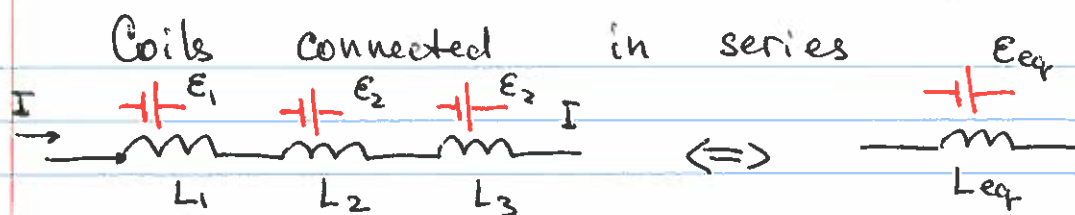


$$\mathcal{E}_1 = L_1 \frac{dI}{dt}, \quad \mathcal{E}_2 = L_2 \frac{dI}{dt}$$

$$\mathcal{E}_3 = L_3 \frac{dI}{dt}$$

$$\mathcal{E}_{\text{tot}} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 = \underbrace{(L_1 + L_2 + L_3)}_{L_{\text{eq}}} \frac{dI}{dt}$$

$$L_{\text{eq}} = L_1 + L_2 + L_3 \quad \text{for series connection}$$

Parallel connection

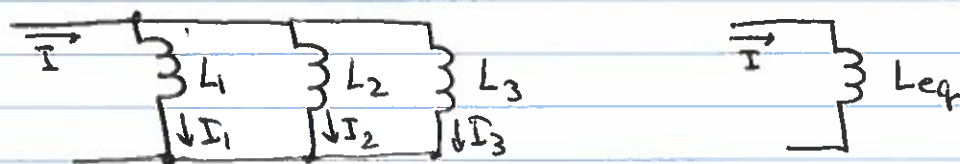

$$\mathcal{E}_{\text{ind}} = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} = L_3 \frac{dI_3}{dt}$$

$$\frac{dI_1}{dt} = \frac{\mathcal{E}}{L_1} \quad \frac{dI_2}{dt} = \frac{\mathcal{E}}{L_2} \quad \frac{dI_3}{dt} = \frac{\mathcal{E}}{L_3}$$

$$\frac{dI}{dt} = \frac{\mathcal{E}_{\text{eq}}}{L_{\text{eq}}} = \frac{d(I_1 + I_2 + I_3)}{dt}$$

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \quad \text{for parallel connection}$$