Resistors and simple network analysis

Eugeniy E. Mikhailov

The College of William & Mary



(마) (레) (토) (토) (토) 토 (키)(연 1/15

Eugeniy Mikhallov (vv&W)

lectronics 1

1 / 15

Notes


Analog Electronics goals

A major portion of the time spent preparing an experiment goes to design, construction, and interfacing different electronic components. Often, commercial circuitry is not available or it has to be matched with electronic front-ends (responsible for collecting usually weak signals) or back-ends (which do general purpose processing).

To perform above tasks we need:


- Lear basic discrete components
 - resistors, capacitors, inductors.
 - diodes, photo-diodes, transistors.
 - Op-amps, comparators.
- Multimeters, oscilloscopes, function generators.
- Breadboards and soldering irons.
- Modern circuit design and lay-out software.
- Master their usage

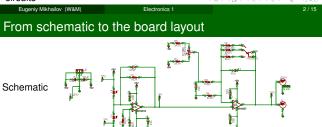As result we will be capable to build simple yet capable electronics circuits



Board layout

Hardware

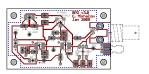



Eugenly Mikhailov (W&M) Electronics 1 3/1t

Evaluations

Your final grade for the course will be determined from the following grading weight distribution:

- Notebooks/Lab: 40% (design exercises 15%, lab 25%)
- Quizzes: 10%
- Participation: 5% (being in class is not enough)
- Midterm: 20%Final: 25%

Most labs will include a design component. The designs must be prepared prior to attending a lab. I will check preparation of the design exercise at the beginning of each lab. An unprepared/incomplete design exercise will have up to 50% penalty.

y Mikhailov (W&M) Electronics 1

Notes
Notes
Notes

Grades table

Grade	Score	Grade	Score	Grade	Score
		Α	94-100	A-	90-94
B+	87-90	В	84-87	B-	80-84
C+	77-80	С	74-77	C-	70-74
D+	67-70	D	64-67	D-	60-64
F	<60				

Eugenly Mikhailov (W&M)

Electronics 1

Electronics 1

Electronics 1

Your lab book is the primary record of your work and data.

- What you did.
- How you did it (e.g. circuit diagrams).
- How you made measurements (which test equipment and how it was connected).
- Your data and enough information to tell us what that data is.
- What you observed.
- Your calculations and analysis (including scratch work).
- Plots
- Answers to questions and justifications for your answers.

Diagrams, data, graphs, and other notes on separate pieces of paper should be glued, taped, or stapled into the lab book.

If something falls out of the lab book during reading, shaking, transporting, it is not the part of the log book and will be discarded.

extent on neatness.

Eugenly Mikhailov (W&M)

Electronics 1

6/15

Due days

Lab books are due by 5pm on next day after lab (i.e. Thursdays for the Wednesday section and Fridays for the Thursday section) and will be returned on Monday during the lecture time.

Late lab book submission will have points deducted. If you know you will have a problem getting the report on time please send me an email as soon as you can to let me know about your situation.

Illness

Please notify the instructor if you are ill, so that arrangements can be made to make up missed labs.

Eugeniy Mikhalov (W&M)

Electronics 1

Electronics 1

Electronics 1

Voltage (V)

Short for electrical potential difference Potential energy divided by charge (V = E/Q) Derived Unit: J/C

SI unit: V (Volt)

Current (I)

Rate of flow of electric charge (dQ/dt) SI unit: A (Ampere)

Power (P)

Energy per time (dE/dt) In electronics: P = VISI unit: W (Watt)

-	٦	-	
8		5	

Notes	
Notes	
Notes	
Notes	
Notes	

Electrical resistance

Resistance (R)

Different objects have different current passing through when the same voltage difference is applied.

Which indicates: they have different electrical resistance.

SI unit: Ω (Ohm)

900 E 4E 4 E 4 4 B 4 4 B 4

Eugeniy Mikhailov (W&M)

Liectronics

9 / 15

Notes

Notes

Ohm's law illustrated


Ohm's law

$$I = \frac{V}{R}$$

Ohm's law illustrated

Ohm's law

 $I = \frac{V}{B}$

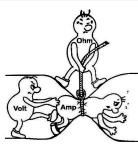

picture taken from www.sengpielaudio.com

Eugeniy Mikhailov (W&M)

←□→ ←□→ ←□→ ←□→ □

Resistors

Standard leaded Power



Surface mounted




Image from www.seed-solutions.com

Image from www.audionote.co.uk

4 D > 4 B > 4 E > 4 E > E 994


Notes

Notes

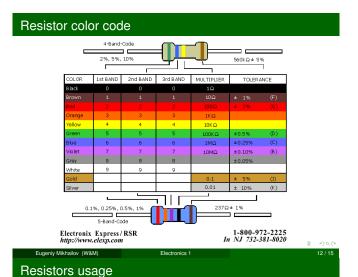

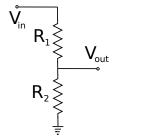- current limiters
- fix voltage from a current source (exotic use)
- generate heat
- fuse (non standard use)
- lowering the voltage of the source (i.e. voltage dividers)






$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

Eugenly Mikhailov (W&M)

Electronics 1

Loaded voltage divider

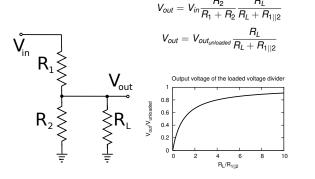

4 D > 4 B > 4 E > 4 E > E 9 Q @

niy Mikhailov (W&M) Electronic

Notes

Notes

Notes

Notes _____